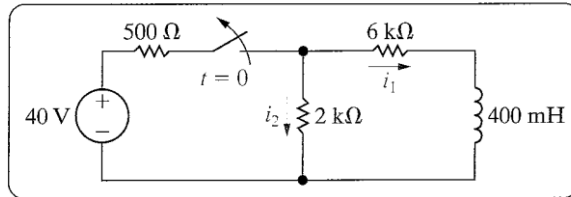


7.1 The switch in the circuit in Fig. P7.1 has been closed for a long time before opening at $t = 0$.



- Find $i_1(0^-)$ and $i_2(0^-)$.
- Find $i_1(0^+)$ and $i_2(0^+)$.
- Find $i_1(t)$ for $t \geq 0$.
- Find $i_2(t)$ for $t \geq 0^+$.
- Explain why $i_2(0^-) \neq i_2(0^+)$.


Figure P7.1



7.3 The switch shown in Fig. P7.3 has been open a long time before closing at $t = 0$.

- Find $i_o(0^-)$.
- Find $i_L(0^-)$.
- Find $i_o(0^+)$.
- Find $i_L(0^+)$.
- Find $i_o(\infty)$.
- Find $i_L(\infty)$.
- Write the expression for $i_L(t)$ for $t \geq 0$.
- Find $v_L(0^-)$.
- Find $v_L(0^+)$.
- Find $v_L(\infty)$.
- Write the expression for $v_L(t)$ for $t \geq 0^+$.
- Write the expression for $i_o(t)$ for $t \geq 0^+$.

Figure P7.3

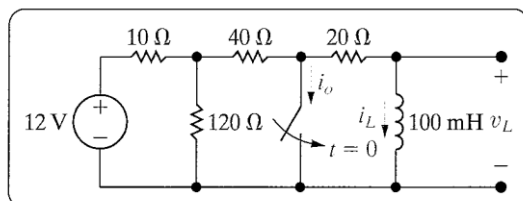

7.4 In the circuit in Fig. P7.4, the voltage and current expressions are


$$v = 400e^{-5t} \text{ V}, \quad t \geq 0^+;$$

$$i = 10e^{-5t} \text{ A}, \quad t \geq 0.$$

Find

- R .
- τ (in milliseconds).
- L .
- the initial energy stored in the inductor.
- the time (in milliseconds) it takes to dissipate 80% of the initial stored energy.

Figure P7.4

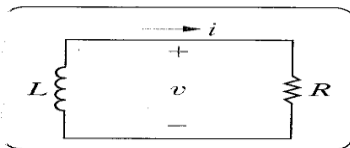


7.8 In the circuit shown in Fig. P7.8, the switch has been in position a for a long time. At $t = 0$, it moves instantaneously from a to b.

P

- Find $i_o(t)$ for $t \geq 0$.
- What is the total energy delivered to the 8Ω resistor?
- How many time constants does it take to deliver 95% of the energy found in (b)?


Figure P7.8

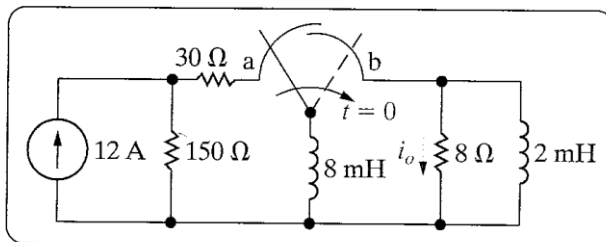

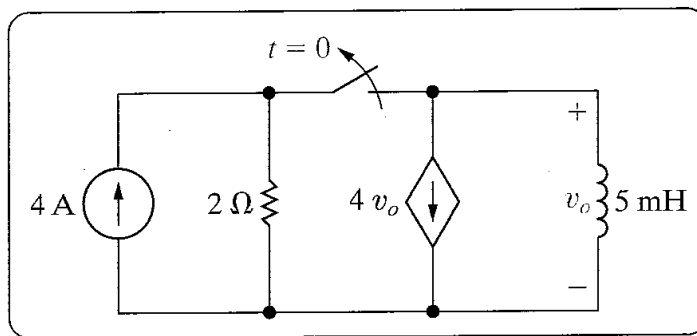- 7.13** The switch in the circuit in Fig. P7.13 has been closed for a long time before opening at $t = 0$. Find $v_o(t)$ for $t \geq 0^+$.

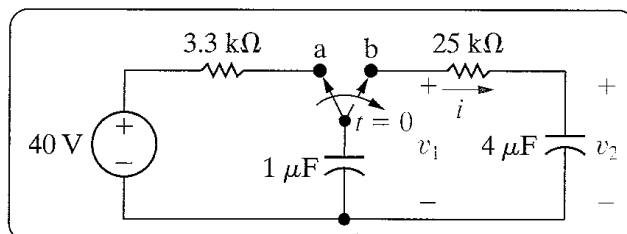


Figure P7.13



- 7.21** The switch in the circuit in Fig. P7.21 has been in position a for a long time. At $t = 0$, the switch is thrown to position b. Calculate
- i , v_1 , and v_2 for $t \geq 0^+$.
 - the energy stored in the capacitor at $t = 0$.
 - the energy trapped in the circuit and the total energy dissipated in the $25 \text{ k}\Omega$ resistor if the switch remains in position b indefinitely.

Figure P7.21



- 7.23** In the circuit in Fig. P7.23 the voltage and current expressions are


$$v = 48e^{-25t} \text{ V}, \quad t \geq 0;$$

$$i = 12e^{-25t} \text{ mA}, \quad t \geq 0^+.$$

Find

- R .
- C .
- τ (in milliseconds).
- the initial energy stored in the capacitor.
- the amount of energy that has been dissipated in the resistor 60 ms after the voltage has begun to decay.


Figure P7.23

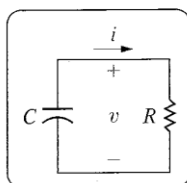

- 7.25** In the circuit shown in Fig. P7.25, both switches operate together; that is, they either open or close at the same time. The switches are closed a long time before opening at $t = 0$.

- How many microjoules of energy have been dissipated in the $12 \text{ k}\Omega$ resistor 12 ms after the switches open?
- How long does it take to dissipate 75% of the initially stored energy?


Figure P7.25

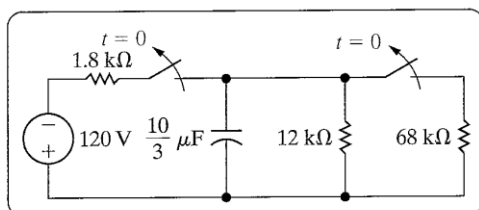

7.26 The switch in the circuit seen in Fig. P7.26 has been in position x for a long time. At $t = 0$, the switch moves instantaneously to position y.


- Find α so that the time constant for $t > 0$ is 40 ms.
- For the α found in (a), find v_{Δ} .

Figure P7.26

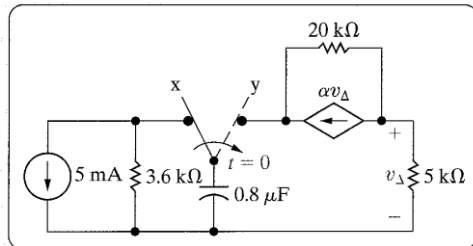

7.28 The switch in the circuit in Fig. P7.28 has been in position 1 for a long time before moving to position 2 at $t = 0$. Find $i_o(t)$ for $t \geq 0^+$.


Figure P7.28

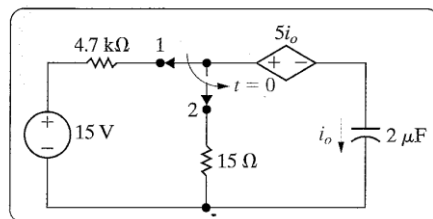

7.29 At the time the switch is closed in the circuit in Fig. P7.29, the voltage across the paralleled capacitors is 50 V and the voltage on the $0.25 \mu\text{F}$ capacitor is 40 V.

- What percentage of the initial energy stored in the three capacitors is dissipated in the $24 \text{ k}\Omega$ resistor?
- Repeat (a) for the 400Ω and $16 \text{ k}\Omega$ resistors.
- What percentage of the initial energy is trapped in the capacitors?


Figure P7.29

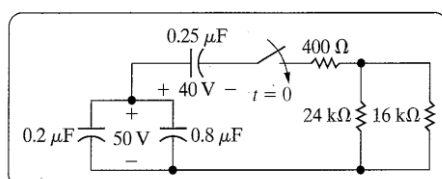

- 7.39** The switch in the circuit in Fig. P7.39 has been open a long time before closing at $t = 0$. Find $i_o(t)$ for $t \geq 0$.

P


Figure P7.39

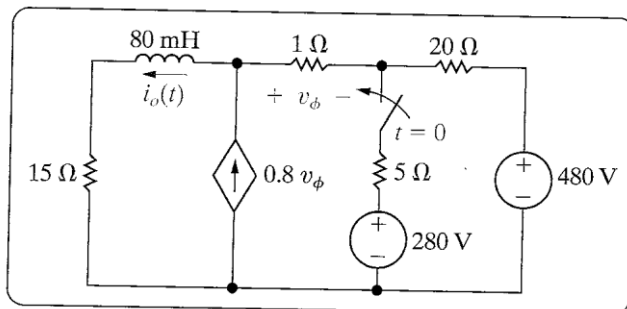

- 7.40** The switch in the circuit in Fig. P7.40 has been open a long time before closing at $t = 0$. Find $v_o(t)$ for $t \geq 0^+$.

P

Figure P7.40

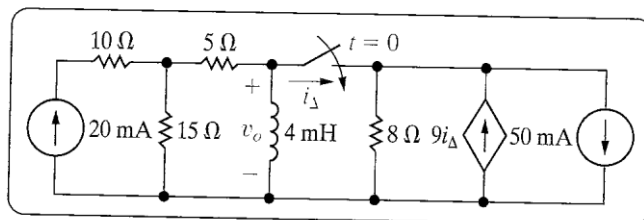


7.48 The switch in the circuit shown in Fig. P7.48 has been closed a long time before opening at $t = 0$. For $t \geq 0^+$, find

P

- $v_o(t)$.
- $i_o(t)$.
- $i_1(t)$.
- $i_2(t)$.
- $i_1(0^+)$.

Figure P7.48

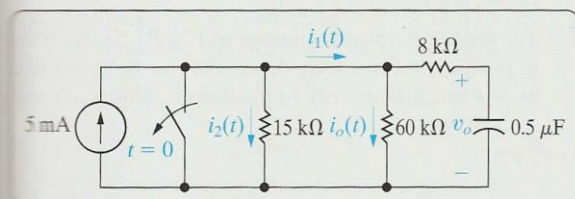

7.49 The current and voltage at the terminals of the capacitor in the circuit in Fig. 7.21 are

$$i(t) = 3e^{-2500t} \text{ mA}, \quad t \geq 0^+;$$

$$v(t) = (40 - 24e^{-2500t}) \text{ V}, \quad t \geq 0.$$

- Specify the numerical values of I_s , V_o , R , C , and τ .
- How many microseconds after the switch has been closed does the energy stored in the capacitor reach 81% of its final value?

7.50 The switch in the circuit in Fig. P7.50 has been in position x for a long time. The initial charge on the 10 nF capacitor is zero. At $t = 0$, the switch moves instantaneously to position y .

P

- Find $v_o(t)$ for $t \geq 0^+$.
- Find $v_1(t)$ for $t \geq 0$.

Figure P7.50

