

## OPERATIONAL AMPLIFIERS Lab#4

### Pre-lab #4

- 1- Calculate the theoretical gain of both the inverting and non-inverting amplifier circuit.

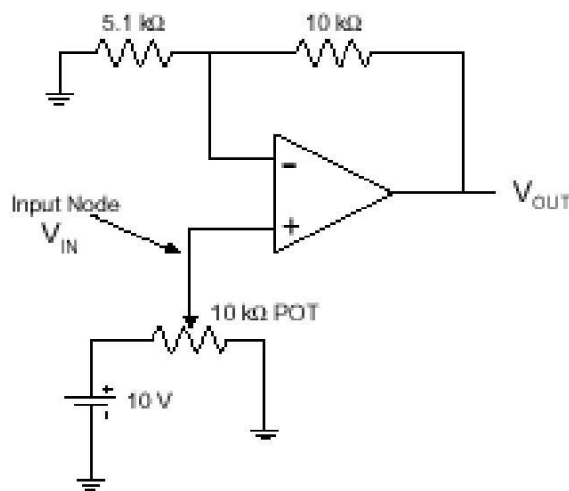


Figure 4.1

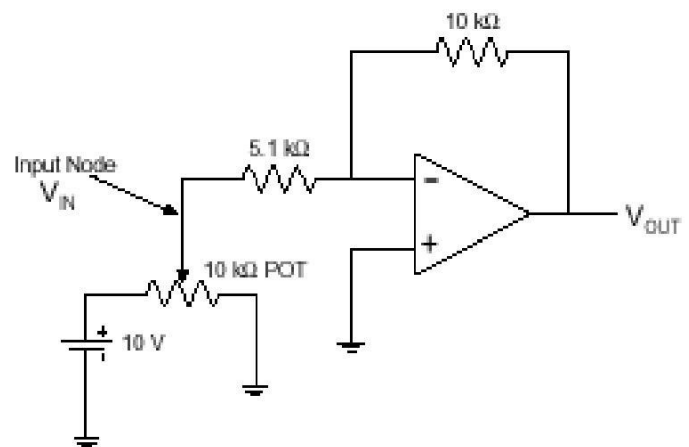


Figure 4.2


- 2- Find the datasheet of the LM741 and draw the internal block diagram.

## Instructional objective

In this experiment, the properties and some applications of operational amplifiers (opamps) will be studied. In particular, the **741 op-amp** will be considered.

## Procedure


1. Set up the circuit in Fig. 4.1:

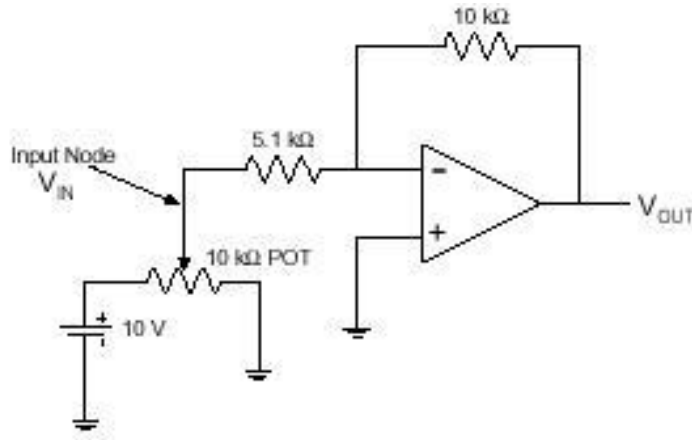

*Figure 4-1. Inverting Op-amp*

2. For the chip supply voltages connect pin 4 to  $-10\text{VDC}$  and pin 7 to  $+10\text{V DC}$ .
3. Adjust the  $10\text{ k}\Omega$  potentiometer (POT) until the voltage at the input node is 0.
4. Increase the voltage at the input node from 0 to 10 volts in 1 volt increments, recording the output voltage at each increment. These measurements will be used in the lab report to find the gain of the circuit and graph the input/output characteristics.

5. Construct Fig. 4.2:

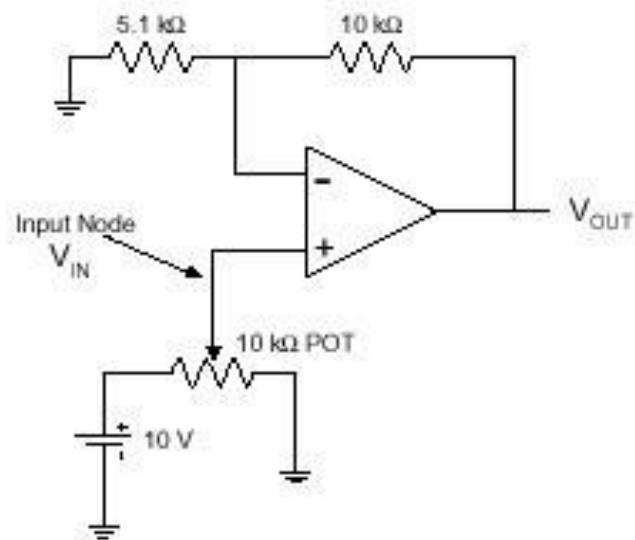

*Figure 4.2 - Non-Inverting Op-amp*

6. Repeat steps 2 through 4 for the non-inverting circuit.