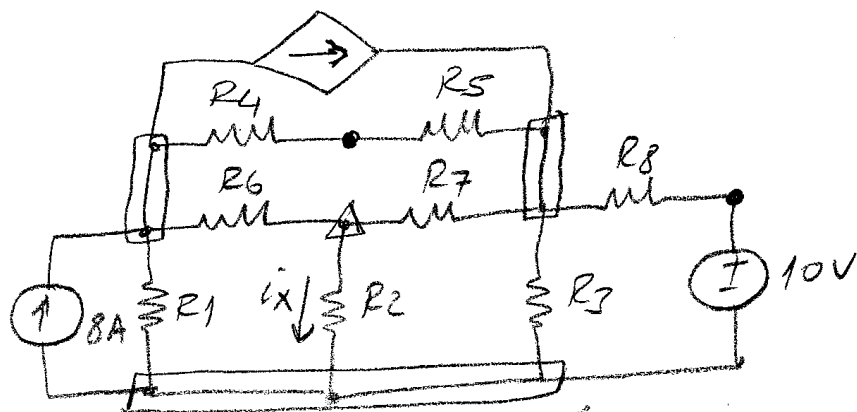



-1-
SOLUTIONS OF PROBLEM SET 4-1
41X

4-1



- a) There are 8 branches with resistors, 2 branches with independent sources, 1 branch with a dependent source.
- b) Except the branch containing the 8A current source, the current is unknown in all branches. Thus there are 10 branches with unknown current.
- c) 9 essential branches R_4 - R_5 forms an essential branch as does R_8 -10V. The remaining seven branches are essential branches that contain a single element.
- d) The current is known only in the essential branch containing the current source, and is unknown in the remaining 8 branches.
- e) From the figure there are 6 nodes - three identified by rectangular boxes, two identified with single dots, and one identified by a triangle.
- f) There are 4 essential nodes, three identified with rectangular boxes and one identified with a triangle.
- g) A mesh is like a window pane, and as can be seen from the figure there are 6 window panes or meshes.


4-4

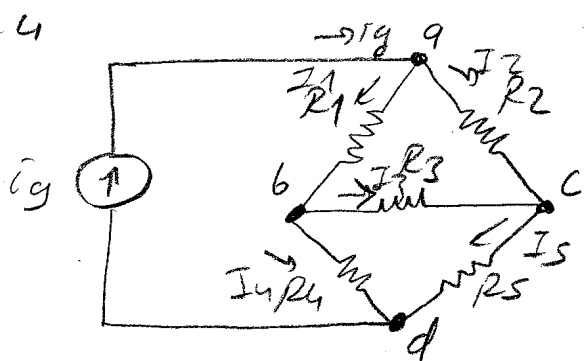

- a) There are 5 unknown currents.
 b) There are 4 nodes, 3 independent KCL equations can be written.

c) Node (a) $-I_g + I_1 + I_2 = 0$
 " (b) $-I_1 + I_3 + I_4 = 0$
 " (c) $-I_2 - I_3 + I_5 = 0$

6

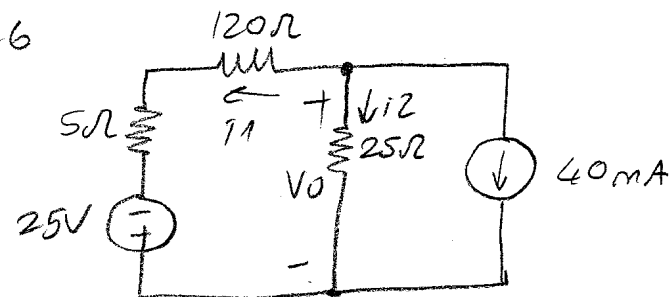

$$\frac{V_0 - (-25)}{125} + \frac{V_0}{25} + 0.04 = 0$$

$$V_0 + 25 + 5V_0 + 5 = 0$$

$$6V_0 = -30$$

$$V_0 = -5V$$

- a) $P_{40mA} = (-5V)(40mA) = -200mW = -0.2W$
 The power developed by the 40mA source is 0.2W.

b) $i_1 = \frac{V_0 + 25}{125} = \frac{-5 + 25}{125} = \frac{20}{125} = \frac{4}{25} = 0.16A$

$$P_{25V} = (-25V)(0.16A) = -4W$$

The power developed by the 25V source is 4W.


c) $P_{5\Omega} = (0.16A)^2(5\Omega) = 0.128W$

$$P_{120\Omega} = (0.16A)^2(120\Omega) = 3.072W$$

$$P_{25\Omega} = \frac{V_0^2}{25} = \frac{(-5V)^2}{25} = 1W$$

$$\Sigma P_{dissipated} = 0.128 + 3.072 + 1 = 4.2W$$
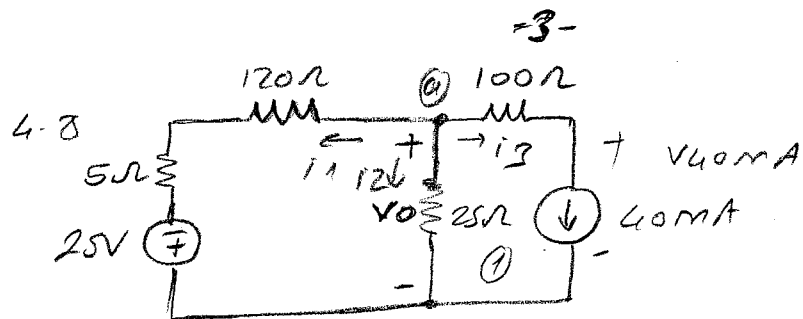
$$\Sigma P_{delivered} = 0.2 + 4 = 4.2W, \text{ the powers dissipated and delivered are equal.}$$



K-C-L at node (a) $\frac{V_0 - (-25)}{125} + \frac{V_0}{25} + 0.04 = 0$

$$V_0 + 25 + 5V_0 + 5 = 0 \Rightarrow 6V_0 = -30 \quad V_0 = -5V$$

b) $V_{40mA} = V_0 - 100 \times i_3 = -5V - 100(0.04A) = -9V$

$$P_{40mA} = (-9V)(0.04A) = -0.36W = -360mW$$

The power developed by the 40mA source is 360mW.

c) $i_1 = \frac{V_0 - (-25)}{125} = \frac{-5 + 25}{125} = \frac{20}{125} = \frac{4}{25} = 0.16A$

$$P_{25V} = (-25V)(0.16A) = -4W$$

The power developed by the 40mA source is 4W.

d) $P_{5\Omega} = (0.16A)^2(5\Omega) = 0.128W$

$$P_{120\Omega} = (0.16A)^2(120\Omega) = 3.072W$$

$$P_{25\Omega} = \frac{V_0^2}{25\Omega} = \frac{(-5V)^2}{25\Omega} = 1W$$

$$P_{100\Omega} = (0.04)^2(100\Omega) = 0.16W$$


$$\Sigma P_{dissipated} = 0.128 + 3.072 + 1 + 0.16 = 4.36W$$

$$\Sigma P_{developed} = 4 + 0.36 = 4.36W$$

The total power dissipated equals the total power delivered.

e) It will have no effect as V_0 is independent on the resistance connected in series, it only depends on the independent voltage source and on the independent current source.

4-12

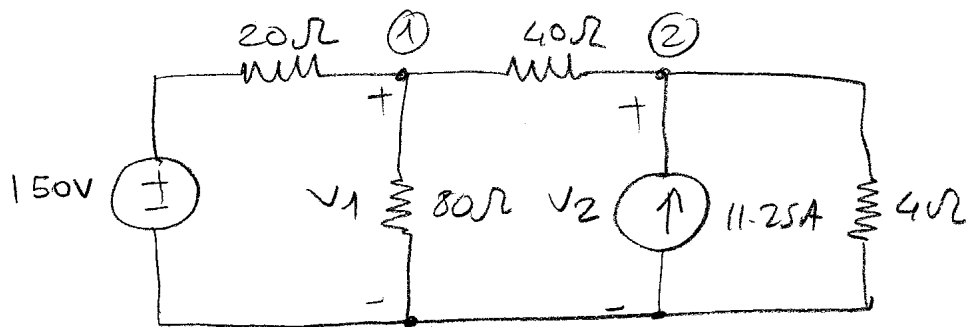

At Node 1
$$\frac{V_1 - 150}{20} + \frac{V_1}{80} + \frac{V_1 - V_2}{40} = 0$$

At Node 2
$$\frac{V_2 - V_1}{40} - 11.25 + \frac{V_2}{40} = 0$$

Multiplying equation 1 by 80, we get:

$$4(V_1 - 150) + V_1 + 2(V_1 - V_2) = 0$$

$$\text{I} \quad 7V_1 - 2V_2 = 600$$

Multiplying equation 2 by 40 we get

$$V_2 - V_1 - 450 + 10V_2 = 0$$

$$\text{II} \quad -V_1 + 11V_2 = 450$$

Solving for V_1 from II $V_1 = 11V_2 - 450$, and substituting this relationship into equation I

$$7(11V_2 - 450) - 2V_2 = 600$$

$$75V_2 - 3150 = 600$$


$$75V_2 = 3750$$

$$V_2 = 50V$$

substituting $V_2 = 50V$ into $V_1 = 11V_2 - 450$, we get

$$V_1 = 11 \times 50 - 450 = 100V$$

4-14 a)

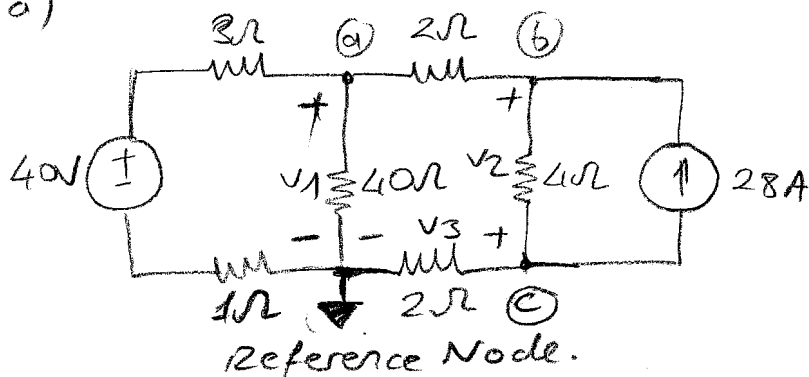

K-C-L of Node (a) $\frac{V_1 - 40}{4} + \frac{V_1}{40} + \frac{V_1 - V_2}{2} = 0$

" " " (b) $\frac{V_2 - V_1}{2} + \frac{V_2 - V_3}{4} - 28 = 0$

" " " (c) $\frac{V_3}{2} + \frac{V_3 - V_2}{4} + 28 = 0$

I $V_1 \left(\frac{1}{4} + \frac{1}{40} + \frac{1}{2} \right) - \frac{V_2}{2} = 10$


II $V_1 \left(-\frac{1}{2} + \frac{1}{4} \right) + \frac{V_2}{2} - \frac{V_3}{4} = 28$

III $V_2 \left(-\frac{1}{4} \right) + V_3 \left(\frac{1}{2} + \frac{1}{4} \right) = -28$

Solving: $V_1 = 60V$; $V_2 = 73V$; $V_3 = -13V$

$P_{28A} = -V_a(28A) = -(V_2 - V_3)(28A) = -(73 + 13)(28) = -2408W$

The 28 A source delivers 2408W

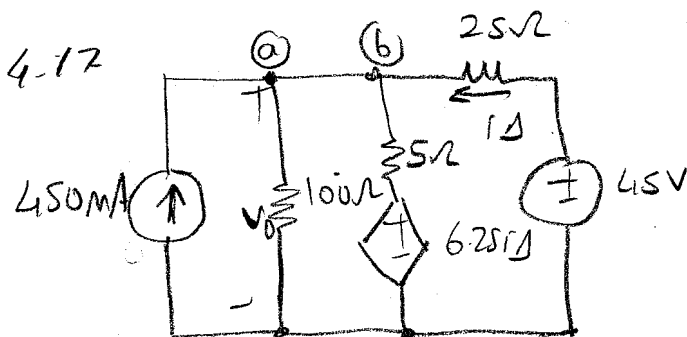

a) of Node (a) K-C-L

$$-0.45 + \frac{V_0}{100} + \frac{V_0 - 6.25V}{5} - 1 = 0$$

$I_\Delta = \frac{45 - V_0}{25} \Rightarrow$ substituting into K-C-L at node a.

$-0.45 + V_0 \left(\frac{1}{100} + \frac{1}{5} \right) + 1 \left(-\frac{6.25}{5} - 1 \right) = 0$

I $V_0 \left(\frac{1}{100} + \frac{1}{5} + \frac{1}{25} \right) + 1 \left(-\frac{6.25}{5} \right) = \frac{45}{25} + 0.45$

II $V_0 \left(\frac{1}{25} \right) + 1(1) = \frac{45}{25}$

Solving $V_0 = 45V$; $I_\Delta = 1.2A$

$$[6] \quad r_{ds} = \frac{v_o - 6.25V}{5} = \frac{15 - 7.5}{5} = 1.5A$$

$$p_{ds} = (6.25)(1.2)(1.5) = 11.25W$$

Thus dependent source absorbs 11.25W.

$$cc) \quad p_{usomA} = -(0.45)(15) = -6.75W$$

$$p_{usv} = -(1.2)(10.5) = -12.6W$$

$$\Sigma P_{dev} = 6.75 + 12.6 = 19.35W$$

Thus the independent source develops 19.35W

Also


$$\Sigma p_{dis} = p_{ds} + p_{100R} + p_{5R} + p_{25R}$$

$$= 11.25 + (1.5)^2 / 100 + (1.5)^2 (5) + (1.2)^2 (25)$$

$$= 11.25 + 2.25 + 11.25 + 36 = 60.75W$$

Total Power dissipated equals total power developed.

4-18

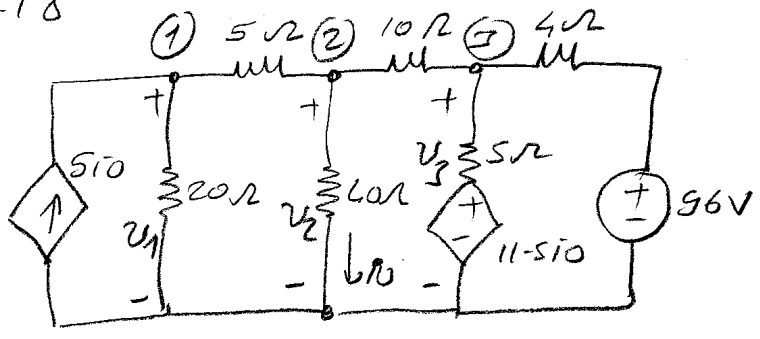

At node ① $-5 + \frac{v_1}{20} + \frac{v_1 - v_2}{5} = 0$

At node ② $\frac{v_2 - v_1}{5} + \frac{v_2}{40} + \frac{v_2 - v_3}{10} = 0$

At node ③ $\frac{v_3 - v_2}{10} + \frac{v_3 + 11.5}{5} + \frac{v_3 - 96}{4} = 0$

The dependent source constraint equation is:

$i_0 = v_2 / 40$

We place these equations in standard form:

$$v_1 \left(\frac{1}{20} + \frac{1}{5} \right) + v_2 \left(-\frac{1}{5} \right) + v_3(0) + i_0(-5) = 0$$

$$v_1 \left(-\frac{1}{5} \right) + v_2 \left(\frac{1}{5} + \frac{1}{40} + \frac{1}{10} \right) + v_3 \left(-\frac{1}{10} \right) + i_0(0) = 0$$

$$v_1(0) + v_2 \left(-\frac{1}{10} \right) + v_3 \left(\frac{1}{10} + \frac{1}{5} + \frac{1}{4} \right) + i_0 \left(-\frac{11.5}{5} \right) = \frac{96}{4}$$

$$v_1(0) + v_2 \left(-\frac{1}{40} \right) + v_3(0) + i_0(1) = 0$$

Solving we get $v_1 = 156V$; $v_2 = 120V$; $v_3 = 78V$; $i_0 = 3A$

(b) Calculate the power:

$P_{\text{current controlled current source}} = -[5(3)](156) = -2340W$

$P_{20\Omega} = (156)^2 / 20 = 1216.8W$

$P_{5\Omega} = (156 - 120)^2 / 5 = 259.2W$

$P_{40\Omega} = (120)^2 / 40 = 360W$

$P_{10\Omega} = (120 - 78)^2 / 10 = 176.4W$

$P_{5\Omega} = (78 - 11.5)^2 / 5 = 378.65W$

$P_{4\Omega} = (78 - 96)^2 / 4 = 81W$


$$P_{96V} = [(78-96)/4](96) = -432W$$

$$P_{\text{current controlled voltage source}} = [(78-3-11.5)/5](11.5-3) = 360.15W$$

$$\Sigma P_{\text{delivered}} = 2340 + 432 = 2772W$$

$$\Sigma P_{\text{dissipated}} = 1216.8 + 259.2 + 360 + 176.4 + 378.65 + 81 + 360.15 = 2772W$$

Thus, the circuit dissipates 2772W.

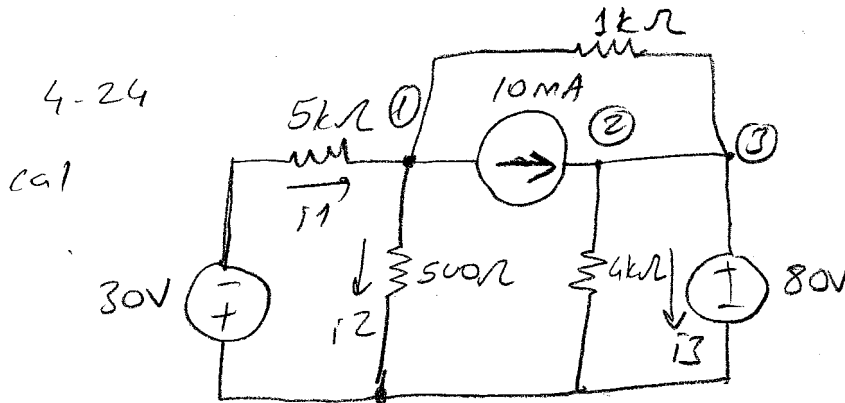

$$\textcircled{1} \quad \frac{V_1 + 30}{5} + \frac{V_1}{0.5} + 10 + \frac{V_1 - 80}{1} = 0$$

Solving

$$V_1 + 30 + 10V_1 + 5V_1 - 400 + 80 = 0, \text{ so } 16V_1 = 320$$

$$V_1 = 20V.$$

$$I_1 = -30 - 20 / 500 = -10mA$$

$$I_2 = 20 / 500 = 40mA$$

$$I_4 = 80 / 4000 = 20mA$$

$$I_3 = (80 - 20) / 1000 = 60mA$$

$$I_3 + I_4 + I_3 - 10mA = 0 \text{ so } I_3 = 0.01 - 0.02 - 0.06 = -0.07 = -70mA$$

$$a) \quad P_{30V} = (30)(-0.01) = -0.3W$$

$$P_{10mA} = (20 - 80)(0.01) = -0.6W$$

$$P_{80V} = (80)(-0.07) = -5.6W$$

$$P_{5k} = (1 - 0.01)^2(500) = 0.5W$$

$$P_{500\Omega} = (0.04)^2(500) = 0.8W$$

$$P_{1k} = (80 - 20)^2 / (1000) = 3.6W$$

$$P_{4k} = (80)^2 / (4000) = 1.6W$$


$$\Sigma P_{\text{TOTAL ABSORBED}} =$$

$$0.5 + 0.8 + 3.6 + 1.6 = 6.5W$$

$$\Sigma P_{\text{TOTAL DELIVERED}} =$$

$$0.3 + 0.6 + 5.6 = 6.5W$$

4-31

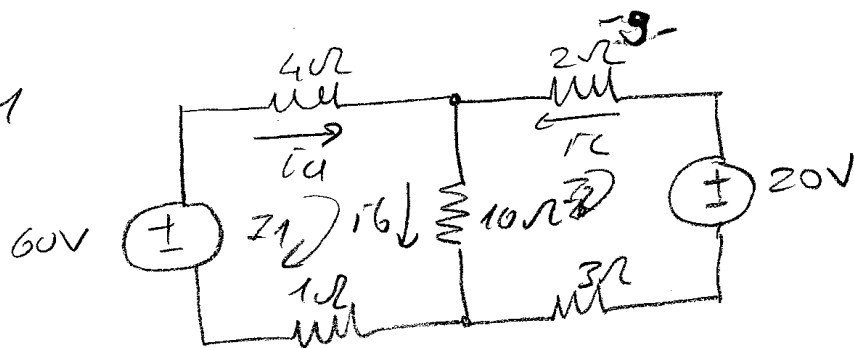

$$\textcircled{1} \quad -60 + 4I_1 + 10(I_1 - I_2) + I_1 = 0$$

$$\textcircled{2} \quad 2I_2 + 20 + 3I_2 + 10(I_2 - I_1) = 0$$

Rearranging the terms

$$15I_1 - 10I_2 = 60$$

$$-10I_1 + 15I_2 = -20$$

$$\rightarrow I_1 = \frac{\det \begin{vmatrix} 60 & -10 \\ -20 & 15 \end{vmatrix}}{\det \begin{vmatrix} 15 & -10 \\ -10 & 15 \end{vmatrix}}$$

$$I_2 = \frac{\det \begin{vmatrix} 15 & 60 \\ -10 & -20 \end{vmatrix}}{\det \begin{vmatrix} 15 & -10 \\ -10 & 15 \end{vmatrix}}$$

$$I_1 = \frac{1700}{175} = 9.71 \text{ A}$$

$$I_2 = \frac{300}{175} = 1.71 \text{ A}, \text{ Now using these mesh currents}$$

we solve for the requested currents:

$$i_a = i_1 = 9.71 \text{ A}; \quad i_b = i_1 - i_2 = 8 \text{ A}; \quad i_c = -i_2 = -1.71 \text{ A}$$

(6) If the polarity of the 60V source is reversed, we have the following mesh current equations in standard form:


$$i_1(4 + 10 + 1) + i_2(-10) = -60$$

$$i_1(-10) + i_2(3 + 10 + 2) = -20$$

$$\text{Solving } i_1 = -8.8 \text{ A}; \quad i_2 = -7.2 \text{ A}$$

$$i_a = i_1 = -8.8 \text{ A}, \quad i_b = i_1 - i_2 = -1.6 \text{ A}, \quad i_c = -i_2 = 7.2 \text{ A}$$

4-36

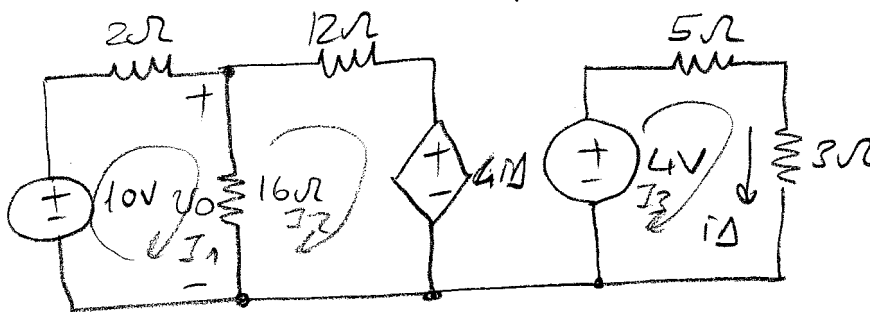

$$-10 + 2I_1 + 16(I_1 - I_2) = 0 \quad \text{I}$$

$$16(I_2 - I_1) + 12I_2 + 4I_2 = 0 \quad \text{II}$$

$$-4 + 5I_3 + 3I_3 = 0 \quad \text{III}$$

Solving for I_3 from III equation $\Rightarrow 8I_3 = 4 \Rightarrow I_3 = 0.5A$

Thus $I_3 = 0.5A$, substituting this value into the second equation and arranging terms, we get:

$$18I_1 - 16I_2 = 10$$

$$-16I_1 + 28I_2 = -2$$

$$\text{Solving for } I_1 = \frac{\det \begin{vmatrix} 10 & -16 \\ -2 & 28 \end{vmatrix}}{\det \begin{vmatrix} 18 & -16 \\ -16 & 28 \end{vmatrix}} = \frac{248}{248} = 1A$$

$$I_2 = \frac{\det \begin{vmatrix} 18 & 10 \\ -16 & 2 \end{vmatrix}}{248} = \frac{124}{248} = 0.5A$$


$$V_0 = 16(I_1 - I_2) = 16(1 - 0.5) = 8V$$

$$(c) P_{4\Omega} = 4I_2^2 = (4)(0.5)(0.5) = 1W \text{ absorbed}$$

Thus the power delivered by the 4Ω source is

$$P_{4\Omega} = -1W.$$

4-33

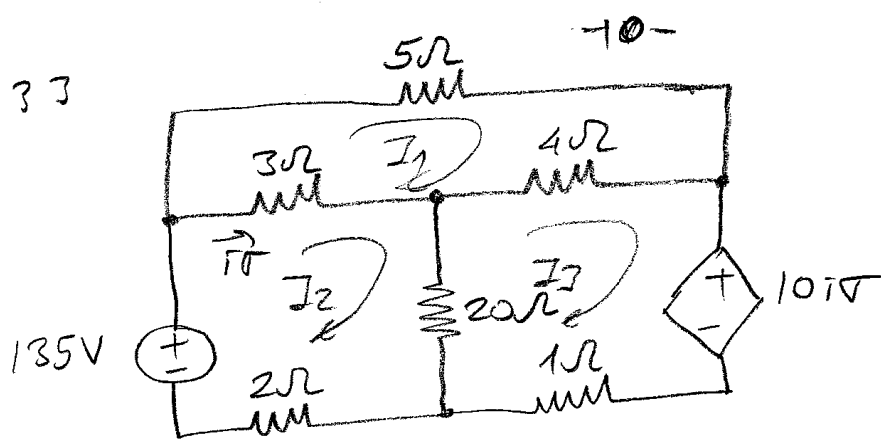

$$\text{Mesh ①: } 5I_1 + 4(I_1 - I_3) + 3(I_1 - I_2) = 0$$

$$\text{Mesh ②: } 3(I_2 - I_1) + 20(I_2 - I_3) + 2I_2 - 135 = 0$$

$$\text{Mesh ③: } 4(I_3 - I_1) + 10i_r + I_3 + 20(I_3 - I_2) = 0$$

We note that the branch current $i_r = I_2 - I_1$
and put the equations into standard form

$$\text{① } 12I_1 - 3I_2 - 4I_3 = 0$$

$$\text{② } -3I_1 + 25I_2 - 20I_3 = 135$$

$$\text{③ } 4(I_3 - I_1) + 10(I_2 - I_1) + I_3 + 20(I_3 - I_2) = 0$$

$$-14I_1 - 10I_2 + 25I_3 = 0$$


$$\text{the coefficient matrix } A = \begin{vmatrix} 12 & -3 & -4 \\ -3 & 25 & -20 \\ -14 & -10 & 25 \end{vmatrix}$$

$$\det A = 12 \begin{vmatrix} 25 & -20 \\ -10 & 25 \end{vmatrix} + 3 \begin{vmatrix} -3 & -20 \\ -14 & 25 \end{vmatrix} - 4 \begin{vmatrix} -3 & 25 \\ -14 & -10 \end{vmatrix} = 12 \times 625 + 3 \times (-355) - 4 \times 320$$

$$= 5100 - 1065 - 1280 = 2755$$

$$I_1 = \frac{\det \begin{vmatrix} 0 & -3 & -4 \\ 135 & 25 & -20 \\ 0 & -10 & 25 \end{vmatrix}}{2755} = \frac{\det \begin{vmatrix} -3 & -4 \\ -10 & 25 \end{vmatrix}}{2755} =$$

4-42

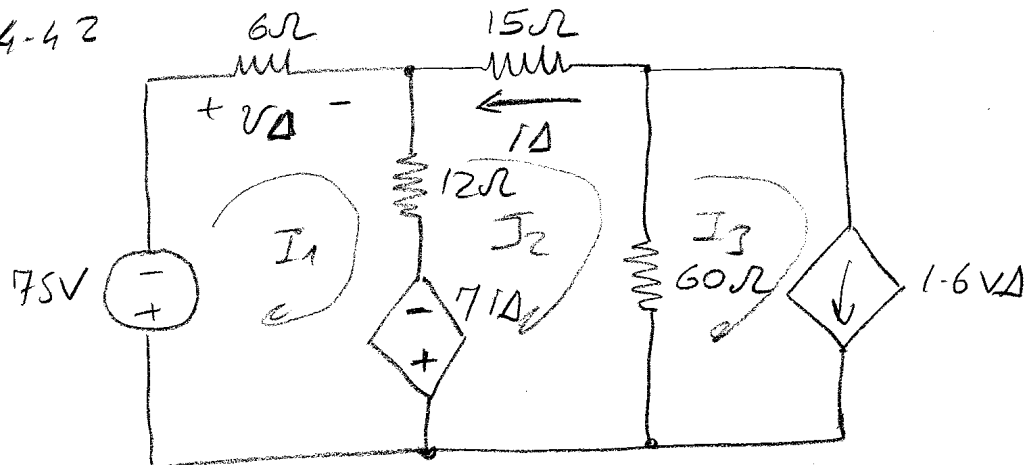

$$1 \quad 75 + 6I_1 + 12(I_1 - I_2) - 7I_\Delta = 0$$

$$2 \quad 15I_2 + 60(I_2 - I_3) + 7I_\Delta + 12(I_2 - I_1) = 0$$

We see that the branch current $I_\Delta = -I_2$ and

$$I_3 = 1.6V_\Delta \quad \text{as } V_\Delta = 6I_1 \Rightarrow I_3 = 1.6 \times 6I_1 = 9.6I_1$$

We can use $I_\Delta = -I_2$ and $I_3 = 9.6I_1$ to eliminate two of the unknowns from the first two equations.

$$1 \quad 75 + 6I_1 + 12(I_1 - I_2) + 7I_2 = 0$$

$$2 \quad 15I_2 + 60(I_2 - 9.6I_1) - 7I_2 + 12(I_2 - I_1) = 0$$

Arranging terms

$$1 \quad 18I_1 - 5I_2 = -75 \quad \rightarrow 5I_2 = 18I_1 + 75$$

$$2 \quad -588I_1 + 80I_2 = 0$$

substituting into the second equation.

$$-588I_1 + 16 \times 5I_2 \Rightarrow -588I_1 + 16 \times (18I_1 + 75) = 0$$

$$-588I_1 + 288I_1 + 1200 = 0$$

$$300I_1 = 1200 \quad I_1 = 4A$$

$$I_2 = \frac{18I_1 + 75}{5} = \frac{18 \times 4 + 75}{5} = 29.4A, \quad I_\Delta = -I_2 = -29.4A$$

$$I_3 = 1.6V_\Delta = 9.6 \times I_1 = 9.6 \times 4 = \underline{\underline{38.4A}}$$

-13-

Calculate the power associated with the three sources:

$$v = 60(i_2 - i_3) = -540V$$

$$v_d = 6i_1 = 6(4) = 24V$$

$$P_{75V} = (75)(4) = 300W$$

$$P_{\text{current controlled voltage source}} = -7(-29.4)(4 - 29.4) = -5227.32W$$

$$P_{\text{voltage controlled current source}} = (-540)[1.6(24)] = -20736W$$

The two dependent sources are generating a total of

$$5227.32 + 20736 = 25,963.32W$$

[6] Find the power dissipated. Remember that the 75V source is generating 300W, as calculated in part (a):

$$P_{6\Omega} = 6(4)^2 = 96W$$


$$P_{12\Omega} = (12)(4 - 29.4)^2 = 7741.92W$$

$$P_{15\Omega} = (15)(29.4)^2 = 12,965.4W$$

$$P_{60\Omega} = (60)(29.4 - 38.4)^2 = 6860W$$

$$\Sigma P_{\text{dissipated}} = 300 + 96 + 7741.92 + 12,965.4 + 6860 = 25,963.32W \text{ (checks).}$$

4-43

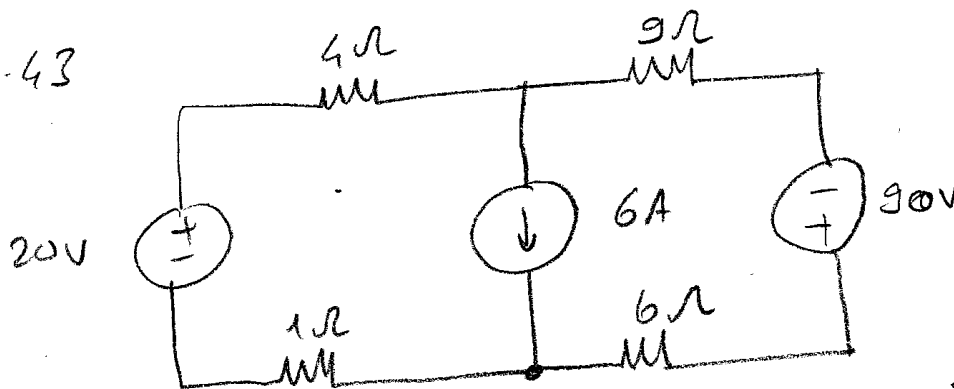

The supermesh equation is

$$-20 + 4i_1 + 9i_2 - 90 + 6i_2 + 11 = 0$$

$$i_1 - i_2 = 6$$

Placing these equations in standard form

$$i_1(4+1) + i_2(9+6) = 20+90$$

$$i_1(1) + i_2(-1) = 6 \quad \text{Solving } i_1 = 10A, \quad i_2 = 4A$$

Now we find the power: $P_{4\Omega} = 10^2(4) = 400W$ $P_{1\Omega} = 10^2(1) = 100W$

$$P_{9\Omega} = 4^2(9) = 144W \quad P_{6\Omega} = 4^2(6) = 96W \quad P_{20V} = -(20)(10) = -200W$$

$$v_{6A} = 9i_2 - 90 + 6i_2 = (9)(4) - 90 + (6)(4) = -30V \quad P_{90V} = -(90)(4) = -360W$$

$$\Sigma P_{\text{dev}} = 200 + 180 + 360 = 740W \quad \Sigma P_{\text{dis}} = 400 + 100 + 144 + 96 = 740W$$