

## Solutions of Problem Set 2

2-5 a) Yes the connection is valid, because independent sources can provide all the current required by the connection.

b) Considering the direction of 5mA current with respect to the voltage sources, we see that it enters both voltage sources at the positive terminal and leaves at the negative terminal, thus both independent voltage sources are absorbing power. The 5mA current source, however, is delivering power to the circuit.

$$(c) \quad P_{18V} = (5 \times 10^{-3})(18) = 90 \text{ mW (absorbing)}$$

$$P_{5mA} = -(5 \times 10^{-3})(25) = -125 \text{ mW (delivering)}$$

$$P_{7V} = (5 \times 10^{-3})(7) = 35 \text{ mW (absorbing)}$$

$$\sum P_{\text{absorbed}} = \sum P_{\text{delivered}} = 125 \text{ mW.}$$

(d) Yes, in that case 18V is delivering power, the 5mA current source and 7V voltage source are absorbing power.


$$P_{18V} = -(5 \times 10^{-3})(18) = -90 \text{ mW (delivering)}$$

$$P_{5mA} = (5 \times 10^{-3})(11) = 55 \text{ mW (absorbing)}$$

$$P_{7V} = (5 \times 10^{-3})(7) = 35 \text{ mW (absorbing)}$$

$$\sum P_{\text{absorbed}} = \sum P_{\text{delivered}} = 90 \text{ mW.}$$

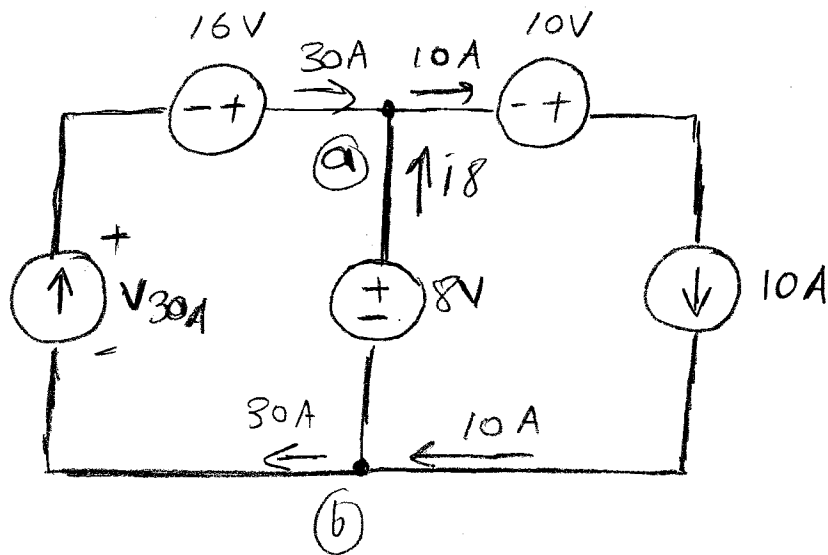2.7 We redraw the circuit assigning a current to the branch containing the 8V Voltage source.



We write Kirchhoff's current law at node (a)

$$-30 - i8 + 10 = 0 \quad i8 = -20A$$

Next we write Kirchhoff's current law at node (b)

$$-10 + i8 + 30 = 0 \quad i8 = -20A$$

As we get the same current value at both nodes, Kirchhoff's current law is not violated. We next write 3 Kirchhoff's voltage law equations, for the three possible loop (closed paths) of the circuit.

$$L_1: \text{left loop} = V_{30} + 16V - 8V = 0 \quad \text{I}$$

$$L_2: \text{right loop} = 8V + 10V - V_{10} = 0 \quad \text{II}$$

$$L_3 = \text{Max outer loop} = V_{30} + 16V + 10V - V_{10} = 0 \quad \text{III}$$

consisting of  $L_1$  &  $L_2$ .

$$\text{From equation I} \quad V_{30} = -8V$$

$$\text{From equation II} \quad V_{10} = 18V$$

Substituting these two voltage values into the third equation, we get

$$-8V + 16V + 10V - 18V = 0, \text{ thus Kirchhoff's voltage law is not violated either.}$$

Because both Kirchhoff's current law and Kirchhoff's voltage law are satisfied at all nodes and loops, the circuit is valid.

⇒ Next we use  $-3$ ,  $18$ ,  $10$  and  $10$  to determine the power associated with each source.

$$P_{30A} = -(30)(-8) = 240W \Rightarrow \text{absorbed}$$

$$P_{16V} = -(30)(16) = -480W \Rightarrow \text{delivered}$$

$$P_{8V} = (-20)(8) = 160W \Rightarrow \text{absorbed}$$

$$P_{10V} = -(10)(10) = -100W \Rightarrow \text{delivered}$$


$$P_{10A} = (10)(18) = 180W \Rightarrow \text{absorbed}$$

$$\Sigma P_{\text{absorbed}} = \Sigma P_{\text{delivered}} = 580W$$

$$P_{\text{C-sources}} = P_{30A} + P_{10A} = 240 + 180 = 420W$$

Since the power is positive, the sources are absorbing  $420W$  power.

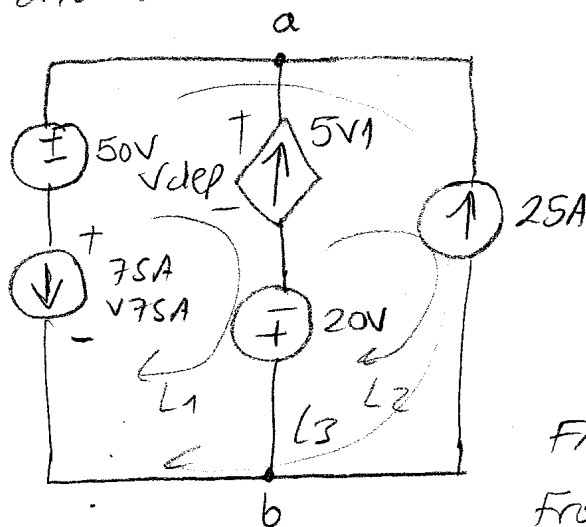2.11 We redraw the circuit labeling the nodes, loops, voltages and current sources.



Kirchoff's Current Law  
(K-C-L) at Node a ⇒

$$7SA - 5V\Delta - 2SA = 0$$

(K-C-L) at Node b ⇒

$$-7SA + 5V\Delta + 2SA = 0$$

$$\text{From a } 5V\Delta = 50 \quad V\Delta = 10V$$

From b, we get the same

result thus, K-C-L is satisfied at both nodes.

Next, we write the three loop equations:

$$\text{Loop 1: } V_{7SA} + 50V - V_{\text{dep}} + 20V = 0$$

$$\text{Loop 2: } -20V + V_{\text{dep}} - V\Delta = 0$$

$$\text{Loop 3: } V_{7SA} + 50V - V\Delta = 0$$

Substituting  $V\Delta = 10V$  into the second loop equation ⇒  $V_{\text{dep}} = 20 + V\Delta = 30V$

Substituting  $V\Delta = 10V$  into the third loop equation ⇒  $V_{7SA} = V\Delta - 50V = 10V - 50V = -40V$

Finally, we substitute these values to check that they satisfy the first loop's Kirchhoff's voltage Law equation.

$-40V + 50V - 30V + 20V = 0V \Rightarrow$  the first equation is satisfied. Kirchhoff's voltage law is not violated either. As neither Kirchhoff's current law, nor Kirchhoff's voltage law is violated, the circuit is valid.

$\Rightarrow V_0, V_{75}$  and  $V_{dep}$  will be used to determine the unknown power.


$$P_{50V} = (175)(50) = 3750W \quad P_{75A} = (175)(-40) = -3000W$$

$$P_{20V} = [5(10)](20) = 1000W \quad P_{\text{dependent source}} = -(50)(30) = -1500W$$

$$P_{2SA} = -(25)(10) = -250W$$

$$\Sigma P_{\text{delivered}} = 3750 + 1000 = 4750W = \Sigma P_{\text{absorbed}}.$$

2-14 We redraw the circuit

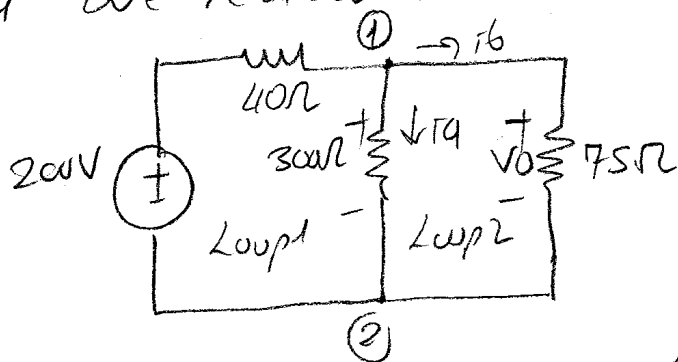

Kirchhoff's current law at Node ①

$$i_b + i_a - I = 0$$

Kirchhoff's voltage law at Loop ①  $-200 + 40I + 300i_a = 0$

Kirchhoff's voltage law at Loop ②

$$75i_b - 300i_a = 0$$

From ② equation  $i_b = 4i_a$  from ① equation

$$40I = 200 - 300i_a \Rightarrow I = \frac{1}{40}(200 - 300i_a) = 5 - 7.5i_a$$

Substituting  $I$  and  $i_b$  in terms of  $i_a$  into the first K-CL equation

$$4i_a + i_a - (5 - 7.5i_a) = 0 \Rightarrow 5i_a - 5 + 7.5i_a = 0$$

$$1.25i_a = 5 \quad i_a = \underline{\underline{0.4A}}$$

$$(b) \quad i_b = 4 \times i_a = 4 \times (0.4A) = \underline{\underline{1.6A}}$$

$$(c) \quad V_0 = 75 \times i_b = 75 \times (1.6A) = \underline{\underline{120V}}$$

$$(d) P_{40\Omega} = (140)^2 \cdot 40\Omega \quad I = 5 - 7.519 = 5 - 7.5 \times 0.6A = \underline{\underline{2A}}$$

$$P_{40\Omega} = (2A)^2 \cdot (40\Omega) = 160W$$

$$P_{300\Omega} = (I_{300})^2 (300\Omega) = I_0^2 \cdot 300\Omega = (0.4A)^2 (300\Omega)$$

$$P_{300\Omega} = 48W$$


$$P_{75\Omega} = (1.75)^2 \cdot (75\Omega) = (1.6)^2 \cdot 75\Omega = (1.6A)^2 (75\Omega) = 192W$$

$$P_{200V} = -(200V)I = -(200V)(2A) = -400W$$

↳ The minus sign comes from passive sign convention.

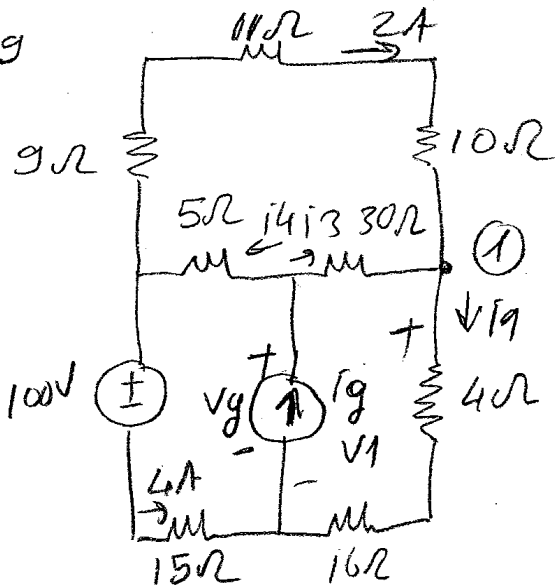(e)  $\sum P_{\text{dissipated}} = 160 + 48 + 92 = 400 \text{ W}$

$\Sigma P_{\text{delivered by the voltage source}} = 400 \text{ W.}$



$$v_2 = 100 + 4(15) = 160 \text{ V}$$

$$V_1 = 160 - 30(2) = 100 \text{ V}$$

$$I_1 = \frac{V_1}{20} = \frac{100}{20} = 5A,$$

Applying Kirchhoff's Current Law  
at node (1)

$$i_1 - 2 - i_3 = 0 \quad i_3 = i_1 - 2 = 5 - 2 = 3A$$

$$V_g = V_1 + 30V_3 = 100 + 30(3) = 190V$$

$$v_g = 5 - i_4 = v_2 \quad \text{thus} \quad 5i_4 = v_g - v_2 = 190 - 160 = 30V$$

Thus  $I_4 = \frac{30}{5} = 6A.$

we can now apply Kirchhoff's current law at node z, to determine the unknown current  $I_y$ .

$$r_9 = r_3 + r_4 = 3 + 6 = 9A.$$

(b) We calculate the powers dissipated by the resistors using the formula  $P = RI^2$

$$P_{9\Omega} = (9)(2)^2 = 36W; \quad P_{11\Omega} = (11)(2)^2 = 44W$$

$$P_{10\Omega} = (10)(2)^2 = 40W; \quad P_{30\Omega} = (30)(3)^2 = 270W$$

$$P_{5\Omega} = (5)(6)^2 = 180W; \quad P_{4\Omega} = (4)(5)^2 = 100W$$

$$P_{16\Omega} = (16)(5)^2 = 400W; \quad P_{15\Omega} = (15)(4)^2 = 240W$$

(c)  $V_g = 190V$

(d)  $\Sigma P_{\text{dissipated}} = 36 + 44 + 40 + 270 + 180 + 100 + 400 + 240$   
 $= 1310W$

The power of voltage source:  $P_V = (100V)(4A) = 400W$

" " current source:  $P_C = -V_g I_g = -(190V)(9A)$   
 $= -1710W.$

Thus the total power dissipated is 1710W and the total power developed is 1710W, so the power balances.


2.24. When  $i_a = 1A$ , the voltage drop across the  $180\Omega$  resistor must be  $V_{180\Omega} = (1A)(180\Omega) = 180V.$

$\Rightarrow$  Applying Kirchhoff's voltage law around the Loop 4  
 $V_{12} = 240V - 180V = 60V$  and  $i_1 = \frac{60V}{15\Omega} = 4A.$

$\Rightarrow$  Applying Kirchhoff's current law at node 2:  $-4A + i_a + i_2 = 0$  but  $i_a = 1A$   
 $-4A + 1A + i_2 = 0 \Rightarrow i_2 = 3A$

$\Rightarrow$  Now to determine the value of the variable resistor  $R$ , we have to use Ohm's law:  $R = \frac{V}{I}$ , but we do not know the voltage and the current. Let's first

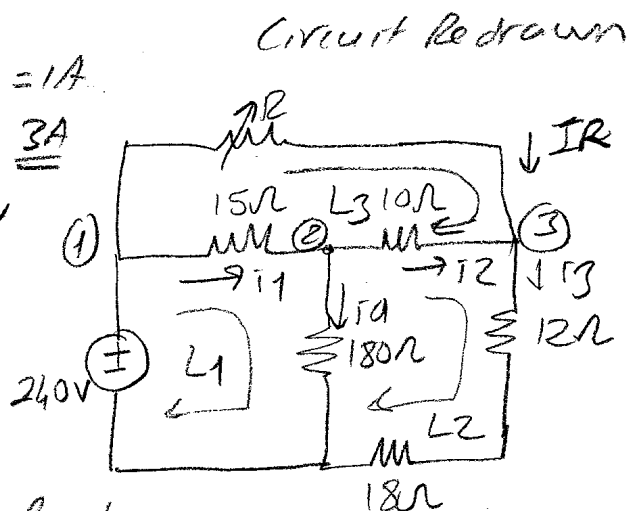determine  $V_R$ , the voltage across the variable resistor.



From Kirchhoff's Voltage law for Loop 3:  $V_R = (15\Omega)(4A) + (10\Omega)(3A)$

$$= 90V$$

$\Rightarrow$  Now, we apply Kirchhoff's current law at node 3, to determine  $I_R$ .

$$K-C-L \text{ III } I_3 - I_2 - I_R = 0 \text{ but } I_2 = 3A \text{ and } I_3 = \frac{V_3}{30\Omega}$$


$$V_3 = 180V - (10\Omega)I_2 = 180V - (10\Omega)(3A) = 150V$$

$$I_3 = \frac{150V}{30\Omega} = 5A \Rightarrow \text{substituting the value of } I_3 \text{ into the}$$

$$K-C-L \text{ equation II } 5A - 3A - I_R = 0 \Rightarrow I_R = 2A$$

$$\text{Finally } R = \frac{90V}{2A} = \underline{45\Omega}$$

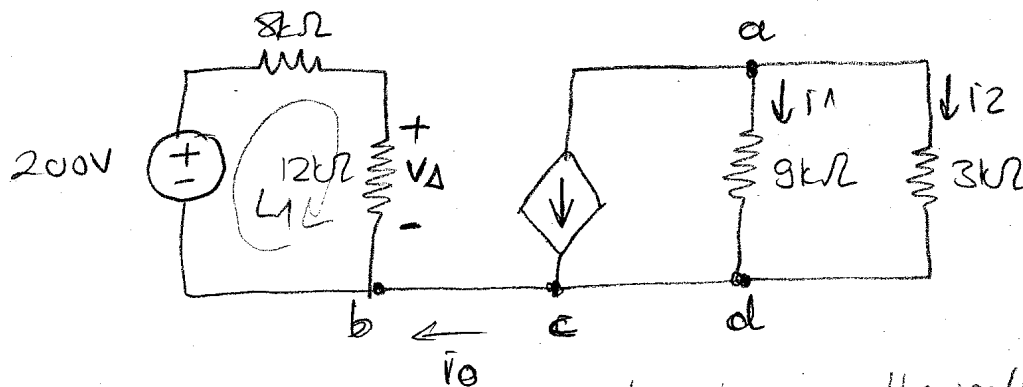2.28 We redraw the circuit labeling the nodes:




$\Rightarrow$  Solution Approach: If we had known the voltage at node a, we could have computed  $I_1$  &  $I_2$  and using Kirchhoff's current law at node c, we could have found the unknown current  $I_0$ . But we do not know the voltage at node a. We have to think of a different strategy. We first write the Kirchhoff's voltage law equations for the loop  $L_1$  containing the 200V voltage source.

$$K-V-L \text{ } L_1: -200V + 8k\Omega I + 12k\Omega I = 0$$

$$20k\Omega I = 200V$$

$$I = \frac{200V}{20k\Omega} = 10mA$$

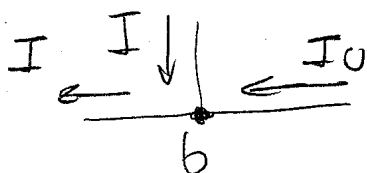Now we write, Kirchhoff's current law at node b.



$$I - I - I_0 = 0 \quad I_0 = 0$$

b) In order to find  $i_1$  and  $i_2$ , we first need to find the current supplied by the dependent source  $5 \times 10^{-3} v_\Delta$ , thus we determine  $v_\Delta$  first.

$$v_\Delta = 12k\Omega I = 12k\Omega \times 10mA = 120V$$

$$5 \times 10^{-3} v_\Delta = 5 \times 10^{-3} \times 120 = 0.6A$$


Now, we write Kirchhoff's voltage law equation for the loop containing the  $9k\Omega$  and  $3k\Omega$  resistors.

$$V_{9k\Omega} = V_{3k\Omega} = V_\Delta$$

From Ohm's law  $9k\Omega I_1 = 3k\Omega I_2 = V_\Delta$

$$\frac{I_1}{I_2} = \frac{1}{3} \quad I$$

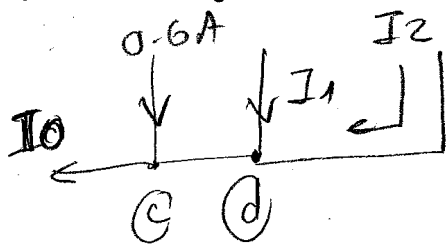We need one more equation to relate  $I_1$  and  $I_2$ , it can be found by writing Kirchhoff's current law at node d.



$$-0.6 - I_1 - I_2 = 0$$


$$I_1 + I_2 = -0.6 \quad II$$

Substituting  $I_2 = 3I_1$  from equation I,

$$I_1 + 3I_1 = -0.6 \quad 4I_1 = -0.6 \quad I_1 = -0.15A$$

$$I_2 = -0.45A$$

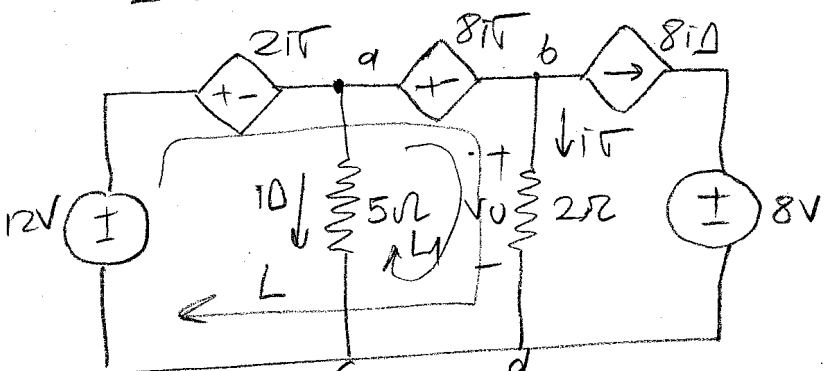2.30 We first redraw the circuit indicating the nodes:



Solution Analysis: To find  $i_\Delta$  we need to know  $v_\Delta$  as  $i_\Delta = \frac{v_\Delta}{5k\Omega}$ , but we don't know it. If we write Kirchhoff's voltage law for the loop containing the 12V source, we see that in addition

to  $i_\Delta$ , there will be a second unknown  $i_\Delta$  due to the dependent voltage source  $2kV$ . Thus writing Kirchhoff's voltage law equation for the leftmost loop, will not lead us any further. We should try another approach. Consider the loop L, consisting of the leftmost loop containing the voltage source and the loop bounded by nodes a, b, c, d.



If we write Kirchhoff's voltage law equation for this loop, the only unknown will be  $i_1$ , we should be able to determine  $i_1$  from this equation alone. Next we consider the loop surrounded by branches,  $ab$ ,  $bd$ ,  $dc$ ,  $da$ , if  $i_1$  is determined, the only unknown in this loop will be  $i_2$ , thus we will find the solution.

Kirchhoff's Voltage Law for Loop  $L_1$ :

$$-12V + 2i_1 + 8i_1 + 2i_1 = 0$$

$$12i_1 = 12V \Rightarrow i_1 = 1A$$

Kirchhoff's Voltage Law for Loop  $L_2$ :

$$-12V + 2 \times 1A + 5i_2 = 0$$

$$5i_2 = 10V \Rightarrow i_2 = 2A$$

$$V_0 = (2\Omega)(1A) = 2V$$

6) In order to show that the power developed equals to the power absorbed in the circuit, we have to determine all all powers delivered or absorbed by the sources and all powers dissipated (absorbed) by the resistances in the circuit. As we know the currents through the resistors, we can first find the power dissipated by them.

$$P = I^2 R \quad P_{5\Omega} = (2A)^2 (5\Omega) = 20W$$


$$P_{2\Omega} = (1A)^2 (2\Omega) = 2W$$

To determine the power of sources, we have to know the voltage and current of all sources. We start with the rightmost section of the circuit and work our way backwards to determine the unknown voltages and currents. The current through the 8V voltage source is  $8i_2 = 8(2A) = 16A$ .

$$P_{8V} = (8V)(8 \times 2A) = 128W.$$

We will now compute the voltage across the 8V dependent source. But we first have to determine the voltage across

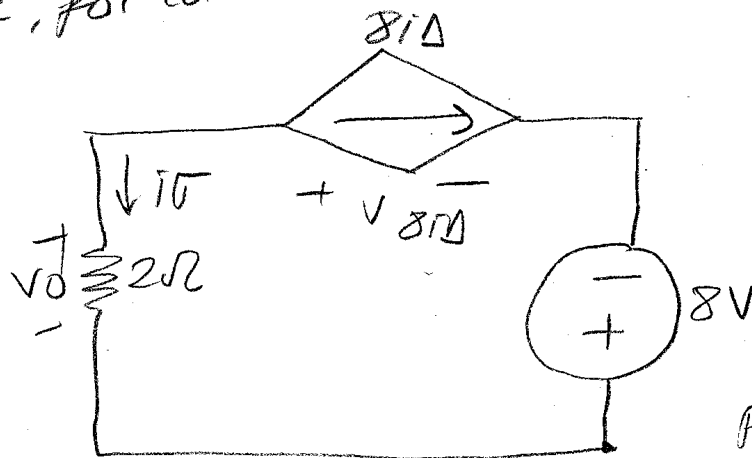70 -  
 this dependent current source, in order to find the power absorbed or delivered by it. Note the sign of the voltage across this source will tell us whether it is absorbing or delivering power to the circuit. We redraw the loop containing the dependent source here, for convenience.



Writing Kirchhoff's voltage law equation for this loop:

$$v_{8i_D} - 8V - v_D = 0 \Rightarrow v_D \text{ has been found to be } 4V.$$

$$v_{8i_D} = 8V + 4V = 12V.$$


$$P_{8i_D} = (12V)(8i_D) =$$

$$= (12V)(8 \times 2A) = -160W$$

⇒ Next, we need to determine the current  $i_D$  dissipating through the dependent voltage source  $8i_D$  to find the power supplied or delivered by it. The voltage of the source can be found easily as we already know  $i_D = 1A$ .

$$v = 8i_D = 8(1A) = 8V.$$

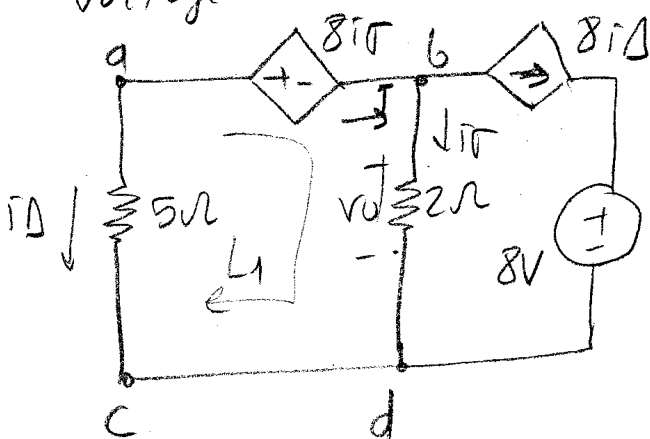We redraw the circuit's 2nd loop containing the  $8i_D$  dependent voltage source, and third loop containing  $8i_D$  dependent current source.



Kirchhoff's current law at node b, yields:


$$8i_D + i_D - i = 0 \text{ where } i_D = 2A, i_D = 1A,$$

$$i = 8 - (2A) + (1A) = 17A,$$

$$P_{8i_D} = -(8 \times 1)(17A) = -136W \text{ dissipating}$$

Finally, we compute the current at node a, to determine the power supplied by the 12V independent voltage source and  $2i_D$  dependent source.

Kirchhoff's Current law at node (a)

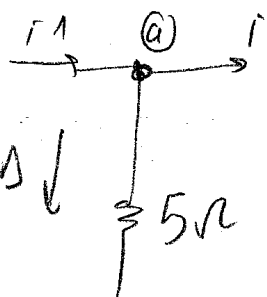

$$i_D + i - 11 = 0 \Rightarrow i = i_D + i = 2A + 17A = 19A$$

$$P_{2i_D} = -(2 \times 1A)(19A) = -38W \text{ dissipating}$$

$$P_{12V} = (12V)(19A) = 228W \text{ delivering}$$

$$\Sigma P_{\text{dissipated}} = 38W + 136W + 160W + 20W + 2W = 356W$$

$$\Sigma P_{\text{delivered}} = 228W + 128W = 356W$$