

EE 210 PROBLEM SET 3

- 1.8** Find the equivalent resistance R_{ab} for each of the circuits in Fig. P3.8.

P

Figure P3.8


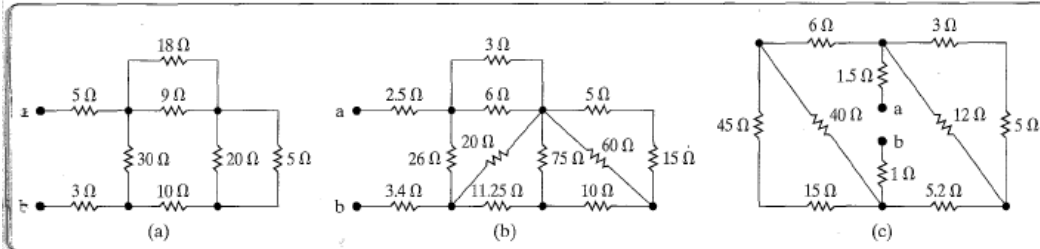


Figure P3.8

- 3.10** Find the power dissipated in the $5\ \Omega$ resistor in the circuit in Fig. P3.10.

P

Figure P3.10

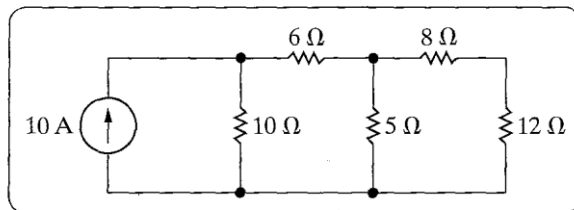


- 3.11** For the circuit in Fig. P3.11 calculate

P

- v_o and i_o
- the power dissipated in the $15\ \Omega$ resistor
- the power developed by the voltage source


Figure P3.11

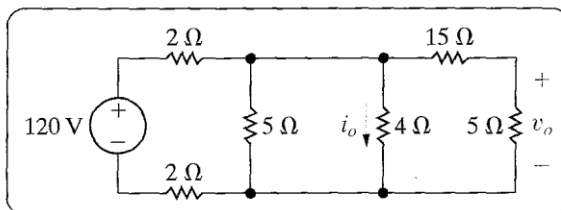

- 3.13**
- Calculate the no-load voltage v_o for the voltage-divider circuit shown in Fig. P3.13.
 - Calculate the power dissipated in R_1 and R_2 .
 - Assume that only 1 W resistors are available. The no-load voltage is to be the same as in (a). Specify the ohmic values of R_1 and R_2 .

P


Figure P3.13

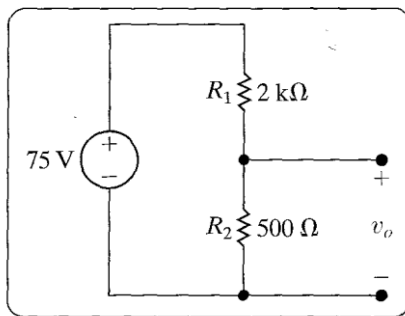

- 3.15** The no-load voltage in the voltage-divider circuit shown in Fig. P3.15 is 8 V. The smallest load resistance that is ever connected to the divider is $3.6 \text{ k}\Omega$. When the divider is loaded, v_o is not to drop below 7 V.


- Design the divider circuit to meet the specifications just mentioned. Specify the nominal value of R_1 and R_2 .
- Assume the power ratings of commercially available resistors are $1/16$, $1/8$, $1/4$, $1/2$, and 1 W . What power rating would you specify for R_1 and R_2 ?

Figure P3.15

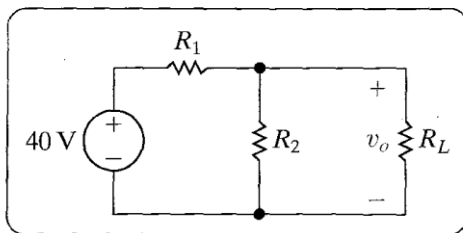


- 3.17** **P**
- a) The voltage divider in Fig. P3.17(a) is loaded with the voltage divider shown in Fig. P3.17(b); that is, a is connected to a', and b is connected to b'. Find v_o .
- b) Now assume the voltage divider in Fig. P3.17(b) is connected to the voltage divider in Fig. P3.17(a) by means of a current-controlled voltage source as shown in Fig. P3.17(c). Find v_o .
- c) What effect does adding the dependent-voltage source have on the operation of the voltage divider that is connected to the 240 V source?

Figure P3.17

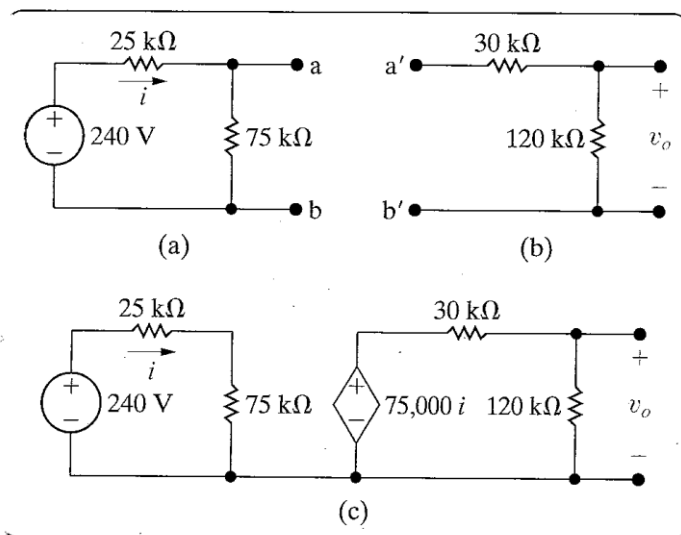

- 3.18** ❖ There is often a need to produce more than one voltage using a voltage divider. For example, the memory components of many personal computers require voltages of -12 V , 6 V , and $+12\text{ V}$, all with respect to a common reference terminal. Select the values of R_1 , R_2 , and R_3 in the circuit in Fig. P3.18 to meet the following design requirements:

Figure P3.18

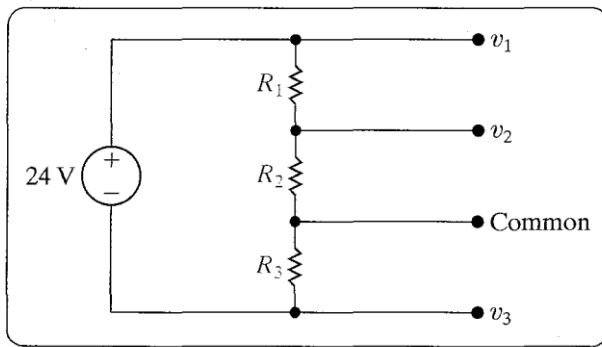


- The total power supplied to the divider circuit by the 24 V source is 36 W when the divider is unloaded.
- The three voltages, all measured with respect to the common reference terminal, are $v_1 = 12$ V, $v_2 = 6$ V, and $v_3 = -12$ V.

- 3.30** In the circuit in Fig. P3.30(a) the device labeled D represents a component that has the equivalent circuit shown in Fig. P3.30(b). The labels on the terminals of D show how the device is connected to the circuit. Find v_x and the power absorbed by the device.

P


Figure P3.30

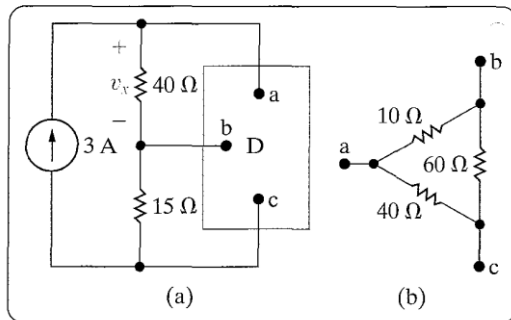

- 3.32** The ammeter in the circuit in Fig. P3.32 has a resistance of $0.1\ \Omega$. What is the percentage of error in the reading of this ammeter if


$$\% \text{ error} = \left(\frac{\text{measured value}}{\text{true value}} - 1 \right) \times 100?$$

Figure P3.32

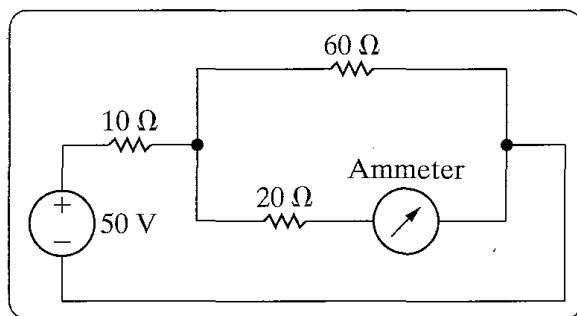

- 3.33** The ammeter described in Problem 3.32 is used to measure the current i_o in the circuit in Fig. P3.33. What is the percentage of error in the measured value?


Figure P3.33

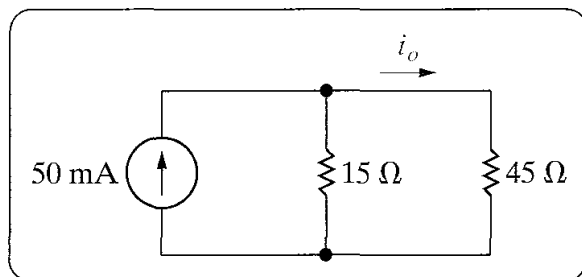

3.47 The circuit model of a dc voltage source is shown in Fig. P3.47. The following voltage measurements are made at the terminals of the source: (1) With the terminals of the source open, the voltage is measured at 50 mV, and (2) with a $15\text{ M}\Omega$ resistor connected to the terminals, the voltage is measured at 48.75 mV. All measurements are made with a digital voltmeter that has a meter resistance of $10\text{ M}\Omega$.

- What is the internal voltage of the source (v_s) in millivolts?
- What is the internal resistance of the source (R_s) in kilo-ohms?

Figure P3.47

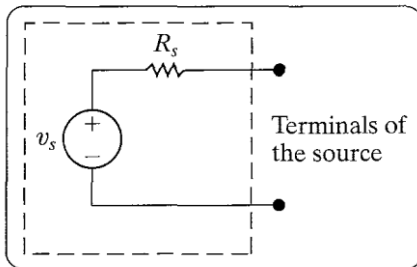


3.58

P

- Find the resistance seen by the ideal voltage source in the circuit in Fig. P3.58.
- If v_{ab} equals 400 V, how much power is dissipated in the $31\text{ }\Omega$ resistor?

Figure P3.58

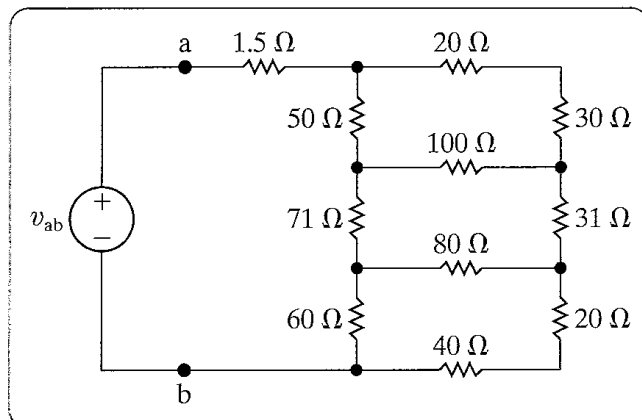

- 3.59** Use a Y-to- Δ transformation to find (a) i_o ; (b) i_1 ; (c) i_2 ; and (d) the power delivered by the ideal voltage source in the circuit in Fig. P3.59.

Fig. P3.59

