

-1-

EE 271 - FALL 2017 MIDTERM SOLUTIONS Instructor: Cenk Eker

$$1-\text{a)} \quad i(t) = \frac{d}{dt} \left[ \frac{1}{5} - (2t+4)e^{-0.5t} \right] = -\frac{d}{dt} \left[ (2t+4)e^{-0.5t} \right] \quad \langle 1 \rangle$$

$$i(t) = - \left[ 2e^{-0.5t} - 0.5e^{-0.5t}(2t+4) \right] = [0.5e^{-0.5t}(2t+4) + 2e^{-0.5t}]$$

$$i(t) = e^{-0.5t} [0.5(2t+4) + 2] = e^{-0.5t} [t+2-2] = te^{-0.5t} \quad t \geq 0 \quad \langle 2 \rangle$$

$$\frac{di(t)}{dt} = \frac{d}{dt} [te^{-0.5t}] = t e^{-0.5t} - 0.5e^{-0.5t} \cdot t = 0$$

$$\Rightarrow e^{-0.5t} [1 - 0.5t] = 0 \quad t=2 \quad \langle 2 \rangle$$

$$\begin{array}{c|ccccccc} t & & & & 2 \\ \hline \frac{di(t)}{dt} & & + & + & + & + & 0 & \dots \end{array}$$

$i(2) = 2e^{-1} = 0.735 \text{ A} \quad \langle 1 \rangle$  at  $t=2$  we have a local maximum.

$$\text{b)} \quad P = VI = e^{-0.5t} \cos \left[ \left( \frac{\pi}{3} \right) t \right] \cdot t \cdot e^{-0.5t} = e^{-t} \cdot t \cdot \cos \left[ \left( \frac{\pi}{3} \right) t \right] \quad \langle 3 \rangle$$

$$P = e^{-2} \cdot 2 \cdot \cos \left( \frac{2\pi}{3} \right) = 2 \cdot e^{-2} \left( -\frac{1}{2} \right) = -e^{-2} = -0.135 \text{ W} \quad \langle 3 \rangle$$

c) The circuit element is delivering power.  $\langle 6 \rangle$

$$2-\text{a)} \quad \text{Error} = \frac{I_{\text{MEASURED}} - I_{\text{TRUE}}}{I_{\text{TRUE}}} \quad , \quad I_{\text{TRUE}} = \frac{12V}{5k\Omega} = 2.4 \text{ mA}$$

$$-0.005 = \frac{I_M - 2.4}{2.4} \quad I_M = 2.4 - (5 \times 10^3)(2.4) \quad I_M = 2.388 \text{ mA}$$

$$I_M = \frac{12V}{5k\Omega + R_A} = 2.388 \text{ mA}$$

$$12 = (5k\Omega)(2.388 \text{ mA}) + (2.388 \text{ mA})R_A$$



$$R_A = \frac{12V - 11.94V}{2.388 \text{ mA}} = 0.025 \text{ k}\Omega \Rightarrow \underline{\underline{25 \Omega}}$$

-2-

b)

$$-0.001 = \frac{I_m - 2.4}{2.4}$$
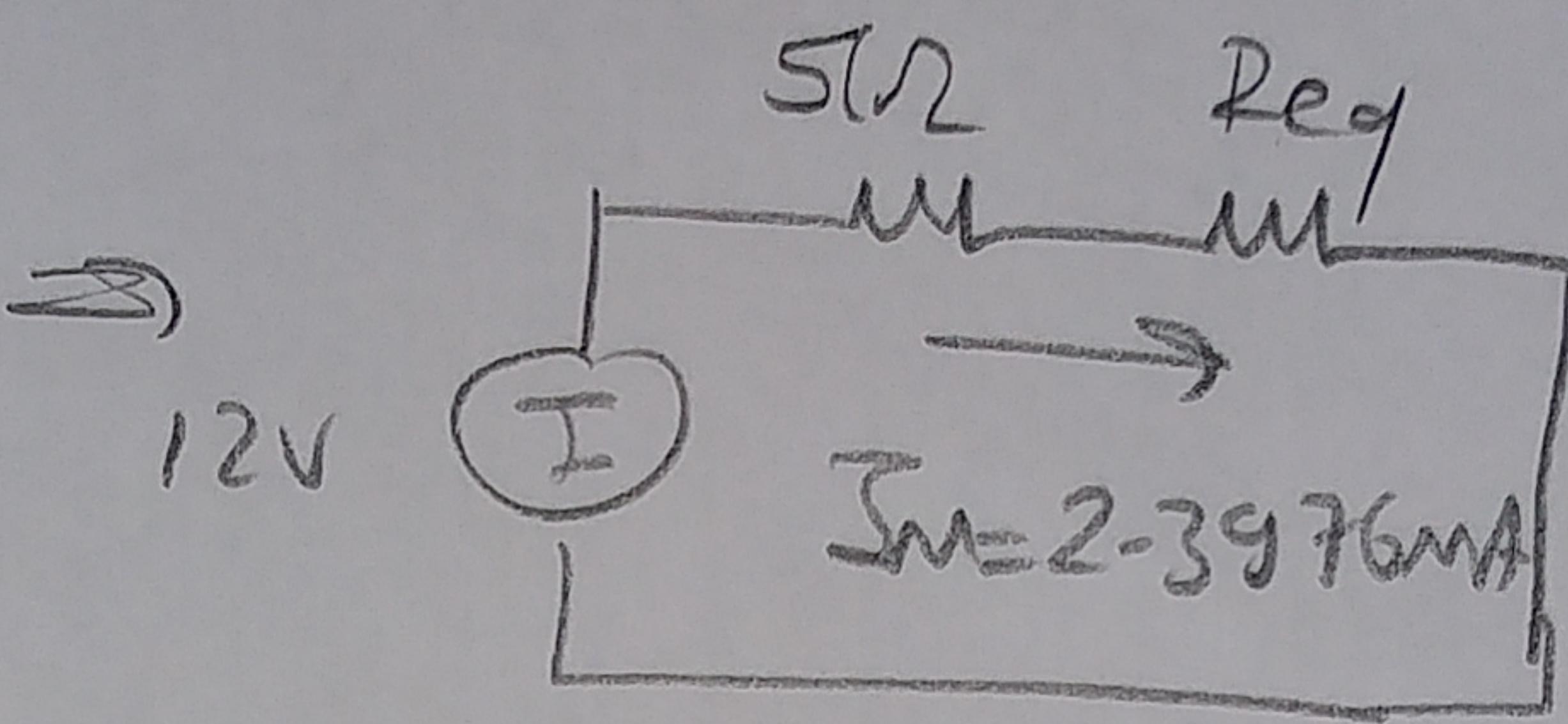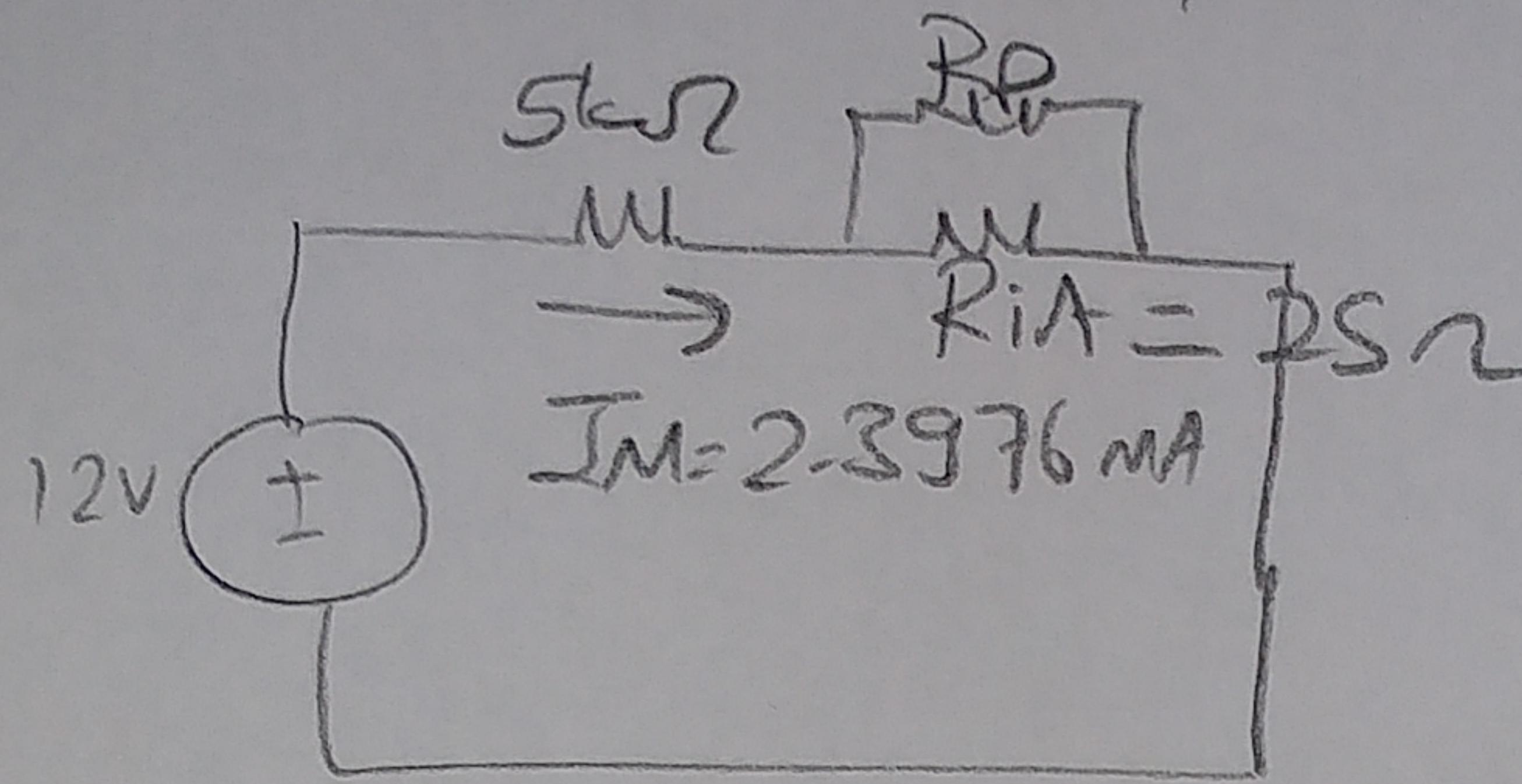
$$I_m = 2.4 - (10^{-3})(2.4) = 203976 \text{ mA}$$



$$I_m = \frac{12V}{5\Omega + R_{eq}} = 2.3976 \text{ mA} \Rightarrow 12V = (5\Omega)(2.3976 \text{ mA}) + R_{eq} \quad (2.3976 \text{ mA})$$


$$R_{eq} = \frac{12V - 11.988V}{2.3976 \text{ mA}} = 5 \times 10^{-3} \Omega = 5\Omega$$

$$R_p \parallel R_{IA} = 5\Omega$$

$$\frac{R_p \times 2\Omega}{R_p + 2\Omega} = 5\Omega$$

$$2R_p = 5R_p + 12.5 \quad 20R_p = 12.5 \quad \underline{\underline{R_p = 6.25\Omega}}$$

3-a)

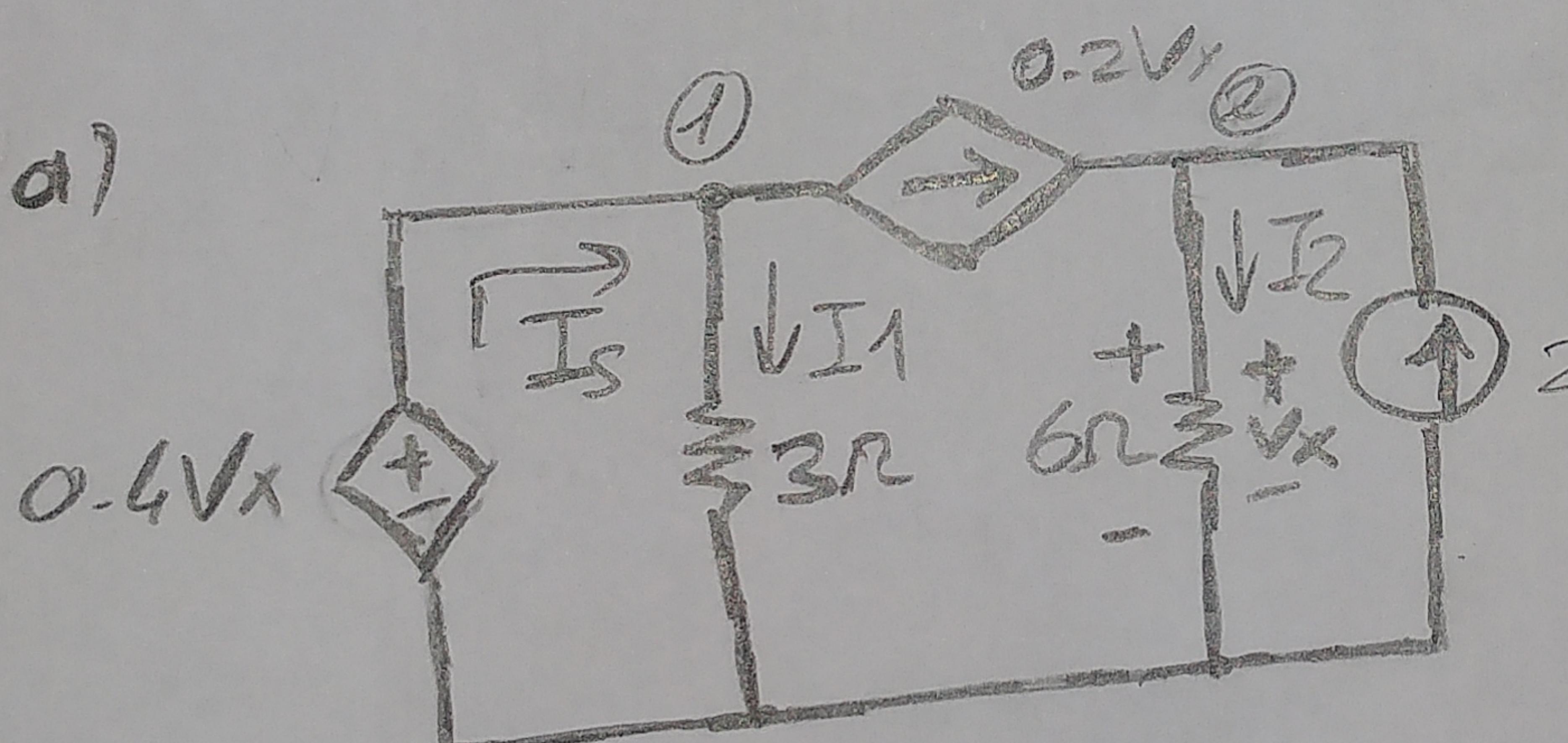

K.C.L at Node ① :

$$-I_s + I_1 + 0.2Vx = 0$$

K.C.L at Node ② :

$$-0.2Vx + I_2 - 2 = 0$$

$$V_x = 6I_2 \quad \text{Substituting into } ② \text{ node equation.}$$

$$-1.2I_2 + I_2 - 2 = 0 \Rightarrow -0.2I_2 = 2 \quad I_2 = \underline{\underline{-10A}}$$

$$V_x = 6(-10A) = \underline{\underline{-60V}}$$

$$\text{K.V.L for leftmost loop: } 0.4V_x = 3I_1 \quad I_1 = \frac{0.4V_x}{3} = \frac{0.4(-60)}{3} = \underline{\underline{-8A}}$$

$$I_s = I_1 + 0.2V_x \Rightarrow \text{From Node equation } ① \quad I_s = -8A + 0.2(-60) = \underline{\underline{-20A}}$$

$$I_s = -8A + (0.2)(-60V) = -8A - 12A = \underline{\underline{-20A}}$$

- 3 -

$$P_{(0.4Vx)} = -(0.4Vx)(I_s) = -(0.4 \times (-60V)) \times (-2A) = -\underline{480W}$$

To find the power associated with the 0.2Vx source, we have to first find the voltage on it.

$$K.V.I \text{ (Mesh 1 & Mesh 2 together)} \quad -0.6Vx + V' + Vx = 0$$

$$V' = -0.6Vx = (-0.6)(-60V) = \underline{36V}$$

$$P_{(0.2Vx)} = (36V)(0.2[\frac{A}{V}]) \times (-60V) = -\underline{432W}$$

$$P_{(2A)} = -(-60V)(2A) = 120W$$


$$P_{\text{TOTAL SOURCES}} = -480W - 432W + 120W = -\underline{792W}$$

$$6) \quad P_{3\Omega} = (I_1)^2(3\Omega) = (-8A)^2 \times (3) = \underline{192W}$$

$$P_{6\Omega} = (I_2)^2(6\Omega) = (-10A)^2 6 = \underline{600W}$$

$$P_{\text{TOTAL}} = 600W + 192W = \underline{792W}$$

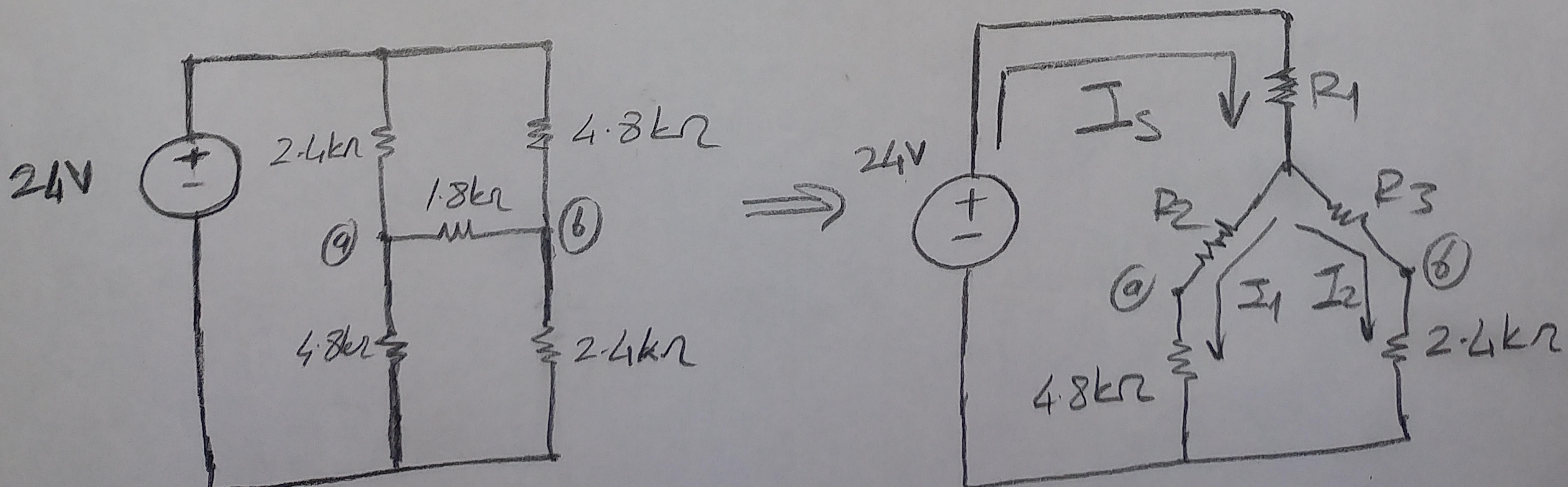4- we apply  $\Delta$  to  $\gamma$  transformation to upper delta.




$$R_1 = \frac{(2.4k\Omega)(4.8k\Omega)}{(2.4k\Omega + 4.8k\Omega + 1.8k\Omega)} = \frac{11.52k\Omega}{9k\Omega} = \underline{1.28k\Omega}$$

$$R_2 = \frac{(2.4k\Omega)(1.8k\Omega)}{9k\Omega} = \underline{0.48k\Omega}$$

$$R_3 = \frac{(4.8k\Omega)(1.8k\Omega)}{9k\Omega} = \underline{0.96k\Omega}$$

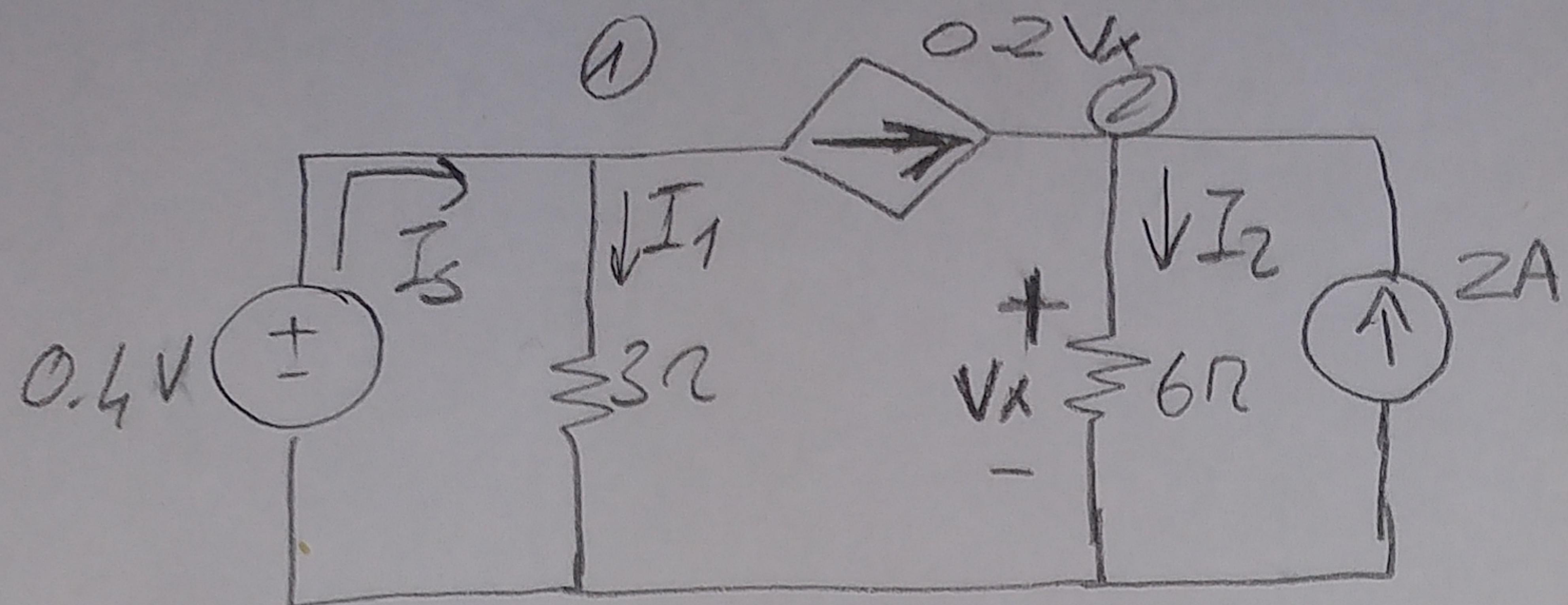3 - a) Alternative solution with independent source = 0.4 V.



$$\text{Node } ① \quad I_S = \frac{V_1}{3} + 0.2V_x \quad V_x = 6I_2$$

$$\text{Node } ② \quad -0.2V_x + \frac{V_1}{6} - 2 = 0 \quad | \times 6$$

$$-1.2V_x + V_x - 12 = 0$$

$$-0.2V_x = 12 \quad V_x = \underline{-60V} \quad (3)$$

$$I_2 = \frac{V_x}{6} = \frac{-60V}{6} = \underline{-10A} \quad (3)$$

$$K.V.L \quad 0.4 = 3I_1 = V_1 \quad I_1 = \frac{0.4}{3} = \underline{0.133A} \quad (3)$$

$$I_S = \frac{0.4}{3} + 0.2(-60) = 0.133 - 12 = \underline{-11.867A}$$

$$6) \quad P(0.4V) = -(0.4V)(I_S) = -(0.4V)(-11.867A) = \underline{4.746W} \quad (3)$$

$V'$ : voltage on the 0.2Vx current source:

$$K.V.L: (\text{Mesh 1} \& \text{Mesh 2 combined}) \quad -0.4V + V' + V_x = 0$$

$$V' = 0.4 - V_x = 0.4 + 60 = \underline{60.4V} \quad (3)$$

$$P(0.2Vx) = (60.4V)(0.2 \left[ \frac{A}{V} \right] \times (-60V)) = \underline{-726.8W} \quad (3)$$

$$P(2A) = -(-60V)(2A) = \underline{120W} \quad (3) \quad P_{\text{TOTAL}} = \underline{600.53W}$$

$$6) \quad P_{3\Omega} = (0.133A)^2(3\Omega) = \underline{0.053W}$$

$$P_{6\Omega} = (-10A)^2(6\Omega) = \underline{600W}$$

$$P_{\text{TOTAL}} = \underline{600.053W}$$

-4-

$$R_{eq} = 1.28k\Omega + (4.8k\Omega + 0.48k\Omega) \parallel (2.4k\Omega + 0.96k\Omega)$$

$$R_{eq} = 1.28k\Omega + 5.28k\Omega \parallel 3.36k\Omega = 1.28k\Omega + 2.053k\Omega = \underline{\underline{3.333k\Omega}}$$

$$I_S = \frac{24V}{3.333k\Omega} = \underline{\underline{7.2mA}}$$

$$I_1 = \frac{3.36k\Omega}{3.36k\Omega + 5.28k\Omega} \times 7.2mA = \underline{\underline{2.8mA}}$$

$$I_2 = \frac{5.28k\Omega}{3.36k\Omega + 5.28k\Omega} \times 7.2mA = \underline{\underline{4.6mA}}$$

$$V_{ab} = V_a - V_b = (4.8k\Omega)I_1 - (2.4k\Omega)I_2$$

$$V_{ab} = (4.8k\Omega)(2.8mA) - (2.4k\Omega)(4.6mA)$$

$$V_{ab} = \underline{\underline{2.88V}}$$

$$I_{(1.8k\Omega)} = \frac{2.88V}{1.8k\Omega} = \underline{\underline{1.6mA}}$$

$$P = I_{(1.8k\Omega)}^2 \cdot (1.8k\Omega) = (1.6mA)^2 (1.8k\Omega) = \underline{\underline{4.608mW}}$$

$$E = P \cdot \Delta t = (4.608mW) \left[ \frac{10^3}{mW} \right] \times 3600s = \underline{\underline{16.589J}}$$