
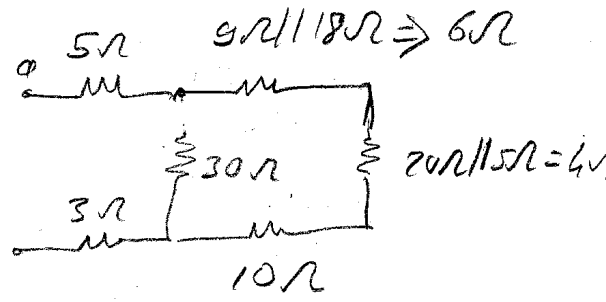


-1-  
Solutions Problem set 3



3.8 a)

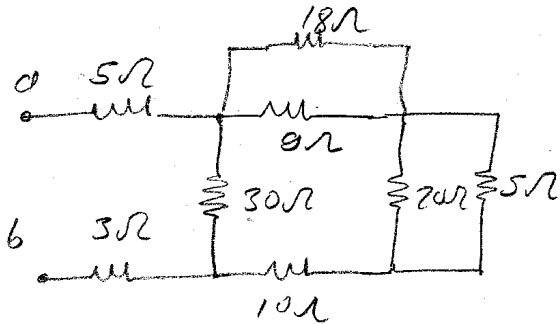


$$9\Omega // 18\Omega = \frac{9 \times 18}{9 + 18} = 6\Omega$$

$$20\Omega // 5\Omega = \frac{20 \times 5}{20 + 5} = 4\Omega$$
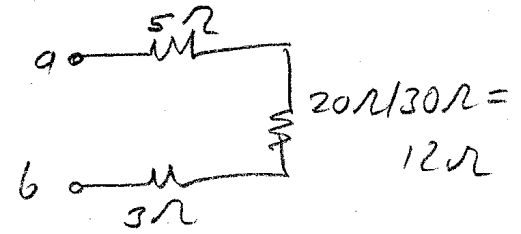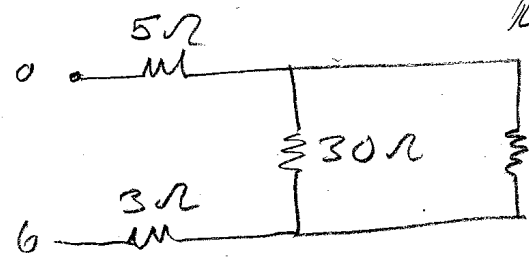
$$R_{series} = 6\Omega + 4\Omega + 10\Omega = 20\Omega$$











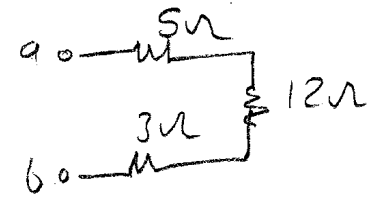
$$20\Omega // 30\Omega = \frac{20 \times 30}{20 + 30} = 12\Omega$$




$$R_{equivalent\ final} = 5\Omega + 3\Omega + 12\Omega = \underline{\underline{20\Omega}}$$

b)

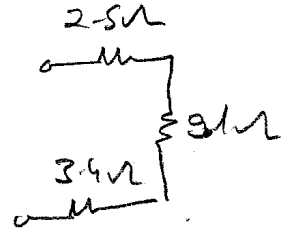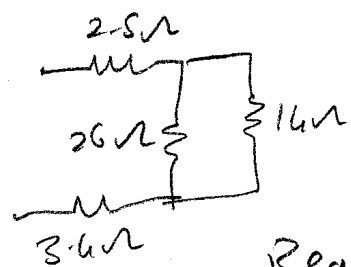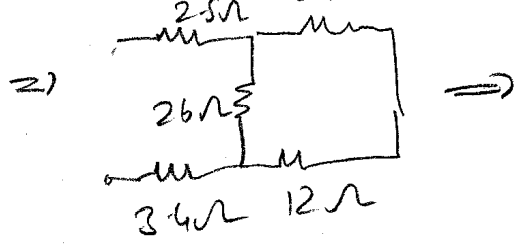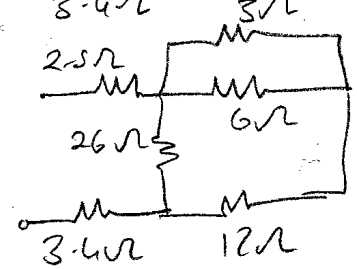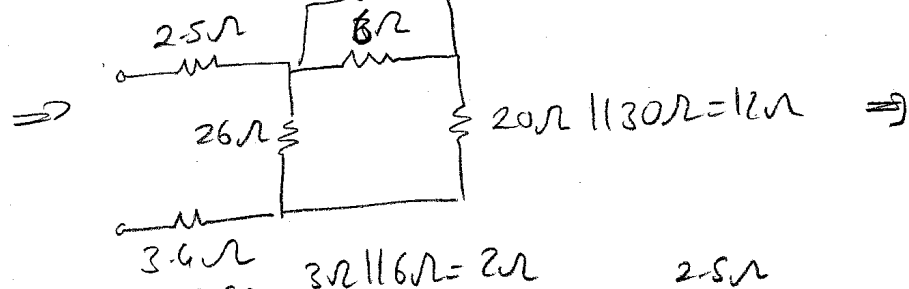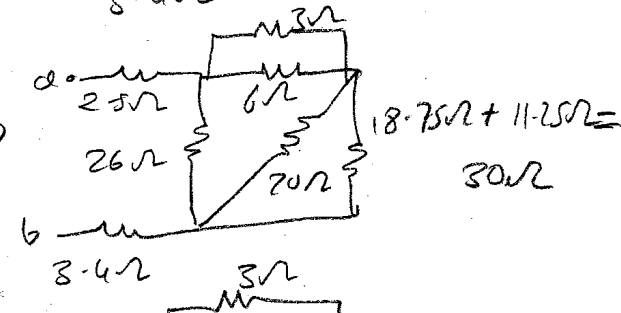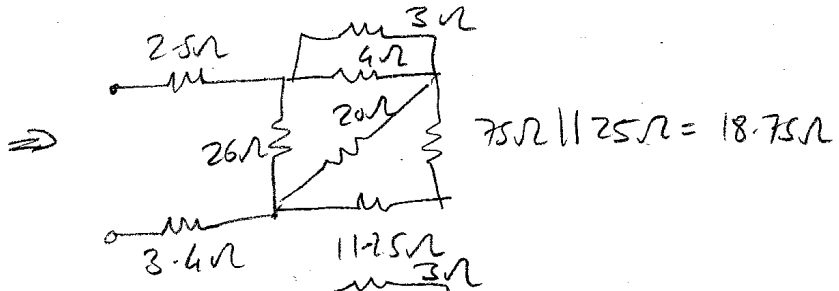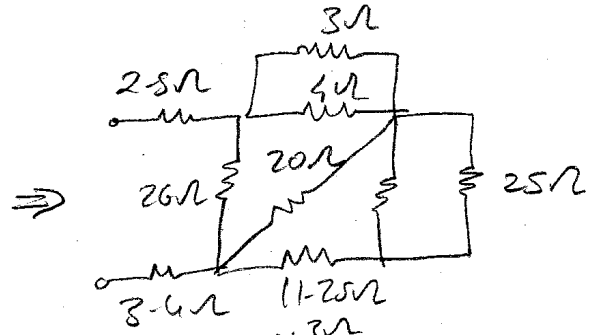
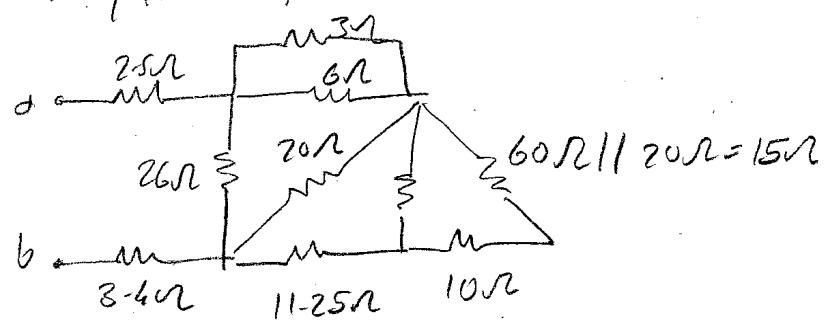


$$R_{eq} = 2.5\Omega + 9.1\Omega + 3.4\Omega = \underline{\underline{15\Omega}}$$



3.8 c)

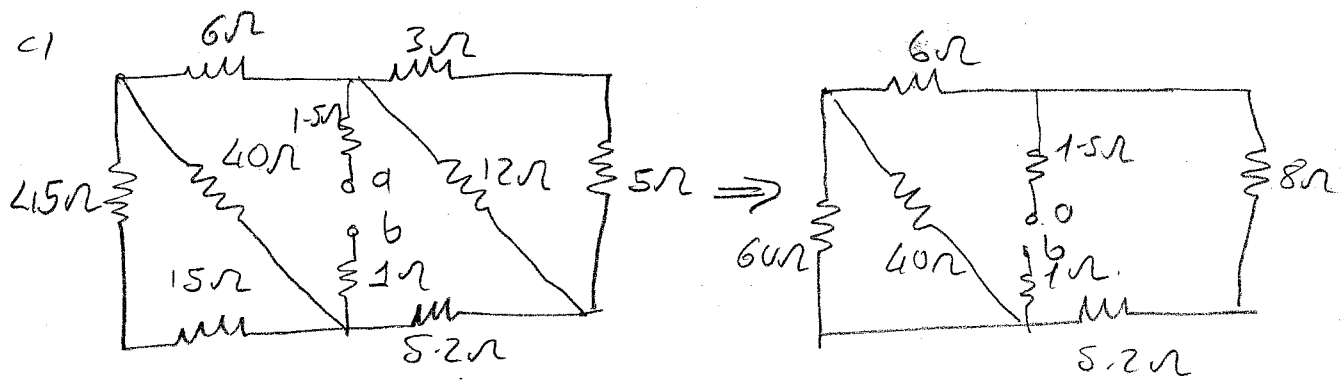

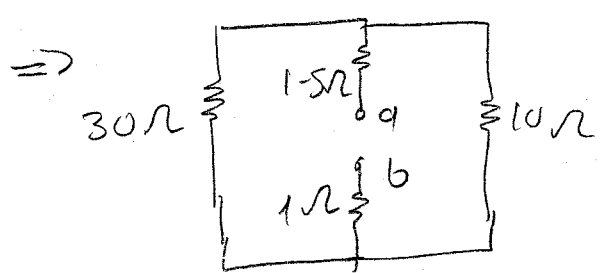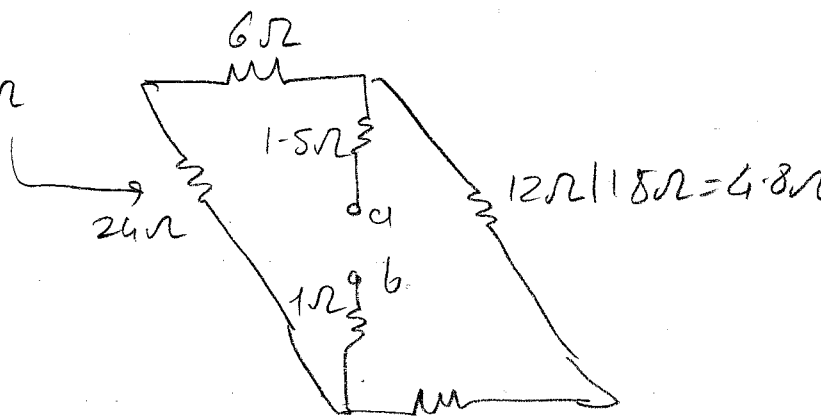$\Rightarrow 60\Omega \parallel 40\Omega = 24\Omega$




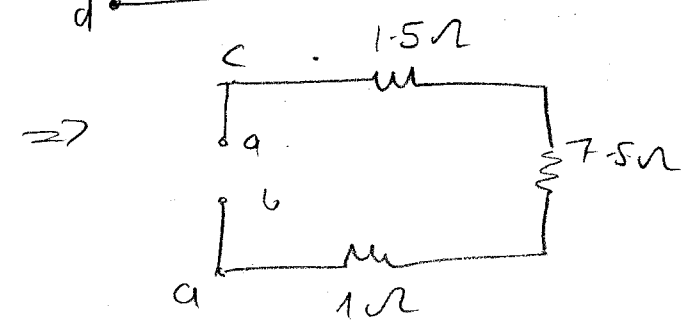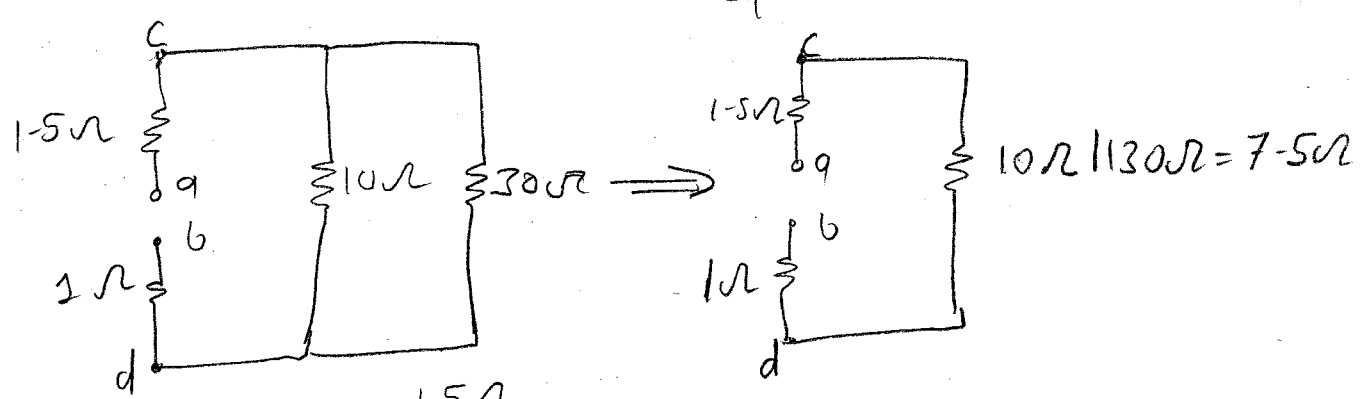$V_{30\Omega} = V_{10\Omega} = V_{cd}$ , thus the  $30\Omega$  and  $10\Omega$  resistors are in parallel, we can draw an equivalent circuit.




$R_{eq} = 1.5\Omega + 7.5\Omega + 1\Omega = \underline{\underline{10\Omega}}$

3.10

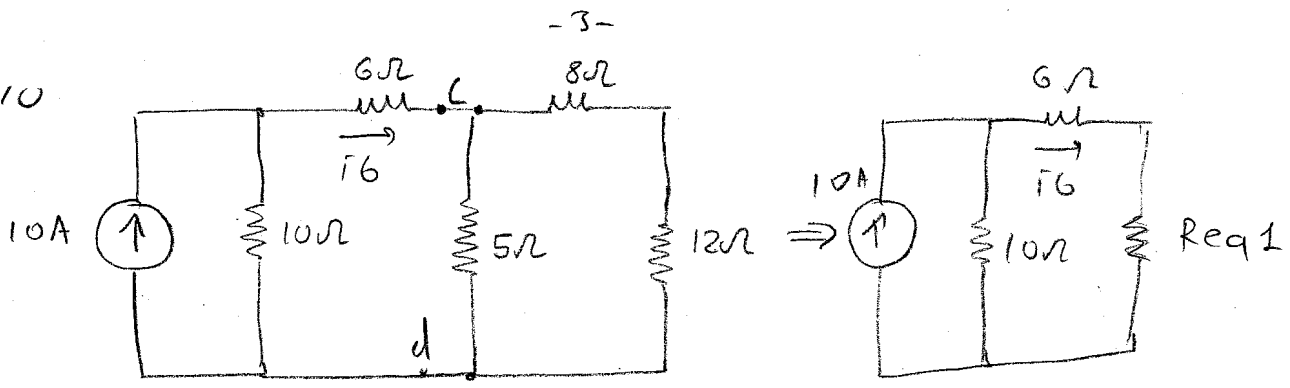
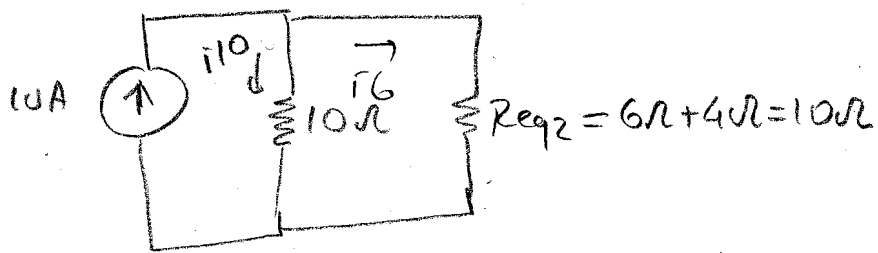
$$R_{eq1} = 5\Omega \parallel (8\Omega + 12\Omega) = 5\Omega \parallel 20\Omega = \frac{5 \times 20}{5 + 20} = 4\Omega$$




Using the Current Division Equation:

$$i_g = \frac{v}{R_g} = \frac{R_{eq1}}{R_g} i$$

Applying to this case  $i = 10A$

$$R_{eq} = 10\Omega \parallel 10\Omega = 5\Omega$$

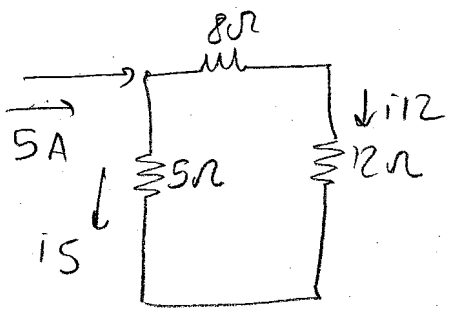$i_g = i_d = \frac{5\Omega}{10\Omega} \times 10A = \underline{5A}$   $\Rightarrow$  Now that we have determined  $i_g$ , we go back to the circuit and compute the current left of terminals c and d, and apply current division equation again.




$$R_{eq} = 5\Omega \parallel (8\Omega + 12\Omega) = 5\Omega \parallel 20\Omega = \frac{5 \times 20}{5 + 20} = 4\Omega$$

$$i_5 = \frac{4\Omega}{5\Omega} \times 5A = \underline{4A}$$

$$P_{5\Omega} = (4A)^2 (5\Omega) = \underline{80W}$$

3.11

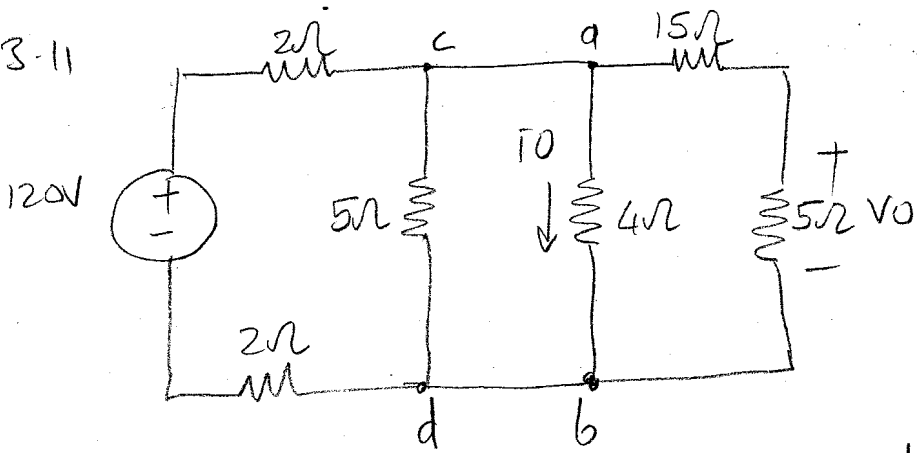


a) In order to determine  $i_0$ , we need to determine  $v_{ab}$  first, once we determine  $v_{ab}$ , we can also determine  $v_o$ .

But  $v_{ab} = v_{cd}$ , as the  $5\Omega$  resistor is connected in parallel to the  $4\Omega$  resistor and the series combination of  $15\Omega$  and  $5\Omega$  resistors. If we can compute the equivalent resistance of the circuit to the right of the terminals  $cd$ , we can use voltage division to determine  $V_{ab}$ .

$$R_{eq \text{ right of } cd} = 5\Omega \parallel 4\Omega \parallel (15\Omega + 5\Omega)$$

$$\frac{1}{R_{eqcd}} = \frac{1}{5} + \frac{1}{4} + \frac{1}{20} = \frac{20 + 25 + 5}{100} = \frac{1}{2}$$

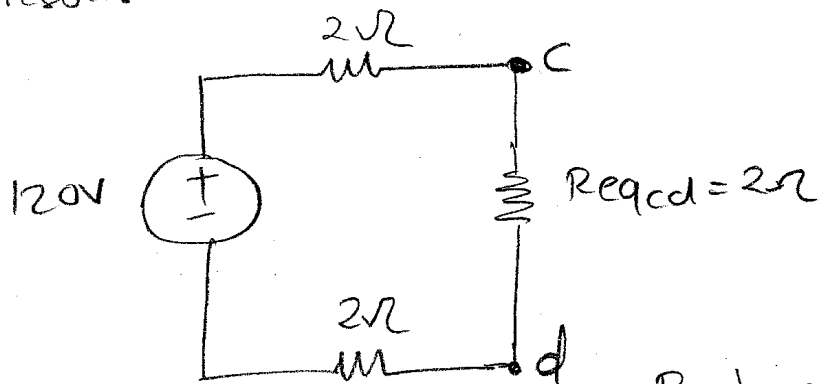$R_{eqcd} = 2\Omega$ , thus, the following equivalent circuit represents the circuit.



$$V_{cd} = \frac{2\Omega}{2\Omega + 2\Omega + 2\Omega} \times 120V$$

$$V_{cd} = \frac{1}{3} \times 120V = 40V$$

But  $v_{ab} = v_{cd} = 40V$ , thus

$I_0 = \frac{v_{ab}}{4\Omega} = \frac{40V}{4\Omega} = \underline{10A}$ . Now to determine the voltage  $v_0$ , we apply voltage division again. The  $40V$ , between terminals  $ab$  is equal to the sum of the voltages across the  $15\Omega$  and  $5\Omega$  resistors. The voltage is simply distributed proportional to the resistors.


$$V_0 = \frac{5\Omega}{5\Omega + 15\Omega} \times 40V = \frac{1}{4} \times 40V = \underline{10V}$$

b)  $I_{15} = \frac{V_{cd}}{15\Omega + 5\Omega} = \frac{40V}{20\Omega} = 2A$  ;  $P_{15\Omega} = (2A)^2 \cdot (15) = \underline{60W}$

c)  $R_{TOTAL} = 2\Omega + 2\Omega + 2\Omega = 6\Omega$  ;  $I = \frac{120V}{6\Omega} = 20A$

$P_{source} = (120V)(-20A) = -2400W$ . The source is losing  $24,00W$ . The power delivered by the source to the circuit is  $2400W = 2.4kW$ .

3.13

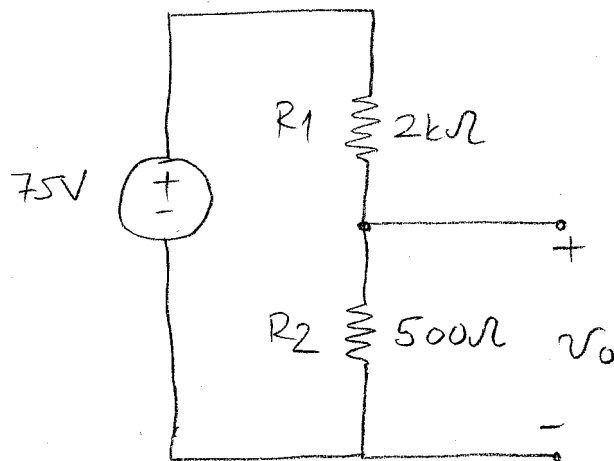

$$a) V_{NOLOAD} = \frac{0.5k\Omega}{2k\Omega + 0.5k\Omega} \cdot 75V = \underline{\underline{15V}}$$

$$b) I = \frac{75V}{2k\Omega + 0.5k\Omega} = 30mA$$

$$P_{2k\Omega} = (30 \times 10^{-3}A)^2 (2 \times 10^3\Omega) = 900 \times 10^{-6} \times 2 \times 10^3 = 1800 \times 10^{-3}W = \underline{\underline{1800mW}}$$

$$P_{500\Omega} = (30 \times 10^{-3}A)^2 (500\Omega) = 900 \times 10^{-6} \times 5 \times 10^2 = 4500 \times 10^{-4}W = \underline{\underline{450mW}}$$

c) We are given the power specification for the resistors, the power dissipated can not exceed 1W.

$$P_{max} = V \cdot i \leq 1W$$

Now if the no-load voltage has to be same as in part a) that is 15V, the voltages  $V_{R1}$  and  $V_{R2}$  across the resistors are fixed.

$$V_{R2} = V_{NOLOAD} = \underline{\underline{15V}}$$

$$V_{R1} = 75V - 15V = 60V$$

$$I_{R1} \leq \frac{1W}{V_{R1}} = \frac{1W}{60V} = 16.67 \times 10^{-3}A = 16.67mA$$


$$I_{R2} \leq \frac{1W}{V_{R2}} = \frac{1W}{15V} = 66.67 \times 10^{-3} = 66.67mA$$

So we get 2 Bounds for the currents, we select the lower one 16.67mA. Thus the current  $I = I_{R1} = I_{R2}$  can be at most 16.67mA.

$$R1 \geq \frac{V_{R1}}{I_{R1}} = \frac{60V}{16.67mA} = \underline{\underline{3.6k\Omega}}$$

$$R2 = \frac{V_{R2}}{I_{R2}} = \frac{15V}{16.67mA} = \underline{\underline{0.9k\Omega}}$$

3.15

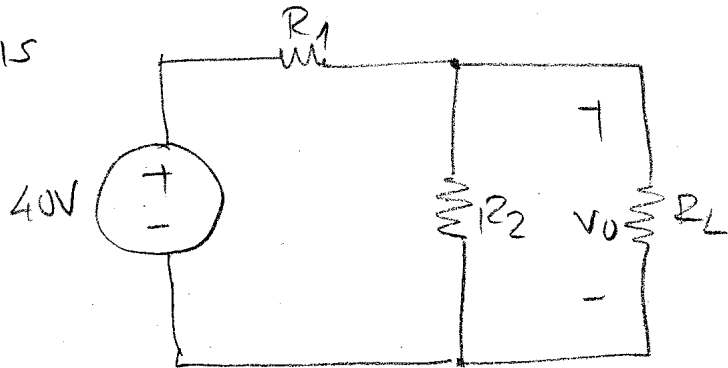


(10)  $V_{NOLOAD} = 8V$

$R_{Lmin} = 3.6k\Omega$


$V_{min} = 7.5V$

From the constraint on no-load voltage
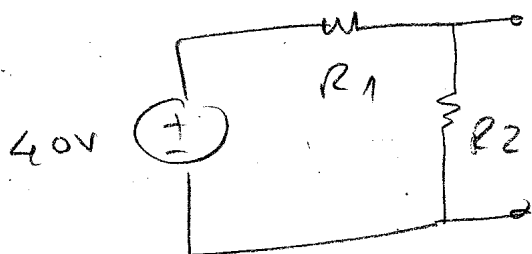
$$\frac{R_2}{R_1 + R_2} (40) = 8 \quad \text{so} \quad R_1 = 4R_2$$



$\Rightarrow$  NO LOAD CIRCUIT

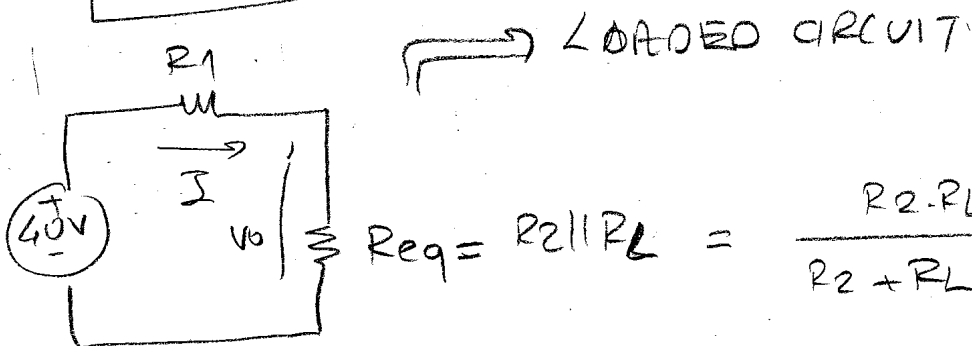

$\hookrightarrow$  LOADED CIRCUIT

$$R_{eq} = R_2 \parallel R_L = \frac{R_2 \cdot R_L}{R_2 + R_L}$$

$$\Rightarrow \frac{v_0}{40} = \frac{R_{eq}}{R_1 + R_{eq}} \Rightarrow v_0 = 40 \times \frac{R_{eq}}{R_1 + R_{eq}}$$


$$v_0 = 40 \times \frac{\frac{R_2 R_L}{R_2 + R_L}}{R_1 + \frac{R_2 R_L}{R_2 + R_L}} = \frac{40 R_2 R_L}{R_1 (R_2 + R_L) + R_2 R_L} = \frac{40 R_2}{\frac{R_1 R_2}{R_L} + R_1 + R_2}$$

Now From No load condition  $R_1 = 4R_2$ , also  
When  $R_L$  is minimum,  $v_0$  is also at its minimum 7.5V.

$$7.5V = \frac{R_2 3600}{4R_2 (R_2 + 3600) + R_2 3600} = \frac{60 \times 3600 R_2}{4R_2^2 + 18000 R_2}$$

$$\frac{1440000}{4R_2 + 18000} = 7.5 \quad R = 300\Omega \text{ and } R_1 = 6R_2 = 1200\Omega$$

3.17 o)

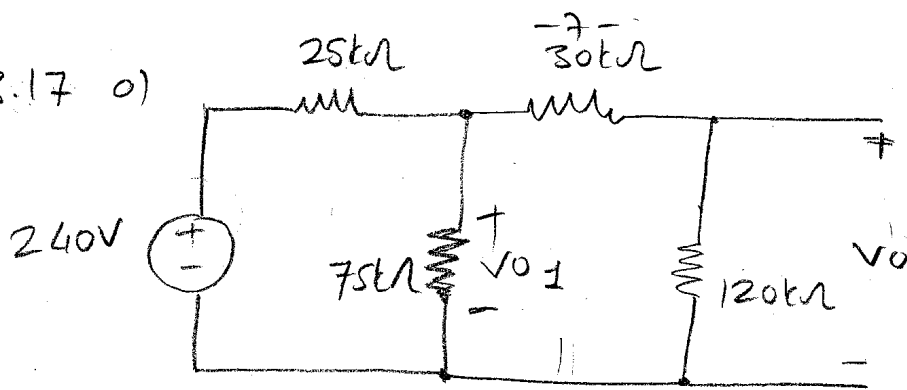


$$120k\Omega + 30k\Omega = 150k\Omega$$

$$75k\Omega \parallel 150k\Omega = \frac{75 \times 150}{75 + 150} = \frac{75 \times 150}{225} = 50k\Omega$$

$$V_{01} = \frac{240 \times 50,000}{25,000 + 50,000} = 160V$$

$$V_0 = \frac{120,000}{150,000} (V_{01}) = \frac{4}{5} \times 160V = 128V$$

b)

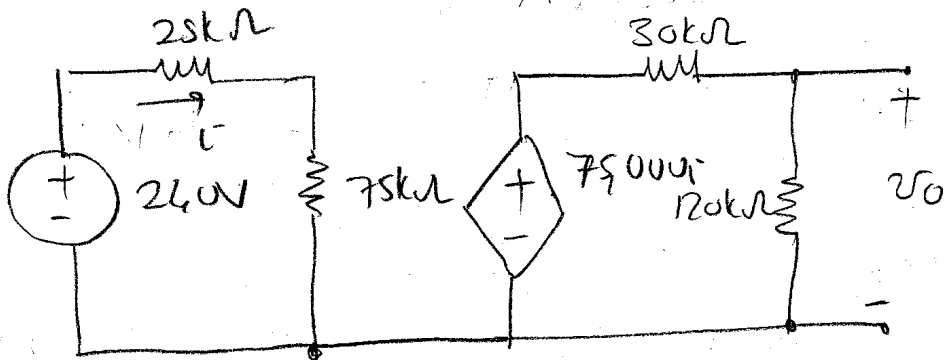

$$i = \frac{240V}{25k\Omega + 75k\Omega} = \frac{240V}{100k\Omega} = 2.4mA$$

$$75,000i = 75 \times 2.4 = 180V$$

$$V_0 = 180V \times \frac{120k\Omega}{120k\Omega + 30k\Omega} = 144V$$

c) It removes loading effect of second voltage divider on the first voltage divider. The open circuit voltage of the first divider is

$$V_{01} = \frac{75,000}{100,000} (240) = 180V$$

Note this is the input voltage to the second voltage divider when the current controlled voltage source is used.

3.18

$$I_s = \frac{P_s}{V_s} = \frac{36W}{24V} = 1.5A$$

$$(R_1 + R_2)(1.5A) = 12V \quad R_1 + R_2 = 8\Omega$$

$$R_2(1.5A) = 0V$$

$$R_2 = 4\Omega \Rightarrow R_1 = 8\Omega - 4\Omega = 4\Omega$$

$$R_3 I_3 = 12V$$

$$R_3 \cdot (1.5A) = 12V \quad R_3 = 8\Omega$$

3.21

$$I_g = I_1 + I_2 + I_3 + I_4 = 8mA \Rightarrow K-C-L$$

$$I_1 = \frac{V_g}{R_1} = \frac{4}{R_1} \Rightarrow I_2 = \frac{I_1}{2} = \frac{2}{R_1} \quad I_3 = \frac{I_2}{10} = \frac{1}{5R_1}$$

$$\text{since } I_3 = I_4 \quad I_4 = \frac{1}{5R_1}$$

Substituting the values of  $I_1, I_2, I_3$  and  $I_4$  into the K-C-L equation

$$\frac{4}{R_1} + \frac{2}{R_1} + \frac{1}{5R_1} + \frac{1}{5R_1} = 8mA$$

$$40R_1 = 20 + 10 + 1 + 1 = 32 \Rightarrow R_1 = \frac{32}{40} = 0.8k\Omega$$


$$I_2 = \frac{V_g}{R_2} \Rightarrow R_2 = \frac{V_g}{I_2} \Rightarrow I_1 = \frac{4V}{0.8k\Omega} = 5mA \quad I_2 = \frac{I_1}{2} = 2.5mA$$

$$\text{Thus } R_2 = \frac{4V}{2.5mA} = 1.6k\Omega \quad R_3 = \frac{V_g}{I_3} \quad \text{but } I_3 = \frac{I_2}{10} = 0.25mA$$

$$R_3 = \frac{V_g}{I_3} = \frac{4V}{0.25mA} = 16k\Omega \quad R_4 = \frac{V_g}{I_4} \quad \text{but } I_4 = I_3$$

$$\text{Thus } R_4 = R_3 = 16k\Omega$$

3.24

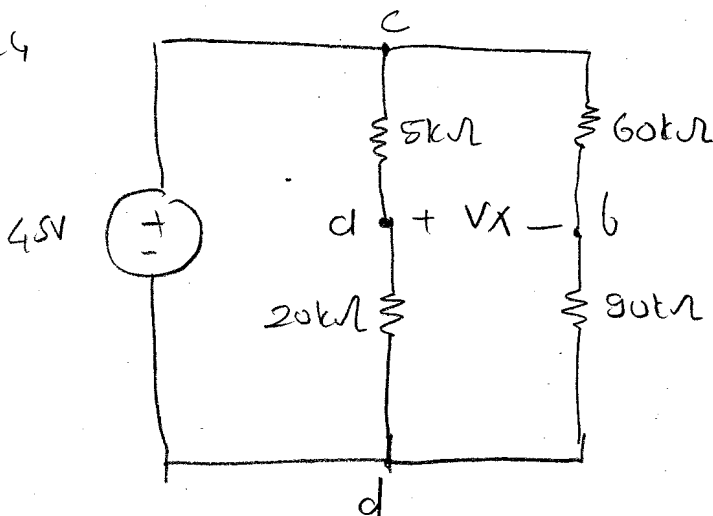

$$a) V_x = V_{ad} - V_{bd} \quad \text{Using Voltage Division:} \\ V_{ad} = \frac{20k\Omega}{20k\Omega + 5k\Omega} \times 45V = 36V$$

$$V_{bd} = \frac{90k\Omega}{90k\Omega + 60k\Omega} \times 45V = 27V$$

$$V_x = V_{ad} - V_{bd} = 36V - 27V = 9V$$

b)


$$V_{ad} = \frac{20}{25} \times V_s = 0.8V_s$$

$$V_{bd} = \frac{90}{150} \times V_s = 0.6V_s$$


$$V_x = V_{ad} - V_{bd} = 0.2V_s$$



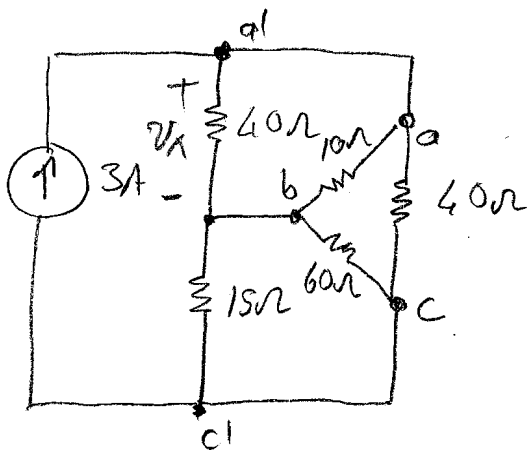
3-30 After connecting the device the circuit looks like this:



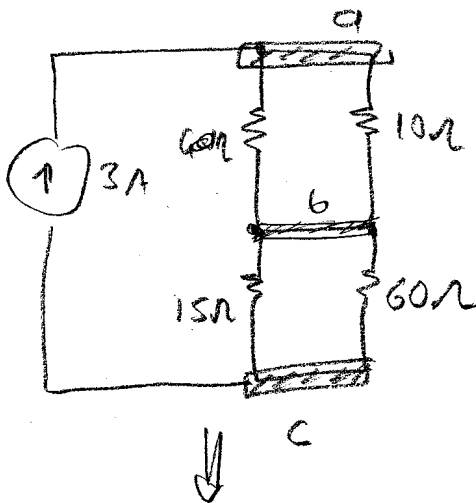Note as  $a$  and  $a'$  and  $c$  and  $c'$  are at the same potential the  $10\Omega$  resistor is connected in parallel with the  $40\Omega$  resistor and the  $60\Omega$  resistor is connected in parallel with the  $15\Omega$  resistor. We can combine  $a$  and  $a'$  into a single node. Similarly we can combine  $c$  and  $c'$  into a single node.



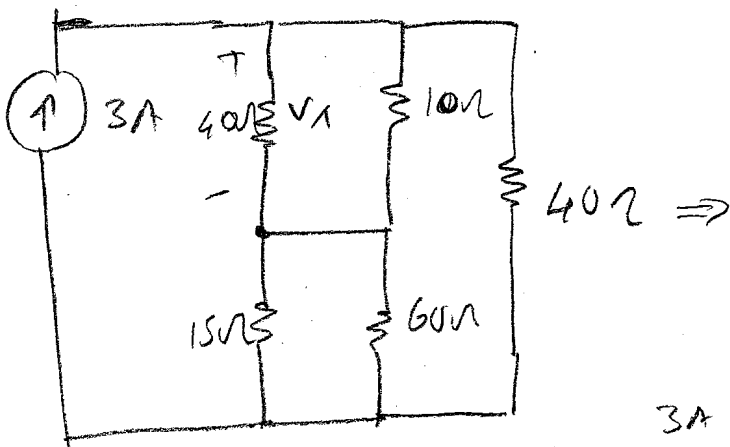Now we note that at the original circuit the  $40\Omega$  resistor on the right was connected between nodes  $a$  and  $c$ . So we connect it the same way between nodes  $a$  and  $c$  and obtain the final circuit.



$$40\Omega \parallel 10\Omega = 8\Omega$$


$$15\Omega \parallel 60\Omega = 12\Omega$$

We can now apply current division to find  $i_1$  and  $i_2$ .

$$R_{eq} = 20\Omega \parallel 60\Omega = \frac{800}{60} = \frac{40}{3}\Omega$$

$$i_2 = \frac{40}{3} \cdot \frac{1}{20} \times 3A = 2A$$
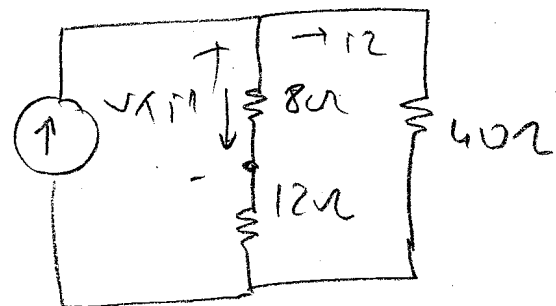
$$i_1 = \frac{40}{3} \cdot \frac{1}{40} \times 3A = 1A$$





$$v_x = 3A \times 16V$$

$$v_y = 20 \times 1 = 40V$$

$$v_{60} = v_y - v_x = 24V$$

$$P_{devce} = \frac{24^2}{60} + \frac{16^2}{10} + \frac{60^2}{40} = \underline{\underline{75.2W}}$$

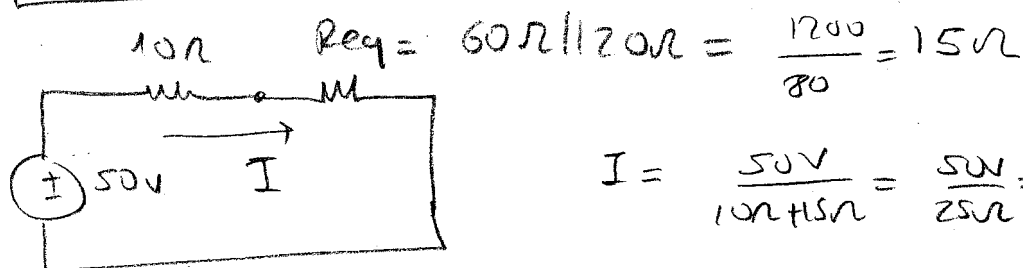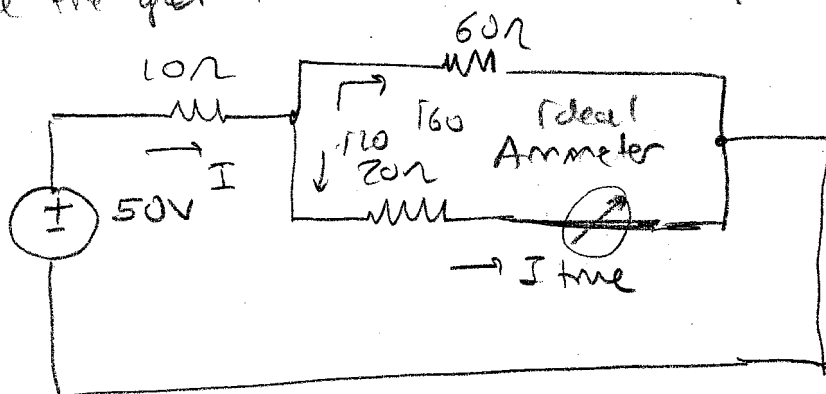3-32 We have to determine both the true value of the current and the measured value of the current. Let's call them  $I_{true}$  and  $I_{measured}$ . The true value of the current  $I_{true}$  can be found by removing the ammeter or equivalently by replacing it with an ideal ammeter with a resistance that is a short circuit. We then get the true or ideal equivalent circuit:



$$I = \frac{50V}{10\Omega + 15\Omega} = \frac{50V}{25\Omega} = 2A$$


Now we will apply current division to determine the currents  $I_{60}$  and  $I_{20}$  on the  $60\Omega$  and  $20\Omega$  resistors.

$$I_{20} = \frac{60\Omega}{60\Omega + 20\Omega} \times 2A = \frac{3}{4} \times 2A = 1.5A$$

$$I_{60} = \frac{20\Omega}{60\Omega + 20\Omega} \times 2A = \frac{1}{4} \times 2A = 0.5A$$

$$\text{Thus } I_{true} = I_{20} = 1.5A$$

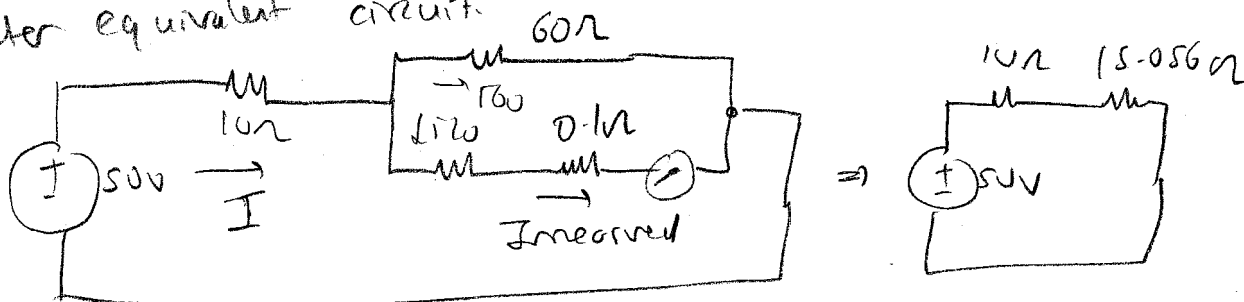Let's draw the equivalent circuit using the non-ideal ammeter equivalent circuit.



$$R_{eq} = 60\Omega \parallel 20.1\Omega = 15.056\Omega$$

$$I = \frac{50V}{10\Omega + 15.056\Omega} = 1.9955A$$

Using current division  $I_{60}$  and  $I_{70}$  become


$$I_{20} = 0.75 \times 1 - 99.55 = 1.495$$

$$I_{60} = 0.75 \times 1 - 99.55 = 0.4988$$

$$I_{\text{measured}} = 1.49664$$

$$\% \text{ error} = \left( \frac{1.495}{1.5} - 1 \right) \times 100 = -0.3488\%$$


3-33

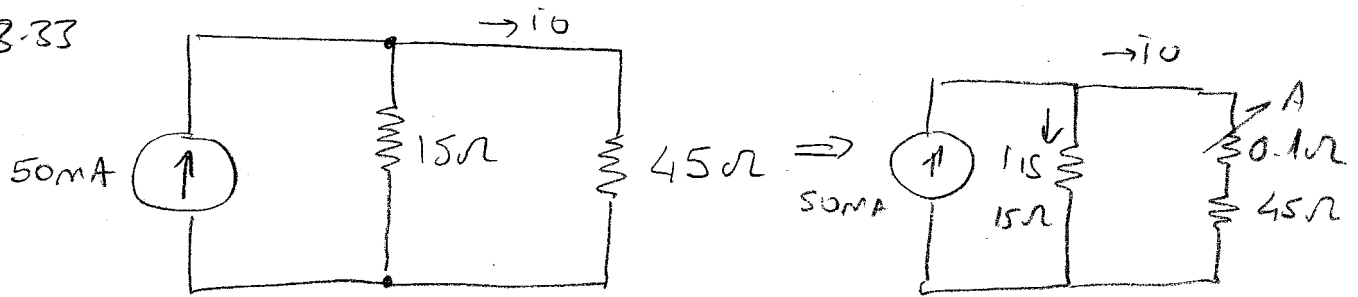



$$I_o = \frac{15\Omega}{15\Omega + 45\Omega + 0.1\Omega} \times 50\text{mA} = 12.479\text{mA}$$

$$\% \text{ error} = \left[ \frac{12.48}{12.5} - 1 \right] 100 = -0.1664\%$$

3-47

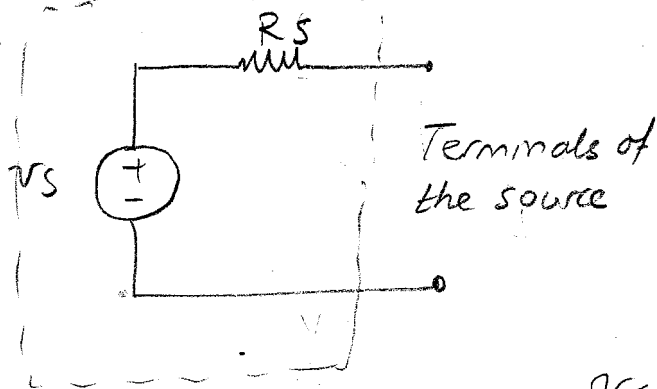

(1)

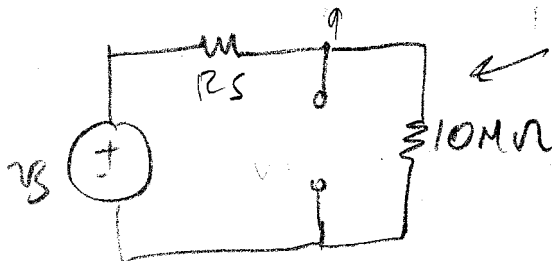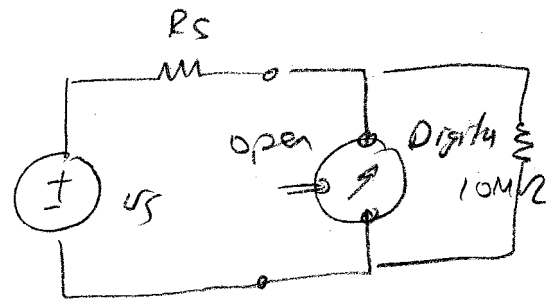

$$1) V_s \times \frac{10\text{M}\Omega}{10\text{M}\Omega + R_s} = 50\text{mV}$$

$$2) V_s \times \frac{6\text{M}\Omega}{6\text{M}\Omega + R_s} = 48.75\text{mV}$$

From Eq (1)  $10 + R_s = 0.2 V_s$ , substituting into Eq (2)

$$\text{yields } 48.75 = \frac{6 V_s}{0.2 V_s - 6} \text{ or } V_s = 52\text{mV}$$

$$\text{61 From Eq (1) } 50 = \frac{520}{10 + R_s} \text{ or } 50 R_s = 20 \text{ so } R_s = 400\text{k}\Omega$$

-58 (a) Convert the upper delta to a wye.

$$R_1 = \frac{(50)(50)}{200} = 12.5\Omega$$

$$R_2 = \frac{(50)(100)}{200} = 25\Omega$$

$$R_3 = \frac{(50)(100)}{200} = 25\Omega$$


Convert the lower delta to a wye.

$$R_4 = \frac{(60)(80)}{200} = 24\Omega$$

$$R_5 = \frac{(60)(60)}{200} = 18\Omega$$

$$R_6 = \frac{(60)(80)}{200} = 24\Omega$$

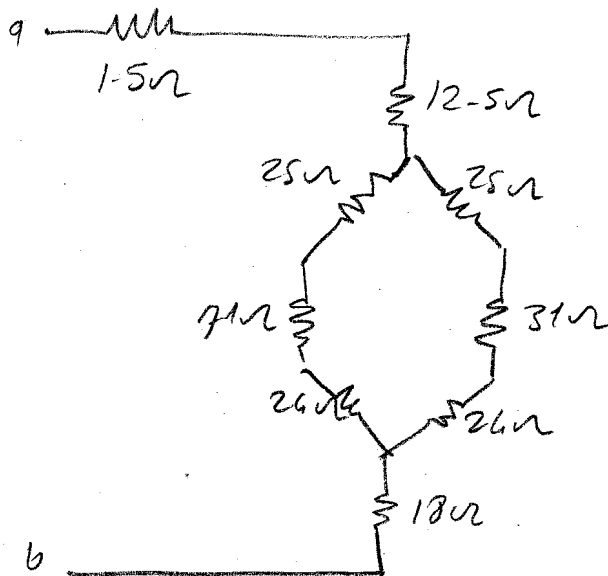Now redraw the circuit using the wye equivalents.



$$R_{ab} = 1.5 + 12.5 +$$

$$(25 + 71 + 24) \parallel (25 + 31 + 24) + 18$$

$$= 1.5 + 12.5 + (120 \parallel 85) + 18$$

$$= 1.5 + 12.5 + 48 + 18 = 80\Omega$$


$$(v) \quad V_{ab} = 400V$$

$$I_g = \frac{400}{80} = 5A$$

$$I_o = \frac{120}{120 + 80} (5) = 3A$$


$$P_{31\Omega} = (31)(3)^2 = 279W$$

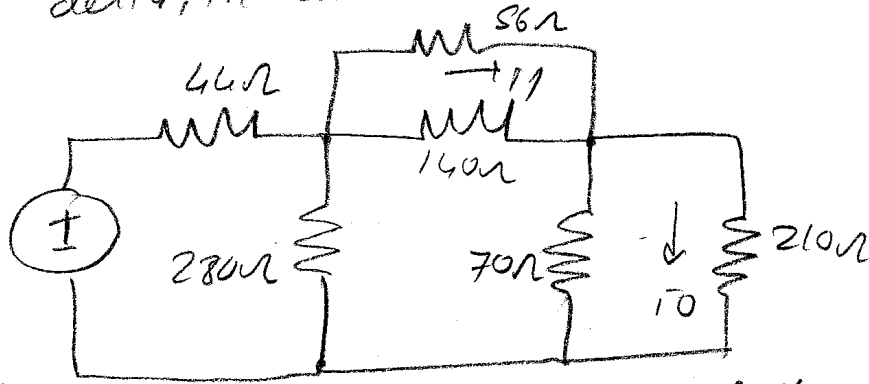3-59 After the  $20\Omega - 80\Omega - 40\Omega$  wye is replaced by its equivalent delta, the circuit reduces to



This circuit can be replaced to the following circuit:
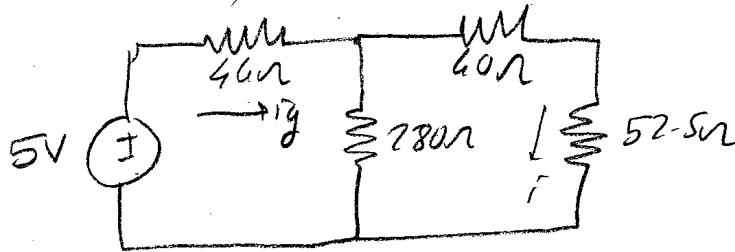
$$56\Omega \parallel 140\Omega = 40\Omega \quad 70\Omega \parallel 210\Omega = 52.5\Omega$$



$$R_{eq} = 44 + 280 \parallel 52.5 = 113.53\Omega$$

$$i_g = 5 / 113.53 = 44.06 \text{ mA}$$

$$i = (280 / 372.5) (44) = 33.11 \text{ mA}$$


$$V_{52.5\Omega} = (52.5) (33.11 \text{ mA}) = 1.74 \text{ V}$$

$$i_o = 1.74 / 210 = 8.28 \text{ mA}$$

$$(6) \quad V_{40\Omega} = (40) (33.11 \text{ mA}) = 1.32 \text{ V}$$

$$i_1 = 1.32 / 56 = 23.65 \text{ mA}$$

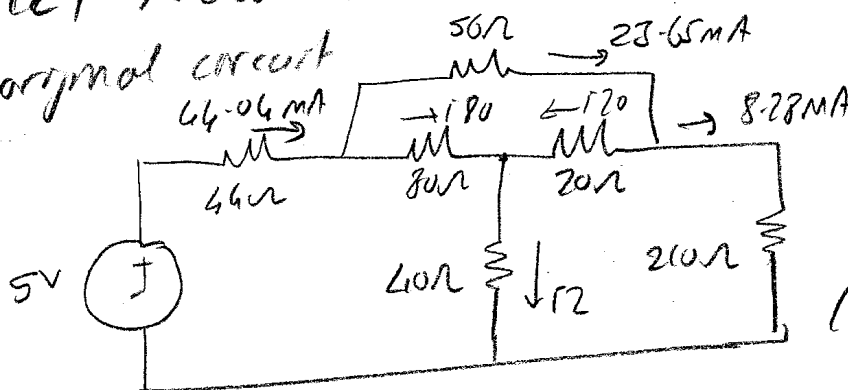(c) Now that  $i_o$  and  $i_1$  are known, we return to the original circuit



$$i_{80\Omega} = 44.06 \text{ mA} - 23.65 \text{ mA} = 20.39 \text{ mA}$$

$$i_{20\Omega} = 23.65 \text{ mA} - 8.28 \text{ mA} = 15.37 \text{ mA}$$

$$i_2 = i_{80\Omega} + i_{20\Omega} = 35.76 \text{ mA}$$

(d)  $P_{delivered} =$

$$(5) (44.06 \text{ mA}) = \underline{\underline{220.2 \text{ mW}}}$$