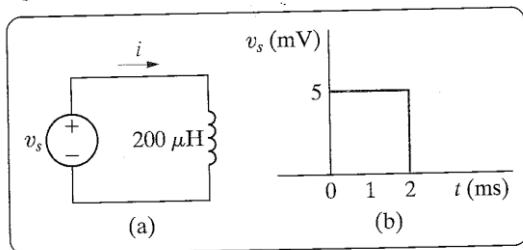


- 6.2** The voltage at the terminals of the $200\ \mu\text{H}$ inductor in Fig. P6.2(a) is shown in Fig. P6.2(b). The inductor current i is known to be zero for $t \leq 0$.



- Derive the expressions for i for $t \geq 0$.
- Sketch i versus t for $0 \leq t \leq \infty$.

Figure P6.2



- 6.4** The current in a $50\ \mu\text{H}$ inductor is known to be



$$i_L = 18te^{-10t}\ \text{A} \quad \text{for } t \geq 0.$$


- Find the voltage across the inductor for $t > 0$. (Assume the passive sign convention.)
- Find the power (in microwatts) at the terminals of the inductor when $t = 200$ ms.
- Is the inductor absorbing or delivering power at 200 ms?
- Find the energy (in microjoules) stored in the inductor at 200 ms.
- Find the maximum energy (in microjoules) stored in the inductor and the time (in microseconds) when it occurs.

- 6.7** a) Find the inductor current in the circuit in Fig. P6.7 if $v = 30 \sin 500t\ \text{V}$, $L = 15\ \text{mH}$, and $i(0) = -4\ \text{A}$.




- Sketch v , i , p , and w versus t . In making these sketches, use the format used in Fig. 6.8. Plot over one complete cycle of the voltage waveform.
- Describe the subintervals in the time interval between 0 and 4π ms when power is being absorbed by the inductor. Repeat for the subintervals when power is being delivered by the inductor.

Figure P6.7

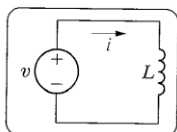

- 6.11** Initially there was no energy stored in the 5 H inductor in the circuit in Fig. P6.11 when it was placed across the terminals of the voltmeter. At $t = 0$ the inductor was switched instantaneously to position b where it remained for 1.6 s before returning instantaneously to position a. The d'Arsonval voltmeter has a full-scale reading of 20 V and a sensitivity of $1000 \Omega/\text{V}$. What will the reading of the voltmeter be at the instant the switch returns to position a if the inertia of the d'Arsonval movement is negligible?

Figure P6.11

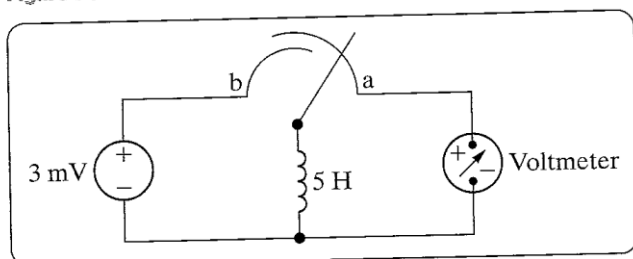

- 6.12** Evaluate the integral

$$\int_0^{\infty} p \, dt$$

for Example 6.2. Comment on the significance of the result.

- 6.14** A $20 \mu\text{F}$ capacitor is subjected to a voltage pulse having a duration of 1 s. The pulse is described by the following equations:


$$v_c(t) = \begin{cases} 30t^2 \text{ V}, & 0 \leq t \leq 0.5 \text{ s}; \\ 30(t - 1)^2 \text{ V}, & 0.5 \text{ s} \leq t \leq 1.0 \text{ s}; \\ 0 & \text{elsewhere.} \end{cases}$$

Sketch the current pulse that exists in the capacitor during the 1 s interval.

6.15 The rectangular-shaped current pulse shown in Fig. P6.15 is applied to a $5\ \mu\text{F}$ capacitor. The initial voltage on the capacitor is a 12 V drop in the reference direction of the current. Assume the passive sign convention. Derive the expression for the capacitor voltage for the time intervals in (a)–(e).

- $0 \leq t \leq 5\ \mu\text{s}$;
- $5\ \mu\text{s} \leq t \leq 20\ \mu\text{s}$;
- $20\ \mu\text{s} \leq t \leq 25\ \mu\text{s}$;
- $25\ \mu\text{s} \leq t \leq 35\ \mu\text{s}$;
- $35\ \mu\text{s} \leq t \leq \infty$;
- Sketch $v(t)$ over the interval $-50\ \mu\text{s} \leq t \leq 300\ \mu\text{s}$.

Figure P6.15

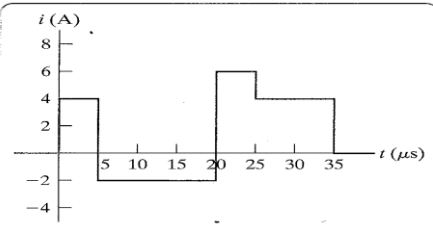

6.16 The voltage at the terminals of the capacitor in Fig. 6.10 is known to be

$$v = \begin{cases} -10\ \text{V}, & t \leq 0; \\ 40 - 1e^{-1000t}(50 \cos 500t + 20 \sin 500t)\ \text{V} & t \geq 0. \end{cases}$$

Assume $C = 0.8\ \mu\text{F}$.


- Find the current in the capacitor for $t < 0$.
- Find the current in the capacitor for $t > 0$.
- Is there an instantaneous change in the voltage across the capacitor at $t = 0$?
- Is there an instantaneous change in the current in the capacitor at $t = 0$?
- How much energy (in microjoules) is stored in the capacitor at $t = \infty$?

6.17 The current pulse shown in Fig. P6.17 is applied to a $0.25 \mu\text{F}$ capacitor. The initial voltage on the capacitor is zero.

P

- Find the charge on the capacitor at $t = 30 \mu\text{s}$.
- Find the voltage on the capacitor at $t = 50 \mu\text{s}$.
- How much energy is stored in the capacitor by the current pulse?

Figure P6.17

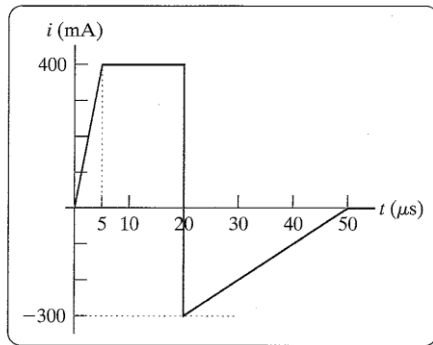

6.18 The initial voltage on the $0.5 \mu\text{F}$ capacitor shown in Fig. P6.18(a) is -20 V . The capacitor current has the waveform shown in Fig. P6.18(b).

P

- How much energy, in microjoules, is stored in the capacitor at $t = 500 \mu\text{s}$?
- Repeat (a) for $t = \infty$.

6.19 The voltage across the terminals of a $0.25 \mu\text{F}$ capacitor is

P


$$v = \begin{cases} 50 \text{ V}, & t \leq 0; \\ A_1 t e^{-4000t} + A_2 e^{-4000t} \text{ V}, & t \geq 0. \end{cases}$$

The initial current in the capacitor is 400 mA . Assume the passive sign convention.

- What is the initial energy stored in the capacitor?
- Evaluate the coefficients A_1 and A_2 .
- What is the expression for the capacitor current?

- 6.21** Assume that the initial energy stored in the inductors of Fig. P6.21 is zero. Find the equivalent inductance with respect to the terminals a,b.

Figure P6.21

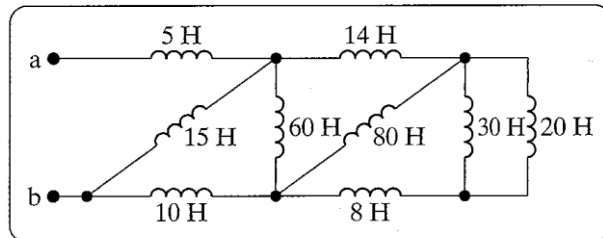


- 23** The three inductors in the circuit in Fig. P6.23 are connected across the terminals of a black box at $t = 0$. The resulting voltage for $t > 0$ is known to be

$$v_o = 160e^{-4t} \text{ V.}$$

If $i_1(0) = 1 \text{ A}$ and $i_2(0) = 3 \text{ A}$, find


- $i_o(0)$;
- $i_o(t), t \geq 0$;
- $i_1(t), t \geq 0$;
- $i_2(t), t \geq 0$;
- the initial energy stored in the three inductors;
- the total energy delivered to the black box; and
- the energy trapped in the ideal inductors.

Figure P6.23

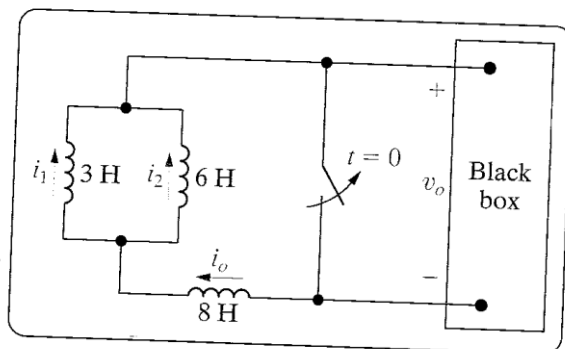

- 6.25** Find the equivalent capacitance with respect to the terminals a,b for the circuit shown in Fig. P6.25.


Figure P6.25

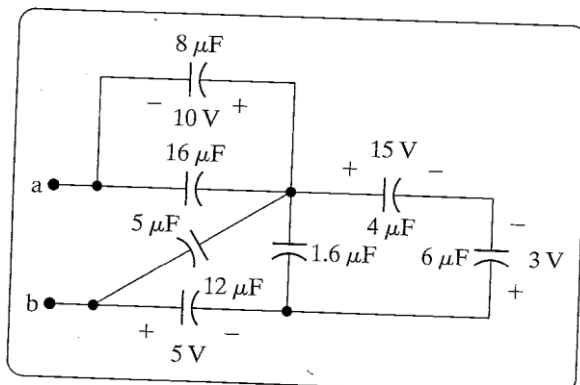

- 6.27** The two series-connected capacitors in Fig. P6.27 are connected to the terminals of a black box at $t = 0$. The resulting current $i(t)$ for $t > 0$ is known to be $20e^{-t} \mu\text{A}$.

- Replace the original capacitors with an equivalent capacitor and find $v_o(t)$ for $t \geq 0$.
- Find $v_1(t)$ for $t \geq 0$.
- Find $v_2(t)$ for $t \geq 0$.
- How much energy is delivered to the black box in the time interval $0 \leq t \leq \infty$?
- How much energy was initially stored in the series capacitors?
- How much energy is trapped in the ideal capacitors?
- Do the solutions for v_1 and v_2 agree with the answer obtained in (f)?

Figure P6.27

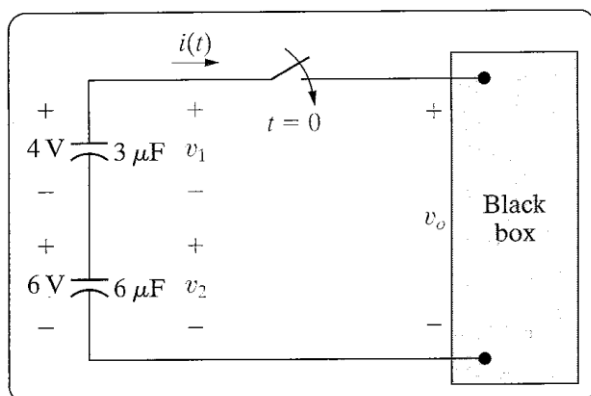


- 6.32** The current in the circuit in Fig. P6.32 is known to be

$$i_o = 5e^{-2000t}(2 \cos 4000t + \sin 4000t) \text{ A}$$

for $t \geq 0^+$. Find $v_1(0^+)$ and $v_2(0^+)$.

Figure P6.32

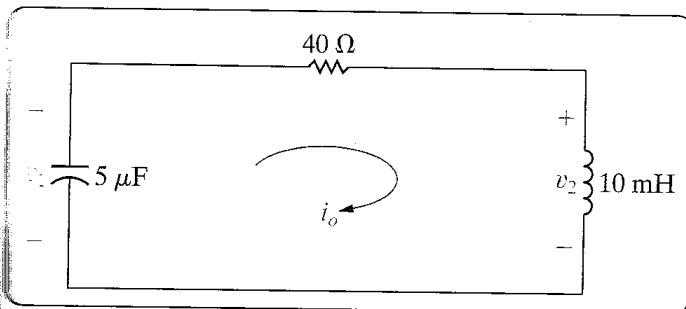

- 6.33** At $t = 0$, a series-connected capacitor and inductor are placed across the terminals of a black box, as shown in Fig. P6.33. For $t > 0$, it is known that

$$i_o = 1.5e^{-16,000t} - 0.5e^{-4000t} \text{ A.}$$

If $v_c(0) = -50 \text{ V}$ find v_o for $t \geq 0$.

Figure P6.33

