

First Order RC Circuits Lab#5

Pre-lab

1- For the circuit in Fig. 5.1:

a- Find the time constant τ .

b- Let $V_s(t)$ be a square wave with amplitude of (0V-5V), and a period of 20τ . Find $V(t)$ and sketch it.


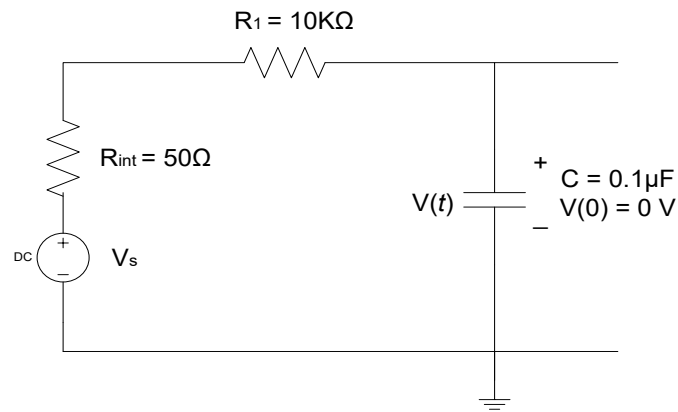


Fig. 5.1

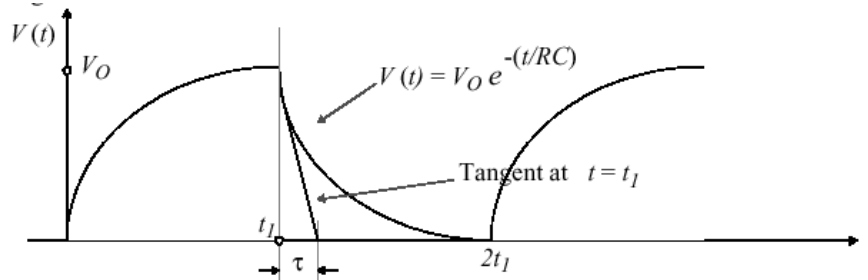2- The **tangent method** to find τ : Sometimes it is convenient to be able to find the time constant of a circuit by just looking at its response on an oscilloscope. The response may look something like this:




- Show that τ in the above diagram is equal to RC .

Instructional objective

Two types of first order circuits will be considered in this lab; RC circuits and RL circuits.

Procedure:

1- Build the circuit in Fig. 5.1.

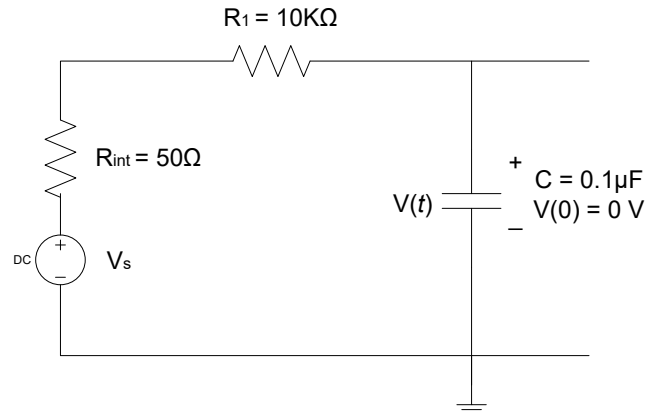

2- Let $V_s(t)$ be a square wave from (0-5V), with a period of 20τ . Note that such a square wave is an approximation of a *STEP* function. **Why?**

3- Sketch $V(t)$ and $V_s(t)$ on the same graph.

4- Find the time constant (τ) using the tangent method. Note that finding the time constant from the oscilloscope display is not accurate to the n^{th} degree, but you can get a very close and quick approximation. Be sure to expand the waveform as much as possible on your screen to get the most accurate measurement.