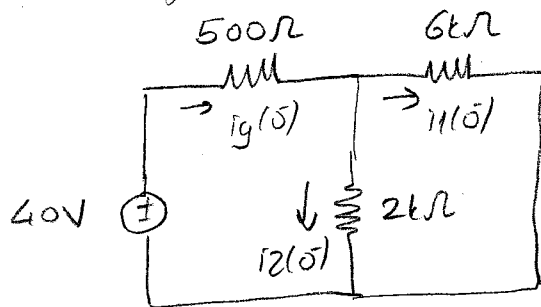


SOLUTIONS OF PROBLEM SET 7

1. (a) for $t < 0$, the equivalent circuit is




$$i_1(t) = \frac{40}{\frac{2 \times 6}{2+6} + 0.5} = \frac{40}{2} = 20 \text{ mA}$$

The branch currents can be found using current division.

$$i_1(t) = \frac{2}{8} \times 20 = 5 \text{ mA} \quad i_2(t) = \frac{6}{8} \times 20 = 15 \text{ mA}$$

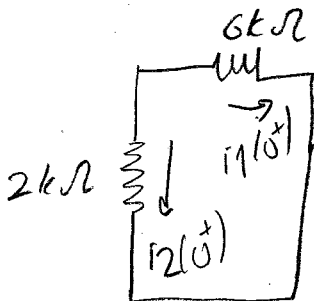(b) Due to the continuity condition of the current in an inductor $i_1(t) = i_1(t) = 5 \text{ mA}$

The equivalent circuit for $t \geq 0$, just at the instant the switch opens at $t = 0^+$.



$$i_1(t) = -i_2(t) \Rightarrow i_2(t) = -i_1(t) \\ i_2(t) = -5 \text{ mA}$$

$$(c) \quad \tau = \frac{L}{R} = \frac{0.4 \times 10^{-3} \text{ H}}{8 \times 10^3 \Omega} = 5 \times 10^{-5} \text{ s}; \quad \frac{1}{\tau} = 20,000$$

$$i_1(t) = i_1(t) e^{-t/\tau} = 5 e^{-20,000t} \text{ mA} \quad t \geq 0.$$


$$(d) \quad \text{when } t \geq 0^+ \quad i_2(t) = -i_1(t) \therefore i_2(t) = -5 e^{-20,000t} \text{ mA}, \quad t \geq 0^+.$$

(e) Once the switch opens the circuit changes and the current in the resistor changes suddenly from 15 mA to -5 mA. The current in a resistor can be discontinuous.

$$\therefore i_2(t) = 15 \text{ mA} \quad \text{and} \quad i_2(t) = -5 \text{ mA}$$

7-3 (a) $i_o(t=0^-) = 0$, since the switch is open for $t < 0$.

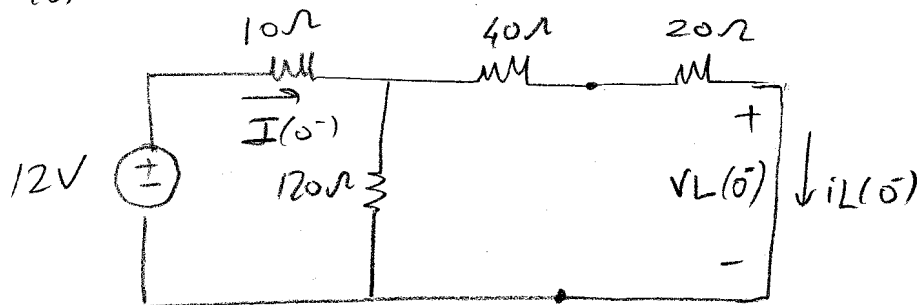(b) For $t = 0^-$ the equivalent circuit is




$$R_{eq} = 10 + 120 \parallel 60 = 10 + \frac{120 \times 60}{120 + 60} = 50 \Omega$$

$$I(0^-) = \frac{12}{50} = 0.24 \text{ A} = 240 \text{ mA}$$


$i_L(0^-)$ can be found using current division rule.

$$i_L(0^-) = I(0^-) \times \frac{120}{120 + 60} = (240 \text{ mA}) \times \frac{2}{3} = 160 \text{ mA}$$

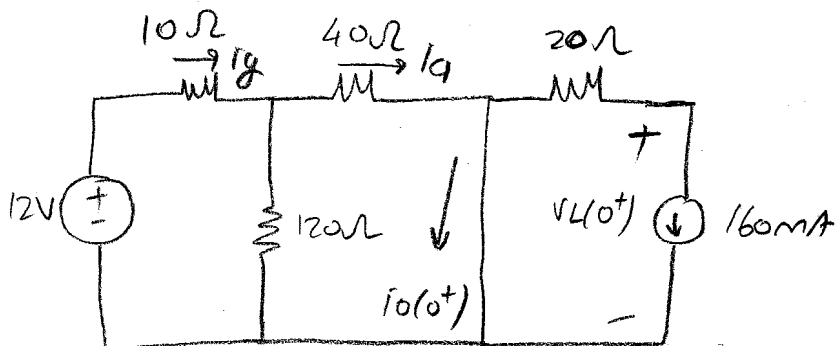(c) For $t = 0^+$, the equivalent circuit is



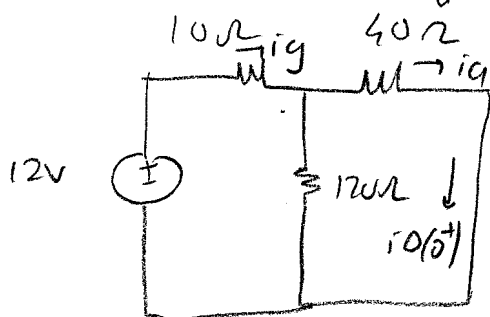⚡ We can ignore this part of the circuit as no current flows there due to the short circuit at the inductor branch.



$$R_{eq} = 40 \Omega \parallel 120 \Omega = 30 \Omega$$

$$\therefore i_g = \frac{12}{10 + 30} = 0.30 \text{ A} = 300 \text{ mA}$$

$$i_a = \left(\frac{120}{160} \right) \times 300 = 225 \text{ mA}$$

$$\therefore i_o(0^+) = 225 - 160 = 65 \text{ mA} \quad (\text{Kirchhoff's current law})$$

(d) $i_L(0^+) = i_L(0^-) = 160 \text{ mA}$

(e) $i_0(\infty) = i_a = 225 \text{ mA}$, because at $t \rightarrow \infty$ the inductor looks like a short circuit.

(f) $i_L(\infty) = 0$, since the switch short circuits the branch containing the 20Ω resistor and the 100 mH inductor.

(g) $\tau = \frac{L}{R} = \frac{100 \times 10^{-3}}{20} = 5 \text{ ms}; \quad \frac{1}{\tau} = 200$

$\therefore i_L = 0 + (160 - 0)e^{-200t} = 160e^{-200t} \text{ mA}, \quad t \geq 0$

(h) $v_L(0^-) = 0$ since for $t < 0$ the current in the inductor is constant

(i) Refer to the circuit at $t = 0^+$ and note:

$20(0.16) + v_L(0^+) = 0 \quad \therefore v_L(0^+) = -3.2 \text{ V}$

(j) $v_L(\infty) = 0$, since the current in the inductor is a constant at $t = \infty$.

(k) $v_L(t) = 0 + (-3.2 - 0)e^{-200t} = -3.2e^{-200t} \text{ V}, \quad t \geq 0$

(l) $i_0 = i_a - i_L = 225 - 160e^{-200t} \text{ mA}, \quad t \geq 0$

7-4 (a) $i(0^+) = 10 \quad v_0(0^+) = 400 \quad R = \frac{v(0^+)}{i(0^+)} = 40 \Omega$

b) $\tau = \frac{1}{5} = 0.2 \quad c) L = \tau R = (0.2 \times 40) = 8 \text{ H}$

d) $W = \frac{1}{2} Li^2(0^+) = \frac{1}{2} (8)(10)^2 = 400 \text{ J}$

e) $p(t) = v(t)i(t) = 4000e^{-10t}$

$$W = \int_0^{t'} 4000e^{-10t} dt = -\frac{1}{10} \times 4000 \times [e^{-10t}]_0^{t'}$$

$$= -400 \times [e^{-10t'} - 1] = 400 [1 - e^{-10t'}]$$

This expression gives the energy as a function of time at an arbitrary time t' . We want this to be equal to 80% of the initial energy, which is $W(0) = 400J$.


$$400 [1 - e^{-10t'}] = 320$$

$$1 - e^{-10t'} = 0.8$$

$$e^{-10t'} = 0.2$$


$$-10t' = \ln 0.2 \Rightarrow t' = -\frac{\ln 0.2}{10} = 0.1609s$$

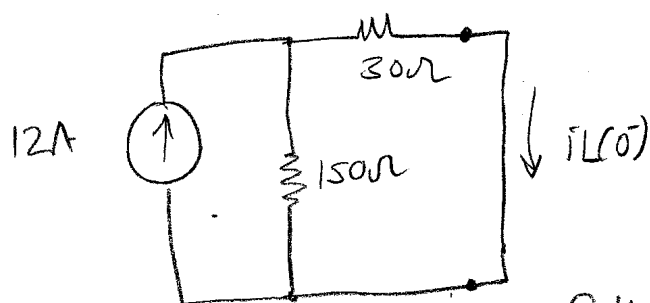7-8 (a) For $t < 0$, we obtain the following equivalent circuit as the inductor appears as a short circuit. Using Current Division:




$$i_L(0) = \frac{150}{180} (12) = 10A$$

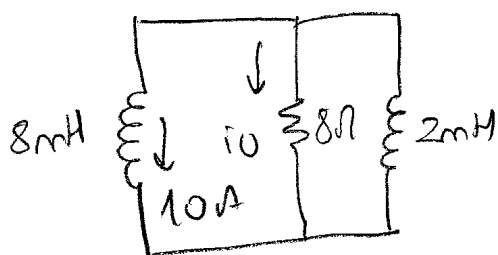For $t \geq 0$, we get the following equivalent circuit



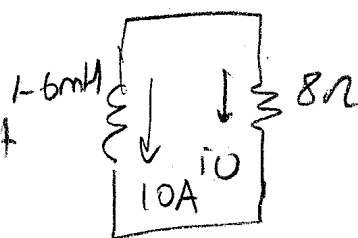which can be represented with the following circuit
Using $L_{eq} = \frac{L_1 \times L_2}{L_1 + L_2}$



$$\tau = \frac{L}{R}$$

$$\tau = \frac{1.6 \times 10^{-3}}{8} = 200 \times 10^{-6}$$

$$i(t) = 5000 - 10e^{-5000t} A \quad t \geq 0.$$

$$(b) W_{del} = \frac{1}{2} (1.6 \times 10^{-3}) (10)^2 = 80 \text{ mJ} \quad (W = \frac{1}{2} L_{eq} I (t_0^+)^2)$$


$$(c) 0.95 W_{del} = 76 \text{ mJ}$$

$$\therefore 76 \times 10^{-3} = \int_0^{t_0} (100 \times e^{-10,000t}) dt \quad \left(\begin{array}{l} p(t) = v(t)i(t) \\ v(t) = L di/dt \end{array} \right)$$

$$\therefore 76 \times 10^{-3} = -80 \times 10^{-3} e^{-10,000t} \Big|_0^{t_0} = 80 \times 10^{-3} (1 - e^{-10,000t_0})$$

$$\therefore e^{-10,000t_0} = 4 \times 10^{-3} \quad \text{so} \quad t_0 = 552.1 \text{ ns}$$


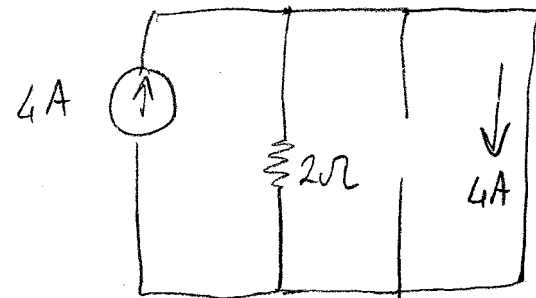
13 for $t < 0$ at
($t=0^-$) the equivalent
circuit is



$$i_L(0^-) = i_L(0^+) = 4A$$

we find the Thevenin resistance seen by the inductor


for $t > 0$

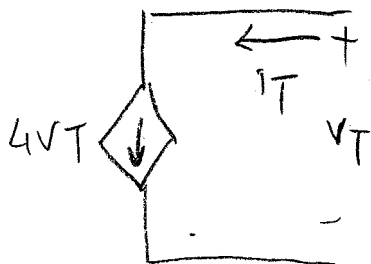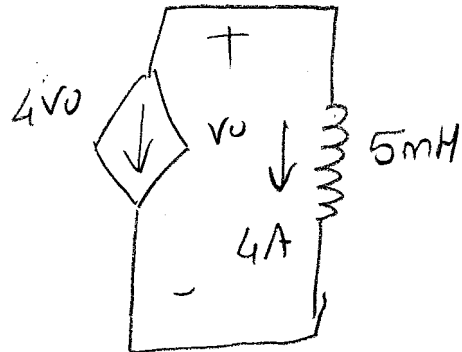

$$i_T = 4v_T; \quad \frac{v_T}{i_T} = R_{TH} = \frac{1}{4} = 0.25 \Omega$$

$$\tau = \frac{L}{R} = \frac{5 \times 10^{-3}}{0.25} = 20 \text{ ms}, \quad \frac{1}{\tau} = 50$$

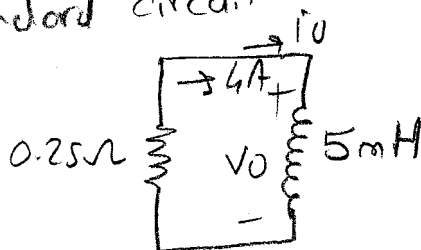We can now replace the above circuit with the following standard circuit.



$$i_0 = 4e^{-50t} \text{ A}, \quad t \geq 0$$


$$v_0 = L \frac{di_0}{dt} = (5 \times 10^{-3})$$

$$(-2 \times 10^{-50t}) = -e^{-50t} \text{ V}, \quad t \geq 0^+$$

7.21 a) $v_1(0^-) = v_1(0^+) = 40V$, when steady state is reached the capacitor voltage is at 40V, the capacitor looks like an open circuit, no current flows through it.


When the switch moves to position b, initially the 4nF capacitor is uncharged, therefore the voltage across the capacitor is zero.

The circuit for $t \geq 0^+$

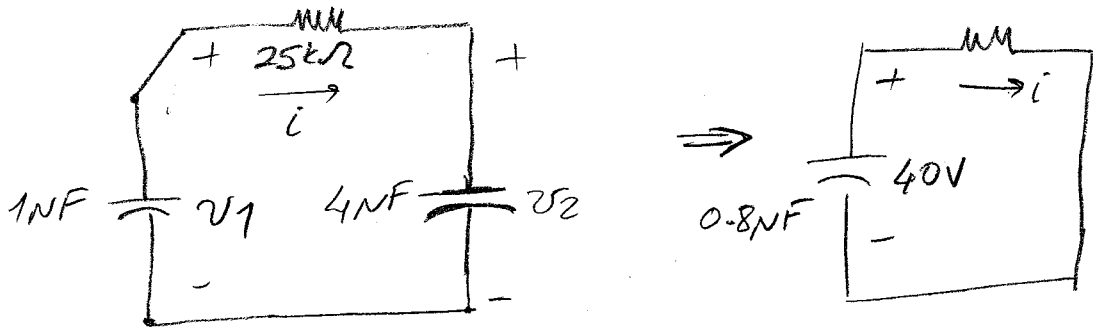

$$C_{eq} = (1)(4)/5 = 0.8nF \quad \tau = RC = (25 \times 10^3)(0.8 \times 10^{-6}) = 20ms$$
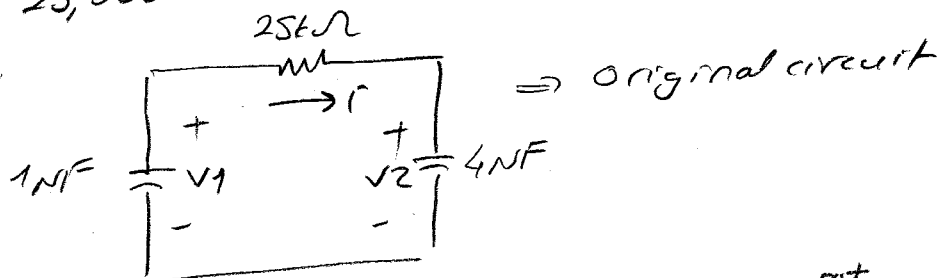
$$i = \frac{40}{25,000} e^{-50t} = 1.6e^{-50t} \text{ mA} \quad \frac{1}{\tau} = 50 \quad t \geq 0^+$$



$$v_1 = \frac{-1}{10^{-6}} \int_0^t 1.6 \times 10^{-3} e^{-50x} dx + 40 = 32e^{-50t} + 8V, \quad t \geq 0$$

$$v_2 = \frac{1}{4 \times 10^{-6}} \int_0^t 1.6 \times 10^{-3} e^{-50x} dx + 0 = -8e^{-50t} + 8V, \quad t \geq 0$$

(b) The energy stored in the 1nF capacitor can be found using the voltage value $v_1(0^-) = 40V$ and $W = \frac{1}{2} CV^2$,

$$W = \frac{1}{2} (10^{-6}F)(40V)^2 = 800nJ$$

$$(c) W_{trapped} = \frac{1}{2} (10^{-6})(8)^2 + \frac{1}{2} (4 \times 10^{-6})(8)^2 = 160nJ.$$

The energy dissipated by the $25k\Omega$ resistor is equal to the energy dissipated by the two capacitors; it is easier to calculate the energy dissipated by the capacitors (final voltage on the equivalent capacitor is zero):

$$w_{dis} = \frac{1}{2} (0.8 \times 10^{-6}) (40)^2 = 640 \text{ nJ}$$

$$\text{Check: } w_{strapped} + w_{dis} = 160 + 640 = 800 \text{ nJ;}$$

$$w(0) = 800 \text{ nJ.}$$


7.23 (a) $R = \frac{v}{i} = 4k\Omega$

(b) $\frac{1}{\tau} = \frac{1}{RC} = 25; \quad C = \frac{1}{(25)(4 \times 10^3)} = 10 \text{ nF}$

(c) $\tau = \frac{1}{25} = 40 \text{ ms}$

(d) $w(0) = \frac{1}{2} (10 \times 10^{-6}) (48)^2 = 11.52 \text{ mJ}$


7.25 (a) $t < 0;$

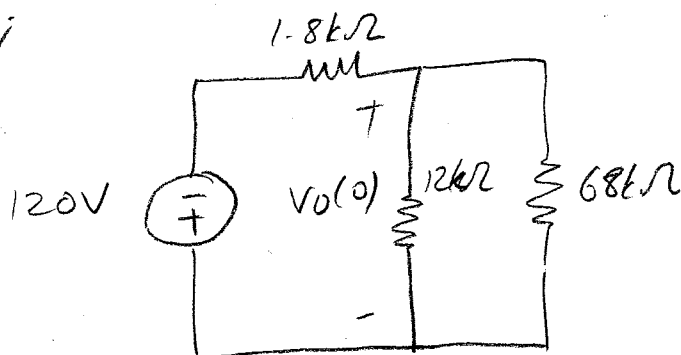

$$R_e = 12k \parallel 68k = 10.2k\Omega$$

$$v_0(0) = \frac{10,200}{10,200 + 1800} (-120) = -102 \text{ V}$$

$t > 0$

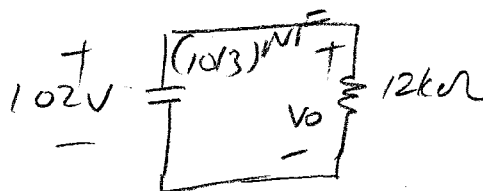

$$\tau = [(10/3) \times 10^{-6}] (12000) = 40 \text{ ms}; \quad \frac{1}{\tau} = 25$$

$$v_0 = -102e^{-25t} \text{ V}, \quad t \geq 0$$

$$P = \frac{v_0^2}{12000} = 867 \times 10^{-3} e^{-50t} \text{ W}$$

$$W_{\text{diss}} = \int_0^{12 \times 10^{-3}} 867 \times 10^{-3} e^{-50t} dt = 17.34 \times 10^{-3} (1 - e^{-50(12 \times 10^{-3})}) = 7.82 \text{ mJ}$$


$$1b) W(0) = \left(\frac{1}{2}\right) \left(\frac{10}{3}\right) (102)^2 \times 10^{-6} = 17.34 \text{ mJ}$$

$$0.75 W(0) = 13 \text{ mJ}$$

$$\int_0^{t_0} 867 \times 10^{-3} e^{-50t} dt = 13 \times 10^{-3}$$

$$\therefore 1 - e^{-50t_0} = 0.75; e^{50t_0} = 4; 50 t_0 = 27.73 \text{ ms.}$$

7.26 1a)

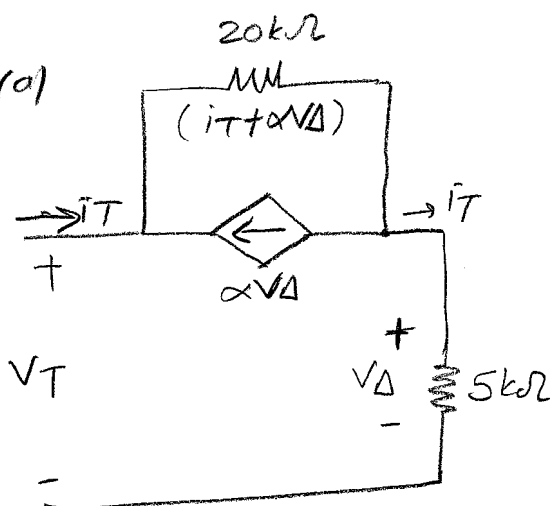

$$V_T = 20 \times 10^3 (i_T + \alpha V_D) + 5 \times 10^3 i_T$$

$$V_D = 5 \times 10^3 i_T$$

$$V_T = 25 \times 10^3 i_T + 20 \times 10^3 \alpha (5 \times 10^3 i_T)$$

$$R_{Th} = \frac{V_T}{i_T} = 25000 + 100 \times 10^6 \alpha$$


$$\tau = R_{Th} C = 40 \times 10^{-3} = R_{Th} (0.8 \times 10^{-6})$$

$$R_{Th} = 50 \text{ k}\Omega = 25,000 + 100 \times 10^6 \alpha$$


$$\alpha = \frac{25,000}{100 \times 10^6} = 2.5 \times 10^{-4} \text{ A/V}$$

$$1b) v_0(0) = (-5 \times 10^3)(3600) = -18 \text{ V} \quad t < 0$$

$t > 0$:

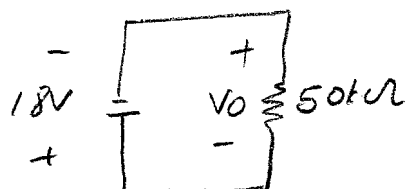
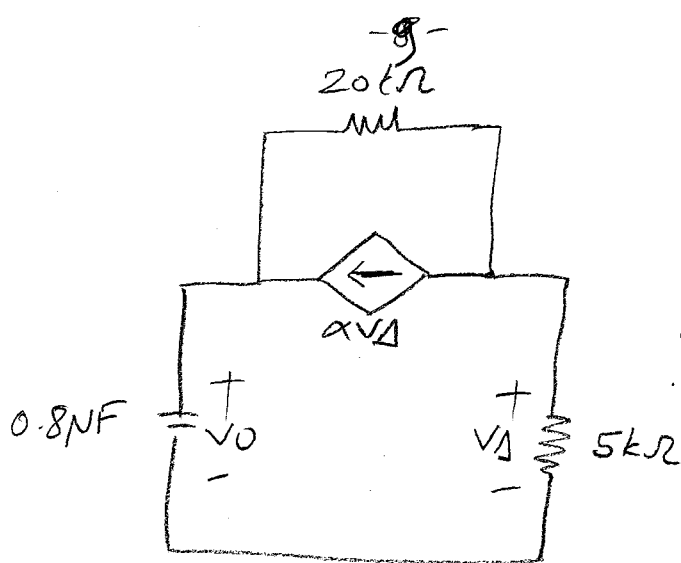
$$v_0 = -18e^{-25t} \text{ V, } t \geq 0$$




$$\frac{V_A}{5000} + \frac{V_A - V_0}{20000} + 2.5 \times 10^{-6} V_A = 0$$


$$4V_A + V_A - V_0 + 5V_A = 0$$

$$\therefore V_A = \frac{V_0}{10} = -1.8 e^{-25t} \text{ V, } t \geq 0^+$$

7.28

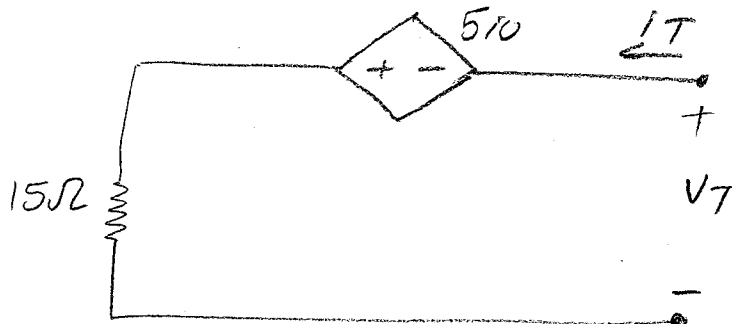
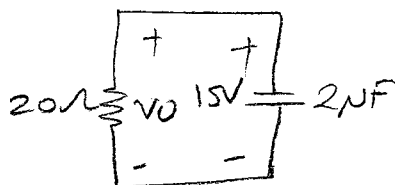
$$V_T = -5I_T + 5I_T = -20I_T = 20I_T \quad \therefore R_{Th} = \frac{V_T}{I_T} = 20\Omega$$



$$\tau = RC = 40\text{ns}; \quad \frac{1}{\tau} = 25,000$$


$$V_0 = 15 e^{-25,000t} \text{ V, } t \geq 0$$

$$I_0 = -\frac{V_0}{20} = -0.75 e^{-25,000t} \text{ A, } t \geq 0^+$$

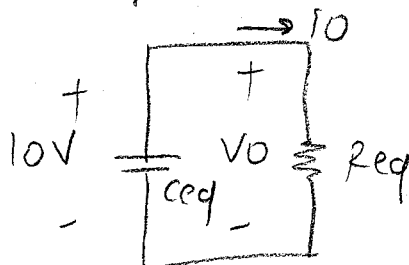7.29 (a) $C_{eq, \text{parallel combination}} = 0.2\text{nF} + 0.8\text{nF} = 1\text{nF}$

$$C_{eq} = \frac{1 \times 0.25}{1 + 0.25} = \frac{0.25}{1.25} = 0.2\text{nF}$$

$$R_{eq} = 0.4 + \frac{24 \times 16}{24 + 16} = 0.4 + \frac{384}{40} = 0.4 + 9.6 = 10\text{k}\Omega$$



$$\tau = 2\text{ms} \quad \frac{1}{\tau} = 500$$


$$V_0 = 10 e^{-500t} \text{ V, } t \geq 0$$

$$I_0 = e^{-500t} \text{ mA, } t \geq 0^+$$

$$i_{24\text{k}\Omega} = e^{-500t} \left(\frac{16}{40} \right) = 0.4 e^{-500t} \text{ mA, } t \geq 0^+$$

$$P_{24\text{k}\Omega} = (0.4 \times 10^{-3} e^{-500t}) (24,000) = 3.84 e^{-500t} \text{ mW}$$

$$W_{24\text{k}\Omega} = \int_0^{\infty} 3.84 \times 10^{-3} e^{-500t} dt = -3.84 \times 10^{-3} (10 - 1) = 3.84 \text{ mJ}$$


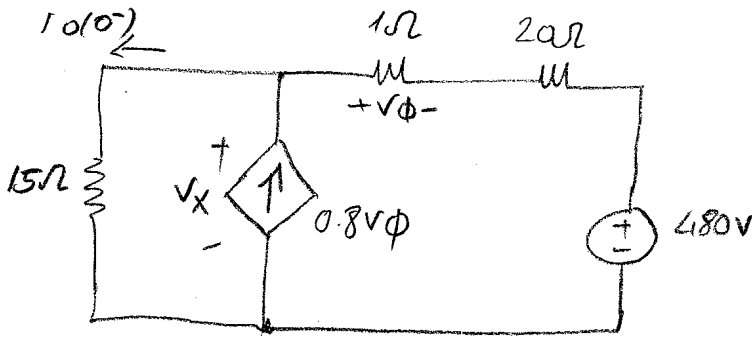
7.39 For $t < 0$ 

$$\frac{v_x}{15} - 0.8v_\phi + \frac{v_x - 480}{21} = 0 \Rightarrow v_\phi = \frac{v_x - 480}{21}$$

$$\frac{v_x}{15} - 0.8 \left(\frac{v_x - 480}{21} \right) + \left(\frac{v_x - 480}{21} \right)$$


$$= \frac{v_x}{15} + 0.2 \left(\frac{v_x - 480}{21} \right) = 21v_x + 3(v_x - 480) = 0$$

$$\therefore 24v_x = 1440 \quad \text{so} \quad v_x = 60V \quad i_0(0^-) = \frac{v_x}{15} = 4A$$

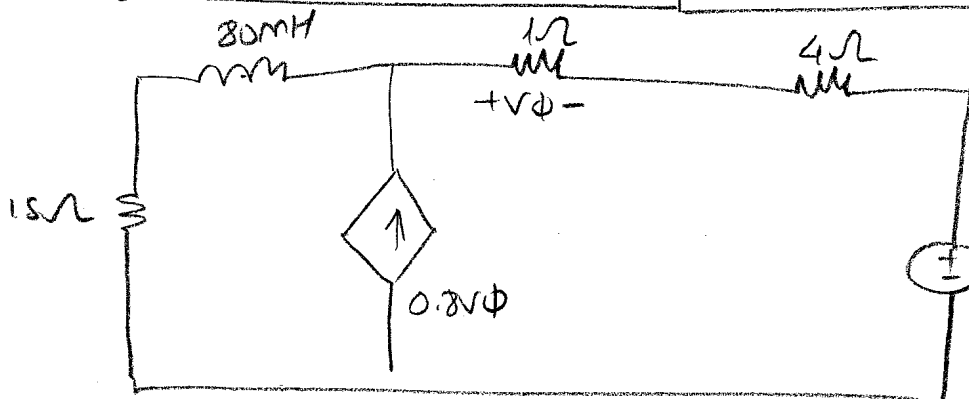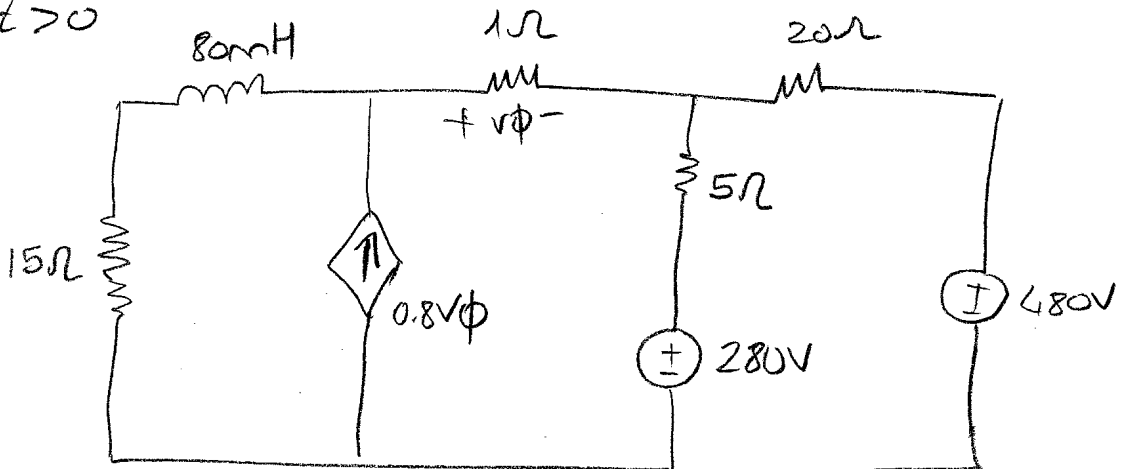
 $t > 0$ 

=16-

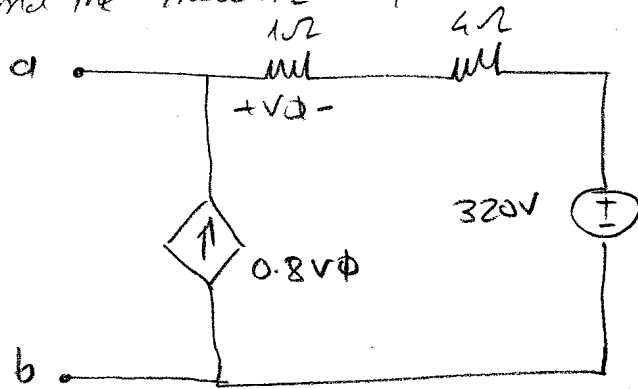We find the Thevenin equivalent with respect to a,b


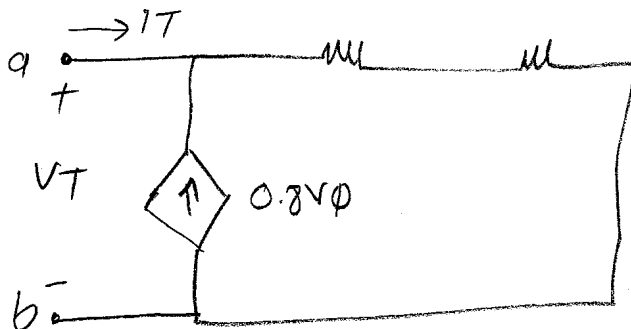
$$\frac{V_{Th} - 320}{5} - 0.8 \left(\frac{V_{Th} - 320}{5} \right) = 0 \quad V_{Th} = 320V$$




$$V_T = (i_T + 0.8V_\phi)(5)$$

$$= \left(i_T + 0.8 \frac{V_T}{5} \right) (5)$$

$$V_T = 5i_T + 0.8V_T \therefore 0.2V_T = 5i_T$$


$$\frac{V_T}{i_T} = R_{Th} = 25\Omega$$

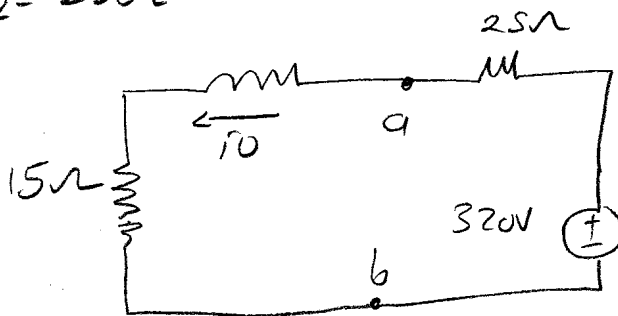

$$i_o(\infty) = 320/40 = 8A \quad \tau = \frac{80 \times 10^{-3}}{40} = 2ms, \quad 1/\tau = 500$$

$$i_o = 8 + (4 - 8)e^{-500t} = 8 - 4e^{-500t} A, \quad t \geq 0.$$

7.40 $t >$

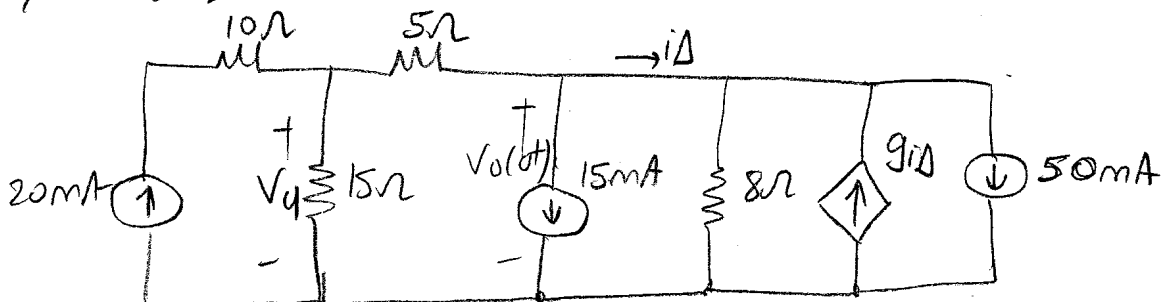

$$\frac{v_d}{15} + \frac{v_d - v_o(0^+)}{5} = 20 \times 10^{-3}$$

$$\therefore v_d = 0.75 v_o(0^+) + 75 \times 10^{-3}$$

$$15 \times 10^{-3} + \frac{v_o(0^+) - v_d}{5} + \frac{v_o(0^+)}{8} - 9i_d + 50 \times 10^{-3} = 0$$

$$13 v_o(0^+) - 8 v_d - 360 i_d = -2600 \times 10^{-3}$$

$$i_d = \frac{v_o(0^+)}{8} - 9i_d + 50 \times 10^{-3} \quad \therefore i_d = \frac{v_o(0^+)}{80} + 5 \times 10^{-3}$$

$$\therefore 360 i_d = 4.5 v_o(0^+) + 1800 \times 10^{-3}$$

$$8 v_d = 6 v_o(0^+) + 600 \times 10^{-3}$$


$$\therefore 13 v_o(0^+) - 6 v_o(0^+) - 600 \times 10^{-3} - 4.5 v_o(0^+) - 1800 \times 10^{-3} =$$

$$-2600 \times 10^{-3}$$

$$2.5 v_o(0^+) = -200 \times 10^{-3}; \quad v_o(0^+) = -80 \text{ mV}$$

$$v_o(\infty) = 0$$

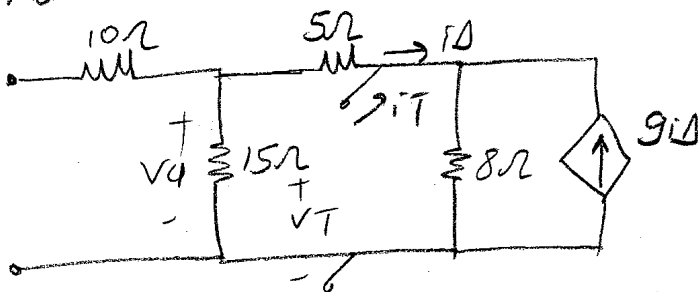Find the Thevenin resistance seen by the 4 mH inductor.



$$i_T = \frac{v_T}{20} + \frac{v_T}{8} - 9i_d$$

$$i_d = \frac{v_T}{8} - 9i_d \quad \therefore 10i_d = \frac{v_T}{8}; \quad i_d = \frac{v_T}{80}$$


$$i_T = \frac{v_T}{20} + \frac{10v_T}{80} - \frac{9v_T}{80}$$

$$\frac{i_T}{v_T} = \frac{1}{20} + \frac{1}{80} = \frac{5}{80} = \frac{1}{16} \text{ S} \quad \therefore R_{Th} = 16 \Omega$$

$$\tau = \frac{4 \times 10^{-3}}{16} = 0.25 \text{ ms}; \quad 1/\tau = 4000$$

$$\therefore v_o = 0 + (-80 - 0)e^{-6000t} = -80e^{-6000t} \text{ mV} \quad t \geq 0^+$$

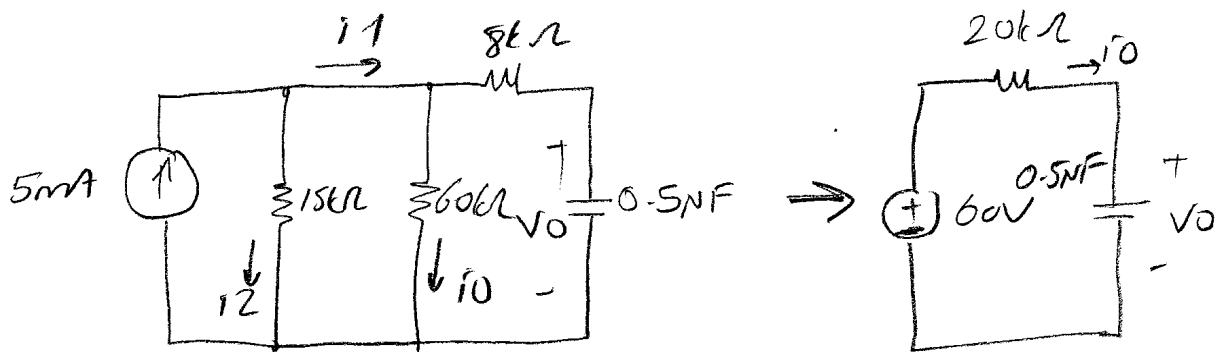7.68 (a) Simplify the circuit for $t > 0$ using source transformation.



$$R_{eq} = \frac{15 \times 60}{15 + 60} + 8 = 20k\Omega$$

Since there is no source connected to the capacitor for $t < 0$.


$$V_0(0^-) = V_0(0^+) = 0V$$

From the simplified circuit,

$$V_0(\infty) = 60V$$

$$\tau = RC = (20 \times 10^3)(0.5 \times 10^{-6}) = 10ms$$

$$\frac{1}{\tau} = 100$$

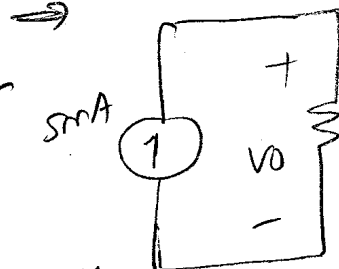

$$15 || 60 = 12k\Omega$$

$$V_0 = 5 \times 12 = 60V$$

$$V_0 = V_0(\infty) + [V_0(0^+) - V_0(\infty)]e^{-t/\tau} = (60 - 60e^{-100t})V, t \geq 0$$

$$(b) \quad i_C = C \frac{dV_0}{dt} = 0.5 \times 10^{-6} (-100) (-60e^{-100t}) = 3e^{-100t} mA$$

$$V_1 = 8000i_C + V_0 = (8000)(3 \times 10^{-3})e^{-100t} +$$

$$(60 - 60e^{-100t}) = 60 - 36e^{-100t} V$$

$$i_0 = \frac{V_1}{60 \times 10^3} = 1 - 0.6e^{-100t} mA, t \geq 0^+$$

$$(c) \quad i_1(t) = i_0 + i_C = 1 + 2.4e^{-100t} mA, t \geq 0^+$$

$$(d) \quad i_2(t) = \frac{V_1}{15 \times 10^3} = 4 - 2.4e^{-100t} mA, t \geq 0^+$$

-14-

$$(e) \quad i(0^+) = 1 + 2.4 = 3.4 \text{ mA} \quad \text{At } t = 0^+$$

$$R_e = 1\text{k} \parallel 60\text{k} \parallel 8\text{k} = 480\Omega$$

$$v_1(0^+) = (5 \times 10^{-3})(480\Omega) = 2.4 \text{ V}$$

$$i(0^+) = \frac{v_1(0^+)}{60,000} + \frac{v_1(0^+)}{8000} = 0.4 \text{ mA} + 3 \text{ mA} = 3.4 \text{ mA} \quad (\text{check})$$

$$7.6 \text{ y (a)} \quad v = I_s R + (V_0 - I_s R) e^{-t/RC} \quad v = \left(I_s - \frac{V_0}{R}\right) e^{-t/RC}$$

$$\therefore I_s R = 40, \quad V_0 - I_s R = -24 \quad \therefore V_0 = 16 \text{ V}$$

$$I_s - \frac{V_0}{R} = 3 \times 10^{-3}; \quad I_s - \frac{16}{R} = 3 \times 10^{-3}; \quad R = \frac{40}{I_s}$$

$$\therefore I_s - 0.4 I_s = 3 \times 10^{-3}; \quad I_s = 5 \text{ mA}$$

$$R = \frac{40}{5} \times 10^3 = 8 \text{ k}\Omega$$

$$\frac{1}{RC} = 2500; \quad C = \frac{1}{2500 \times 8} = \frac{10^3}{20 \times 10^3} = 50 \text{ nF};$$

$$\tau = RC = \frac{1}{2500} = 400 \text{ ns}$$

$$16) \quad v(\infty) = 40 \text{ V} \quad w(\infty) = \frac{1}{2} (50 \times 10^{-9}) (1600) = 40 \text{ nJ}$$


$$0.81 w(\infty) = 32.4 \text{ nJ}$$

$$v^2(t_0) = \frac{32.4 \times 10^{-6}}{25 \times 10^{-9}} = 1296; \quad v(t_0) = 36 \text{ V}$$

$$40 - 24 e^{-2500 t_0} = 36; \quad e^{-2500 t_0} = 6; \quad \therefore t_0 = 716.70 \text{ ns}$$

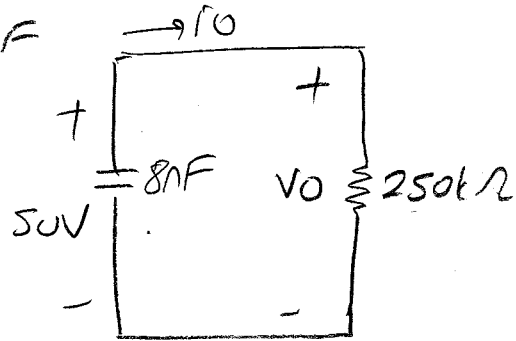7-50 (a) For $t > 0$ The equivalent circuit

$$C_{eq} = \frac{40 \times 10}{40 + 10} = 8 \text{ nF}$$



$$\tau = RC = 250 \times 10^3 \times 8 \times 10^{-9} = 2 \text{ ms} \quad \frac{1}{\tau} = 500$$

$$V_0 = 50 \times e^{-500t} \text{ V}, \quad t > 0$$

$$(b) \quad I_0 = \frac{V_0}{250,000} = \frac{50e^{-500t}}{250,000} = 200e^{-500t} \text{ nA}$$

$$V_1 = \frac{1}{C_1} \int_0^t I_0(\tau) d\tau + V_1(0^+)$$

$$= \frac{-1}{40 \times 10^{-9}} \times 200 \times 10^{-6} \int_0^t e^{-500\tau} d\tau + 50 =$$

$$10e^{-500t} + 40 \text{ V}, \quad t > 0$$